

Power Quality FACTS
unit-I

→ **what is power Quality** :- is defined as the fitness of electrical power supplied to consumers. However, there can be different definitions based on different perspectives. Ex:- Manufacturers of electrical equipments define power quality as those features of electrical power supply which are needed for proper working of equipments.

power supplies define power quality in terms of reliability. from the point of view of electrical consumers "any power problem manifested in voltage, current or frequency deviation in failure or misoperation of consumer equipment".


→ **Different types of power quality disturbances:-**

- Transients
- Short duration Variation
- Long duration Variation
- Voltage Imbalance
- wave form distortions
- Voltage fluctuations
- power frequency Variations.

Power Quality Problems in distribution System:-

- Correcting Power Quality Problems requires an understanding of all power distribution system components and how a problem in one component can cause a problem in other components.
- Distribution system components include transformer, distribution lines, switch boards, disconnects, circuit breakers, fuses etc.
- Electrical distribution system must deliver quality power to loads, if the loads are to operate properly for their rated life-time and performance.
- Quality power is power delivered to a load that is within the load specific voltage, is capable of delivering enough current under any operating condition, and includes minimal, not damaging changes.
- ^{Poor} power quality is power delivered to a load that includes excessive & damaging changes such as voltage drops, voltage unbalance, transients and harmonic distortion.

Power Quality Problems:-

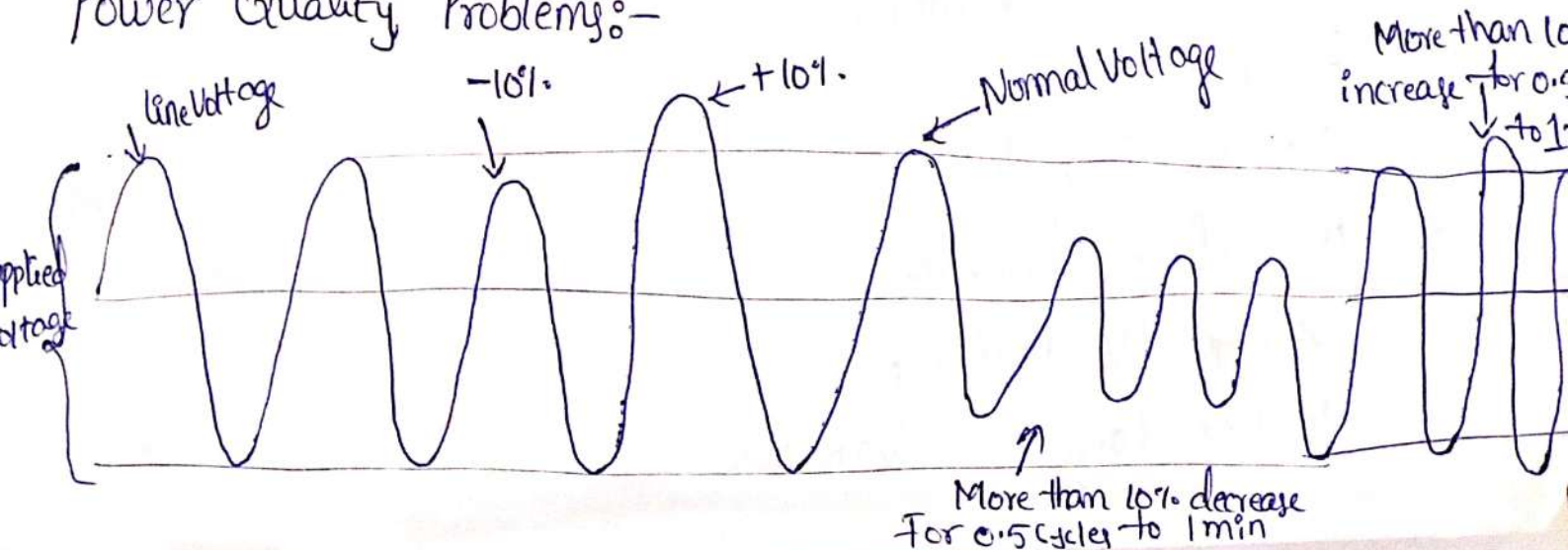

Power Quality:-

- It is the ability of electrical grid or network to supply a clean and stable power to the consumers.
- Electrical power quality mainly involves voltage, frequency and wave form.

Power Quality = Voltage Quality

→ Good power quality can be defined as:

→ Steady Supply Voltage within prescribed range.

Ex:- 1-ph supply is for domestic consumers.

230V RMS, 50Hz & pure sinusoidal voltage.

→ Steady AC frequency close to rated value.

Ex:- 48.5 to 50Hz.

→ Smooth voltage wave form.

Power Quality Problems:-

- Poor load Power factor
- Harmonic contents in load
- Notching in load variation
- DC offset in load voltage
- Unbalance loads.
- Supply Voltage distortion
- Voltage Sag/Swell
- Voltage Flicker.

Different Power Quality Terms:-

- Transients:- short duration problem due to sudden change of state.
- Short duration Voltage Variation
- long " " "
- Voltage imbalance in unbalance
- waveform distortions.
- Voltage fluctuations.
- Power freq Variations.

Power Quality Problems and their Causes:-

Broad Categories	Specific Categories	Method & Characterisation	Typical Causes.
1) Transients	Impulsive	Peak magnitude, rise time and duration.	Lightning Strokes, transformer energisation Capacitor Switching.
	Oscillatory	peak magnitude, freq components.	Line or Capacitor or load Switching.
2) Short duration Voltage Variation (up to 1 min)	Sag.	Magnitude, Duration	Ferroresonant transformer, single L-G faults.
	Swell	Magnitude, Duration.	" " "
	Interruption	Duration.	Temporary (self-cleaning) faults.
	under voltage.	Magnitude, Duration.	Switching on loads, Capacitor deenergisation
Long duration Voltage Variation. (More than 1 min)	over voltage.	" "	Switching off loads, Capacitor energisation (very large loads)
	Sustained interruptions	Duration.	faults.

4) Voltage Imbalance

5) wave form distortion

Harmonics

Notching

DC-offset

Voltage flicker

Symmetrical components.

THD, Harmonic Spectrum.

THD, "

Volts, Amps.

Frequency & co-occurrence,
modulating freq.

Single-phase loads, 1-phasing
Condition.

Adjustable speed drives,
and other non-linear
loads.

Power electronic converters.

Geo magnetic disturbances,
half-wave rectification.



Arc furnances, arc lamps.

phase unbalance - is the unbalance that occurs when power lines are out of phase.

phase unbalance of a 3- ϕ power system occurs when 1- ϕ loads are applied, which causes one or two of the lines to carry more or less of the load. So this can be avoided by proper installation process.

A power quality meter can be used to check phase unbalance of load on power lines. An unbalance begins to occur when additional 1- ϕ loads are added to the system. This unbalance causes the 3- ϕ lines to move out of phase so the lines are no longer 120° apart.

phase unbalance

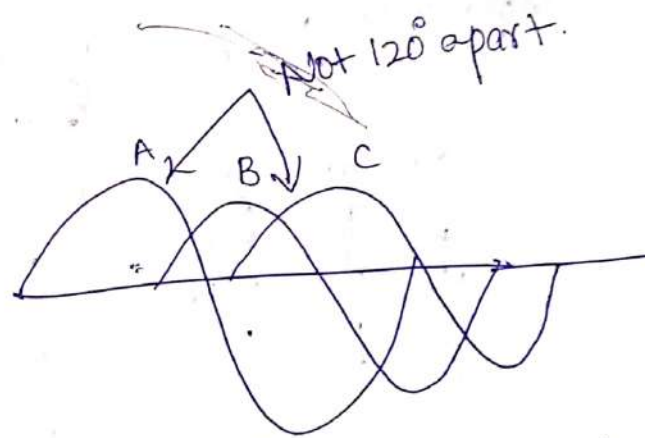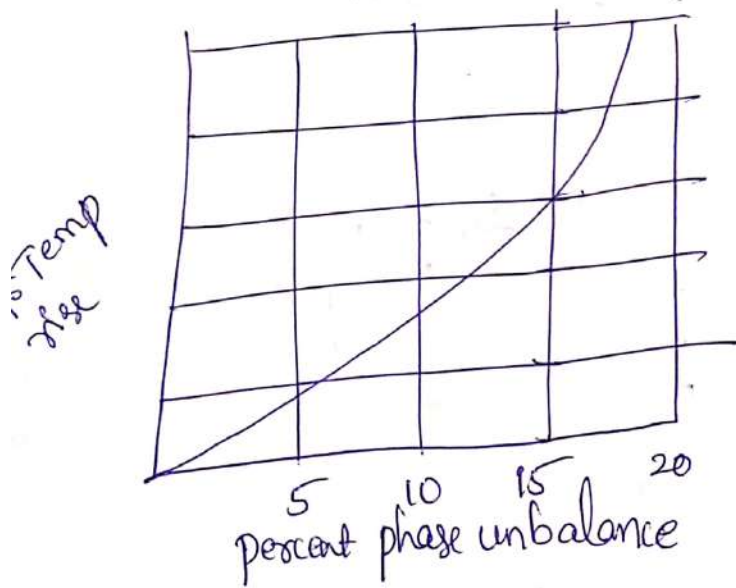

phase unbalance causes 3- ϕ motors to run at temperatures higher than listed ratings.

The greater the phase unbalance

the greater the temp rise. High Temp causes insulation break and other related problems.


→ A 3- ϕ motor operating in an unbalanced circuit cannot deliver its rated horse power.

- power quality problems can damage electrical equipment and to unsafe operating conditions like
 - Improper phase seq of motor.
 - Voltage unbalance.
 - Voltage surges.


Single phasing:- is the operation of a motor is designed to operate on 3- ϕ but it is only operating on two phases bcz one phase is lost.

Single phasing occurs when one of the 3-lines leading to a 3- ϕ motor does not deliver voltage to the motor. Single phasing is the maximum condition of voltage imbalance in a distribution system.


Motor wdg damage

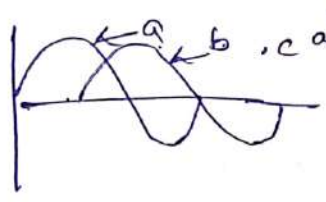

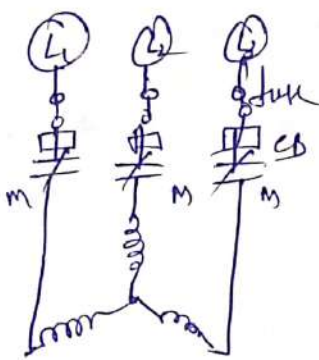- is reduced by using:-
 - properly sized dual element fuse and heaters.
 - An electronic phase loss monitor




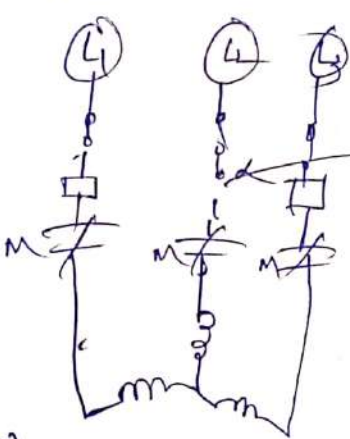
Normal motor operation (All 3 wdg carry motor current)



Single phasing causes severe burning & distortion to one or two wdg

→ Improper phase seq:- means changing the sequence of any two phases

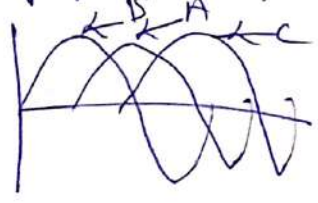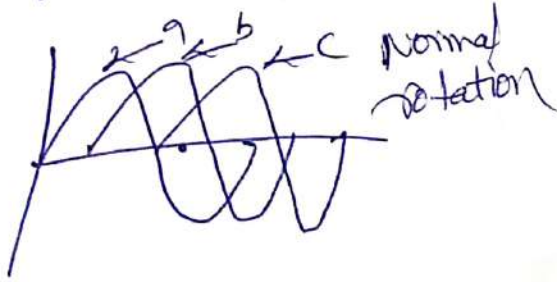(phase reversal) in a 3- ϕ motor ckt. Improper phase sequences ~~change~~ reverse the motor rotation. Improper phase seq can damage motor internally.



Currents unbalance

$$L_1 = 58 \text{ A}$$

$$L_2 = 53 \text{ A}$$

$$L_3 = 57 \text{ A}$$

$$V_a = \frac{58 + 53 + 57}{3} = \frac{168}{3} = 56 \text{ A}$$

$$I_d = 56 - 53 = 3$$


$$I_d = \frac{3}{56} \times 100 = 5.35\%$$

Transients and Steady State Variations in Voltage and Frequency:-

- Transient over voltages in electrical transmission and distribution networks result from the unavoidable effect of lightning strike and network switching operations.
- Response of an electrical network to a sudden change in network conditions.
- Oscillation is an effect caused by a transient response of a system or circuit. It is a momentary event preceding the steady state during a sudden change of load.

So this can be avoided by using proper lightning arrester, surge arresters in distribution system.

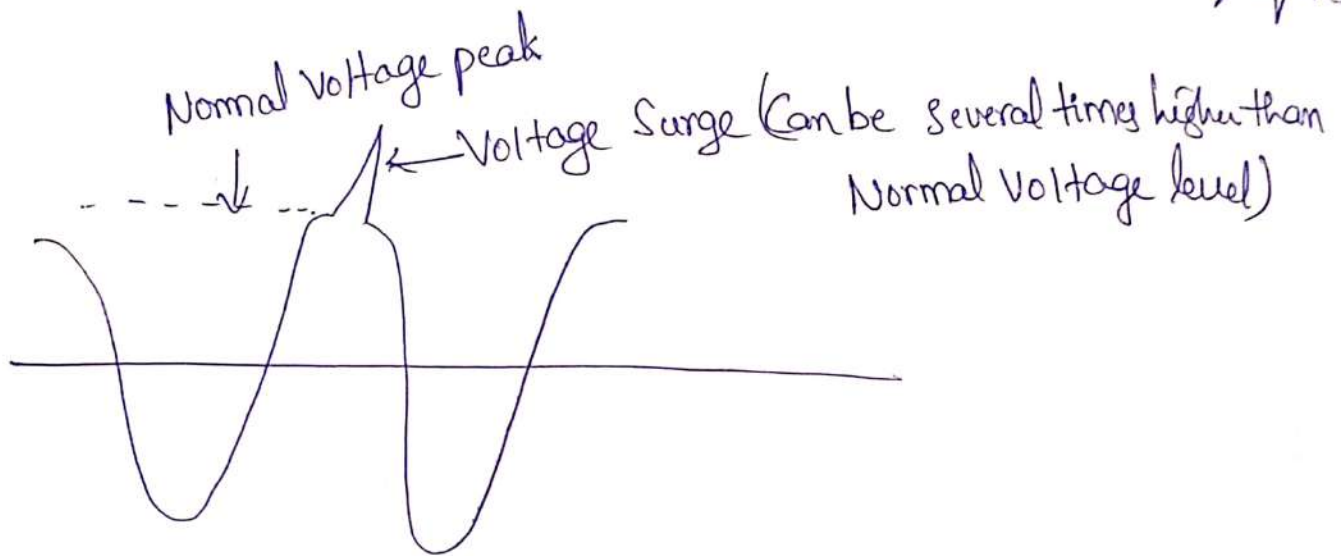→ Voltage Surges can also occur due to normal switching of high power circuit, this causes lesser damage to electrical equipments.



$$\text{Normal Voltage Peak} = \text{Normal Rms Voltage} \times 1.4$$

$$\text{Normal Rms} = 230\text{V}$$

$$\text{peak Voltage} = 1.4 \times 230 = 322\text{Volts.}$$

$$V_{RY} = 442\text{V}$$

$$V_{YB} = 474\text{V} \quad V_{BR} = 456\text{V.}$$

$$V_a = \text{Add} = 442 + 474 + 456 = 1372 / 3 = 457.\text{V}$$

Find voltage deviation $474 - 457 = 17\text{V.}$

$$V_d =$$

$$\text{Voltage unbalance} = \frac{V_d}{V_a} = \frac{17}{457}$$

$$= \frac{17}{457} \times 100 = 3.72\%$$

2, 3, 10, 11
9, 11, 13, 14, 15

+5% -5%
Slightly decrease →

DC Motor performance Characteristics

	+10% Below		-10% above	
	Shunt	Comp	Shunt	Comp
Stator Current	-15%	-15%	+15%	+15%
F.L Current	-5%	-6%	+5%	+6%
Motor torque	+12%	+12%	-8%	-8%
Motor ebb	Decrease		Increase	
Speed	Increase		Decrease	
Temp rise	"		"	

Voltage Surges:- A Voltage Surge is a higher-than normal v_{tg} that temporarily exists on one or more power lines. Lightning is a major cause of large voltage surges.

A lightning surge on a power line comes from direct lightning hit or induced voltage. The lightning energy moves in both directions on the power line like rapidly moving wave.

A travelling surge of lightning energy causes a large voltage rise in short duration of time period. This causes destroying the insulation and burning out of motor wdg.

Voltage Variation characteristics.

Performance characteristics	10% Above Rated Voltage	10% Below Rated Voltage
→ Starting current	+10% to +12%	-10% to -12%
→ Full-load current	-7%	+11%
→ Motor torque	+20% to +25%	-20% to -25%
→ Motor efficiency	Little change →	
→ Speed	+1%	-1.5%
→ Temp rise	+3°C to +4°C	+6°C to +7°C

A motor operates satisfactorily with a voltage variation of $\pm 10\%$ from the voltage rating listed on the nameplate.

AC freq Variation:- AC motors are rated for operation at specific frequencies. Motor performance is affected when freq varies from a motor's rated freq. A motor operates satisfactorily with a freq variation of $\pm 5\%$.

5% above Rated freq	5% below rated freq
-5 to -6%	+5% to +6%
-1%	+1%
-10%	+11%
Slightly increase →	

Long duration Voltage Variation: - These are defined as the RMS Variations in the Supply Voltage at fundamental frequency for period more than 1min.

These are classified as.


Over Voltage: - An over voltage is a 10% increase in RMS Voltage for more than 1min.

under Voltage: - An under voltage is a 10% decrease in RMS Voltage for more than 1min.

Sustained interruption: - It happens when the Supply Voltage becomes zero for more than 1min.

Voltage Imbalance: ^{Vtg unbalance} - In the Case of Voltage imbalance, the ^{& currents} Voltages, ~~of~~ the three phases of the Supply are not equal in magnitude.

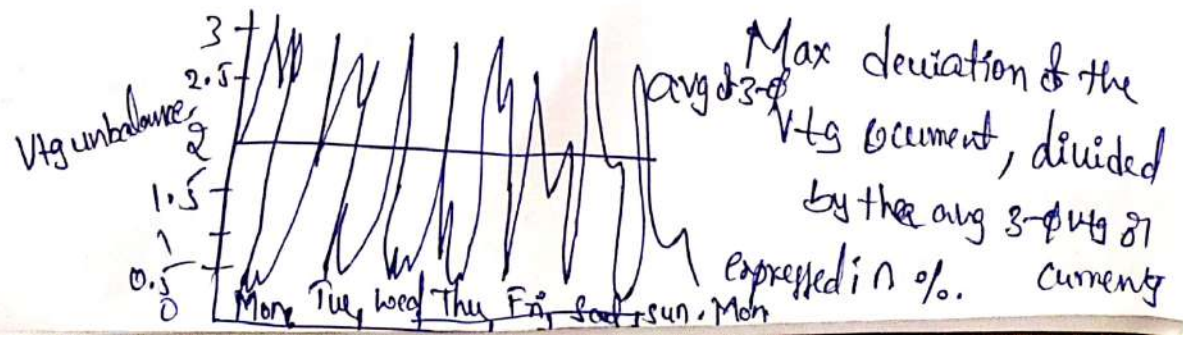- Voltages of three phases may not even be equally displaced.
- The primary Cause of Voltage imbalance is the single phase loads in three phase circuits and ^{unequal} equal line parameters.
- These are restricted to within 5%.





Waveform Distortion:— Steady state deviation in Voltage or current waveform an ideal sine wave.

Dc offset:— The major cause of dc offset in power systems are geomagnetic disturbance and half wave rectification.

Harmonics:— Power electronic loads like UPS, adjustable speed drives etc. usually cause harmonics. measure is (THD)

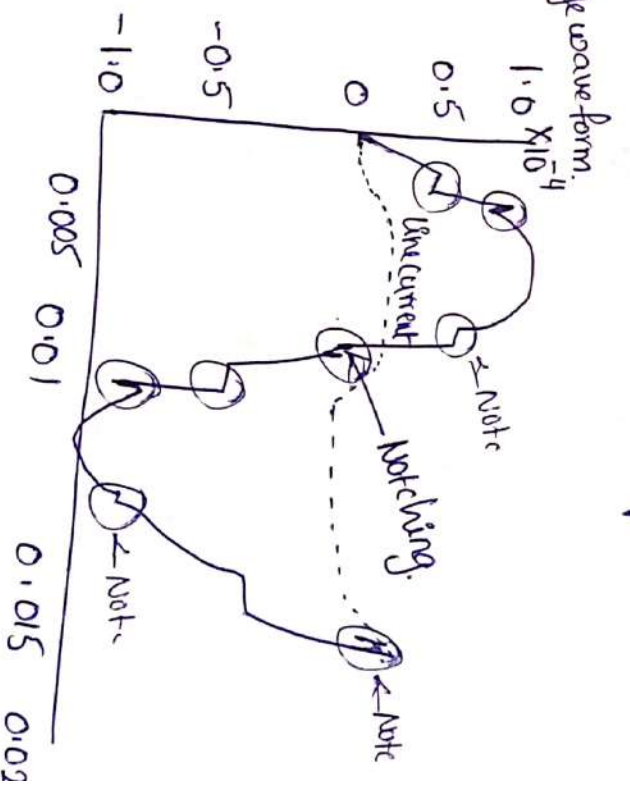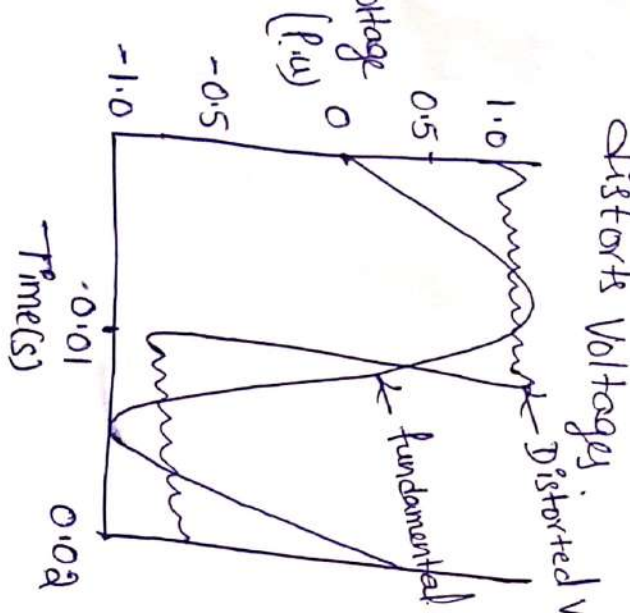Notching:— It is a periodic voltage distortion due to the operation of power electronic converters when current commutates from one phase to other. During this period there is momentary short circuit b/w the two phases that distorts voltage.



Voltage Distortion limit

Bus Voltage:

69kV to 161kV

P.u Voltage for n-th harmonic

3.0
1.5

Voltage (THD)%

5.0
2.5


Voltage fluctuations:-

- These are systematic random variations in supply voltage.
- A very rapid change in the supply voltage is called voltage flicker. This is caused by rapid variations in load current due to application of non-linear loads.

Power Frequency Variations:-

- These variations are usually caused by rapid changes in the load connected to the system.
- The maximum tolerable variation in supply frequency is often limited within $\pm 0.5 \text{ Hz}$.
- The frequency is directly related to the rotational speed of the generator.

Most Common PQ Prob.

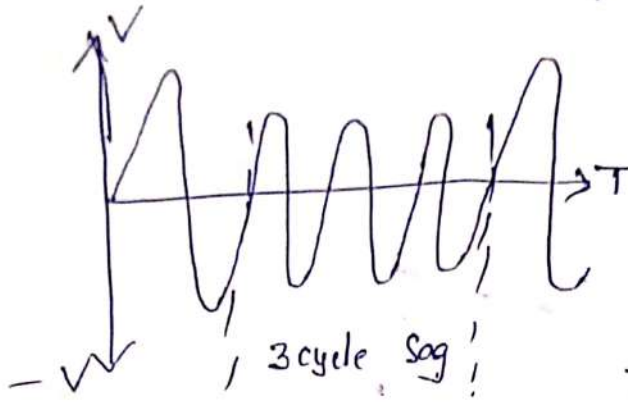

Sag

- Dip
- Consumer loads.
- either 1-φ or 3-φ
- 3 to 30 cycles.
- 0.1 to 0.9 pu.
- 0.5 cycle to 1 min.
- L-G, L-L & Symmetric

Swells

V & T $\frac{1}{10}$ to 1.1 & 1.8 P.U.

- 0.5 to 1 min.
- Single L-G faults, unbalanced phase, Capacitor banks etc.
- unbalanced faults, transients, shutdown & large loads.

Damages to sensitive equipments.

Interruption: - failure of equipment, Power by faults, trees, cars, striking lines or poles, human errors

Consequences: - stoppage of all equipments.


Transients:- A Transient is short duration problem due to sudden change of state.

Classified in to 2 types.
 Ex:- Lightning strike & Switching operations.

① Impulsive transient:- is a sudden, non-power freq change


→ in Voltage, Current etc. It is unipolar in nature.

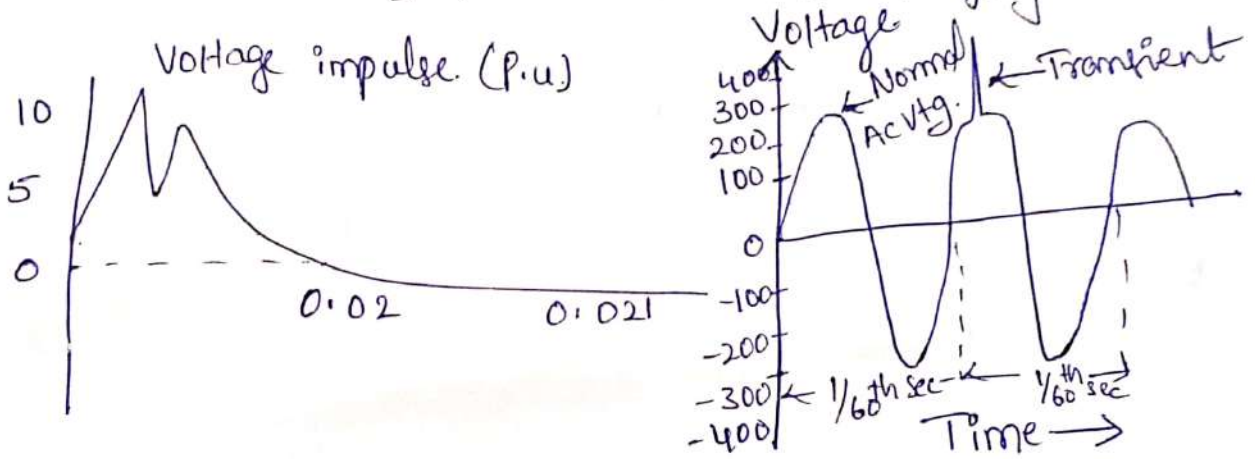→ It has very fast rise time and decaying time.



② Oscillatory transient:- It is bi-polar in nature.

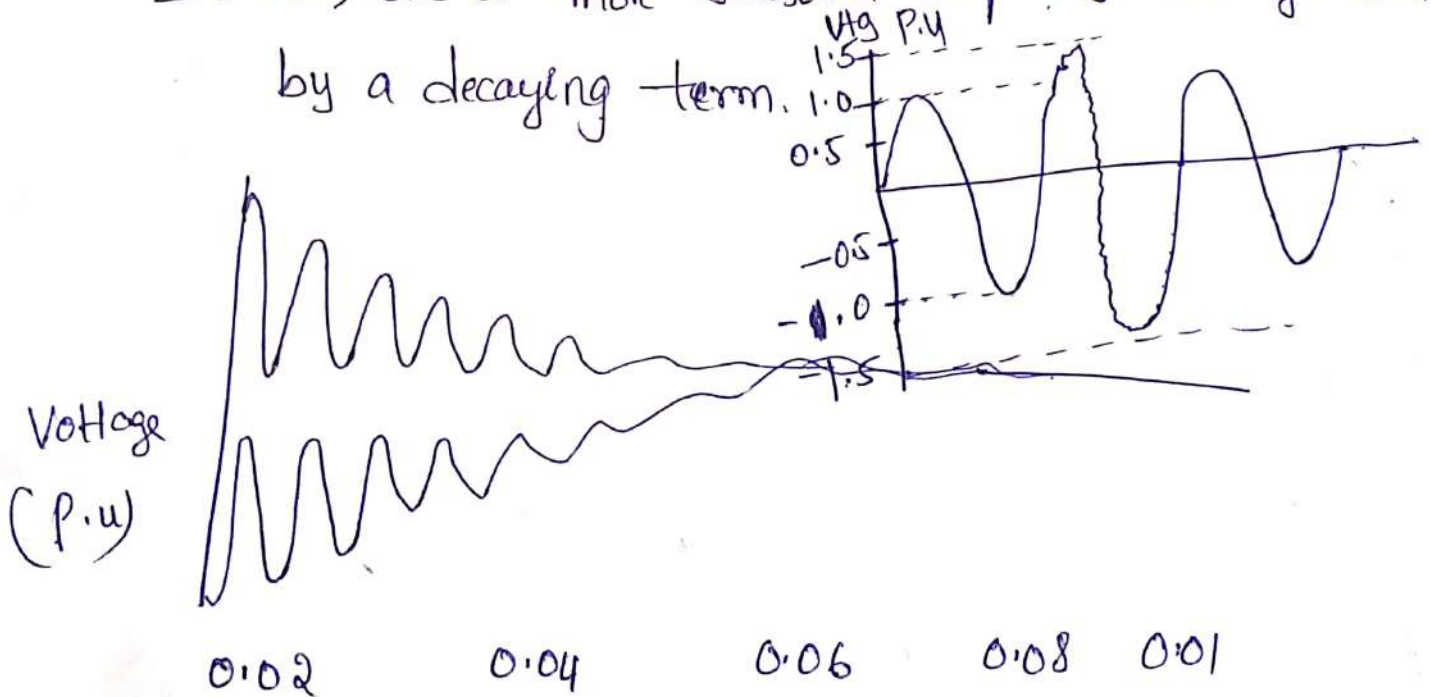It has one or more sinusoidal components that get multiplied by a decaying term.



Short duration Voltage Variation:— typically sustain for a few cycles up to 1 min.


→ usually such variations are caused by faults, energisation of large loads, and intermittent loss connection in wiring.

Classified as



Voltage Sag:— It is defined as fundamental frequency decrease in supply voltage magnitude for a short duration (5 cycles to 1 min) 0.1 to 0.9 p.u in rms

Voltage Swell:— defined as increase of fundamental frequency voltage magnitude for a short duration.

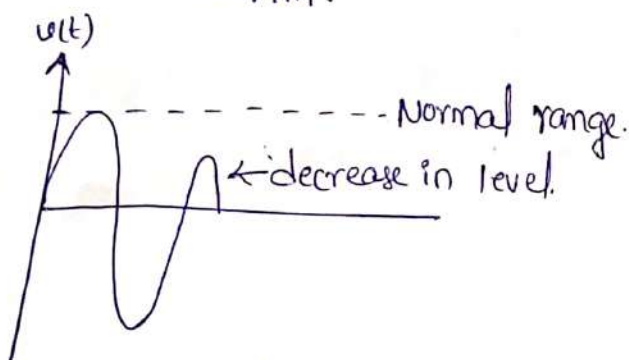Interruptions:— It occurs when supply voltage or load current decreases to less than 0.1 per unit for a period of less than 1 min.



Voltage Sag.

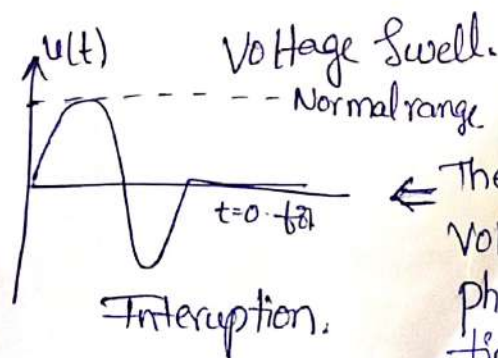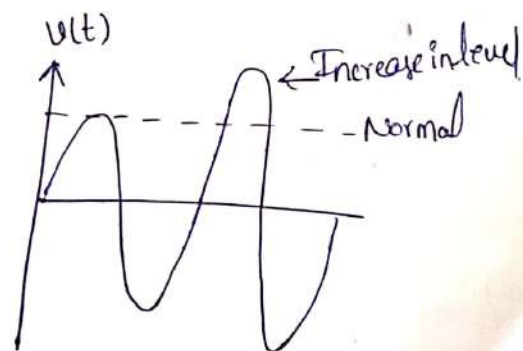

← The complete loss of voltage on one or more phase conductors for a time less than 1 min.

UNIT-III

static shunt compensators SVC & STATCOM.

objectives of shunt compensation:-

→ The main function of reactive shunt compensator is to improve the steady-state transmittable power and voltage stability along the line.

→ The purpose of reactive compensation is to change natural electrical characteristics of the transmission line and improve the line performance to meet the load demand.

→ shunt compensators as fixed or mechanically switched reactors are used for minimise line over voltage under light load conditions, capacitor controllers is used to minimise voltage ~~under~~ levels under heavy load conditions.


→ The main objective of shunt compensation is a t/n on system is to increase the transmittable power. This may improve

steady-state transmission characteristics as well as stability of the system.



→ var compensation is used for voltage regulation at the mid point of the line and at the end of the line to prevent Vtg instability, dynamic voltage control to improve transient stability and damp power oscillations.

End of line voltage support to prevent voltage


instability :-

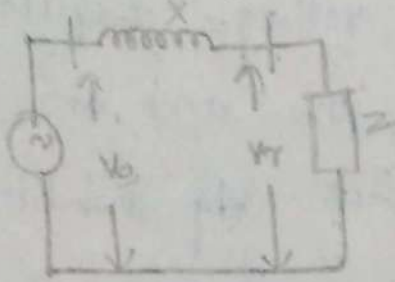

fig(a) without using any compensator

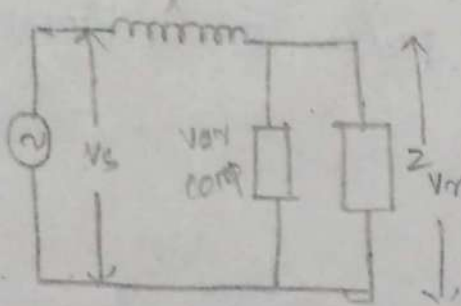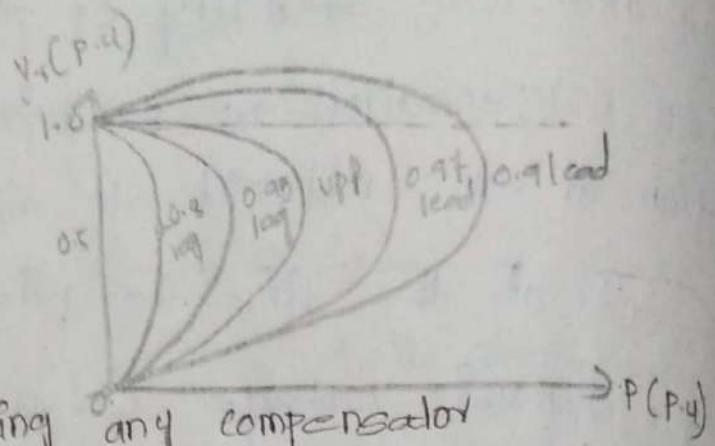

fig(b) with using compensator.

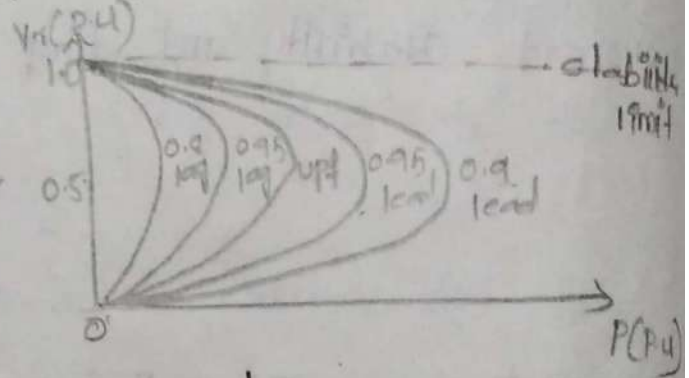

fig(i) shows without using any compensator, the

fig(i) shows sim

with line reactance " X " and load impedance " Z "

The plot is drawn b/w terminal vlg and power at various load p.f ranging from 0.8 lag to 0.9 lead.

→ The nodes point at each plot given for a specific p.f represents vlg for instability.

→ WKT vlg stability limit decreases with inductive load and \uparrow with capacitive load

fig (b) shows that using shunt reactive compensator of radial line is to be connected \parallel to the load



→ shunt reactive compensation can effectively increase the V_L stability limit by supplying reactive load. & resulting terminal V_L .

$V_s - V_r = 0$ shown in fig b.

→ Reactive shunt compensation is used in practice to regulate the voltage at a given bus against load variation.

→ Improvement of transient stability:

(a)

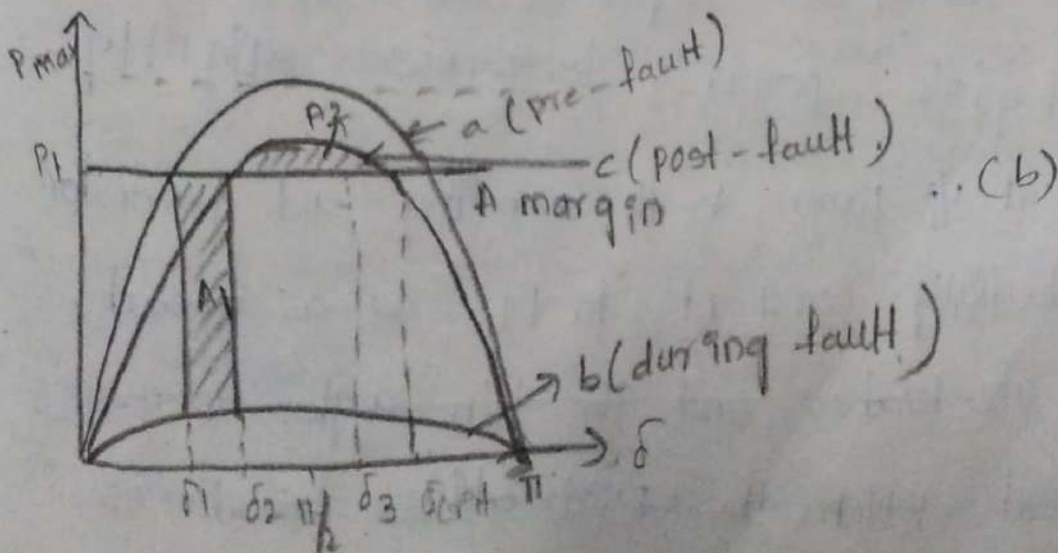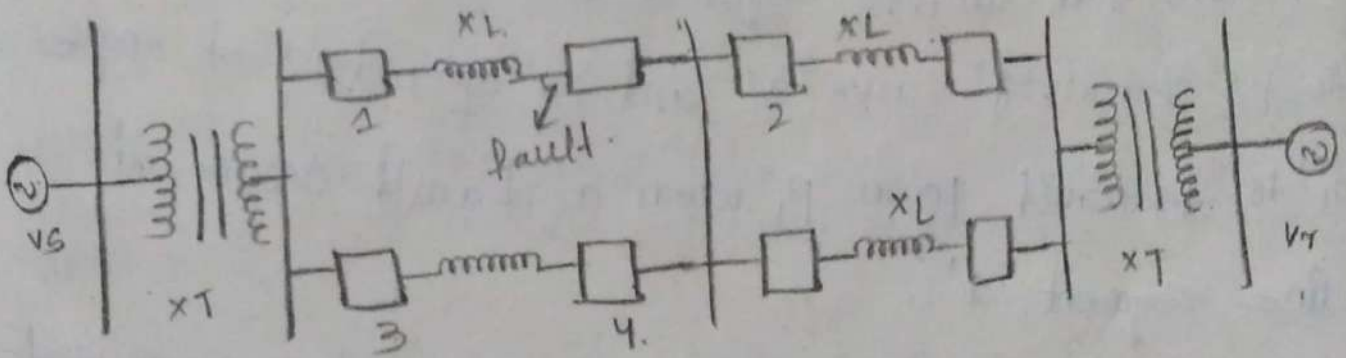


→ Illustration of the equal area criteria for transient stability of a two m/c, two-line power system

→ shunt compensation will be able to change the power flow in the system during and following disturbances is as to increase the transient stability limit and provide effective power oscillation damping


The potential effectiveness of shunt on transient stability improvement can be conveniently evaluated by the "equal area criteria".

→ Assume that complete system is characterised by the "P" versus δ curve "a" and is operating at angle δ_1 to transmit power P_1 when a fault occurs at line segment "1".

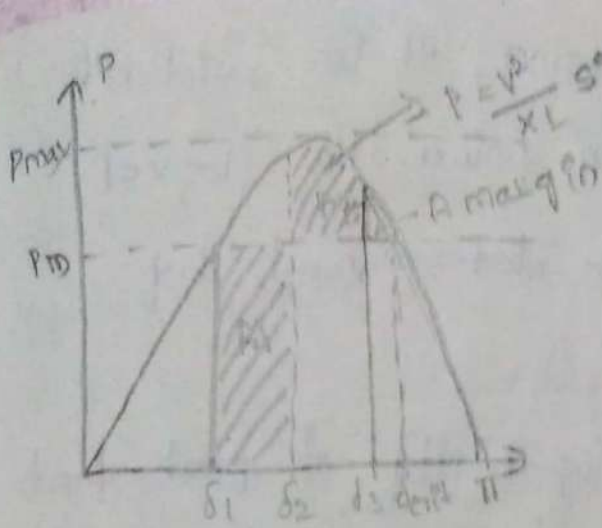→ During the fault the system is characterised by the "p" electric power decreases slightly while mechanical \dot{p} power to the sending end generator remains substantially constant to P_1 . as a result, the generator accelerates and the δ angle increases from δ_1 to δ_2 at which the protective breakers disconnect the faulted line segment "1" and the sending end generator 'absorbs' accelerating



(c)

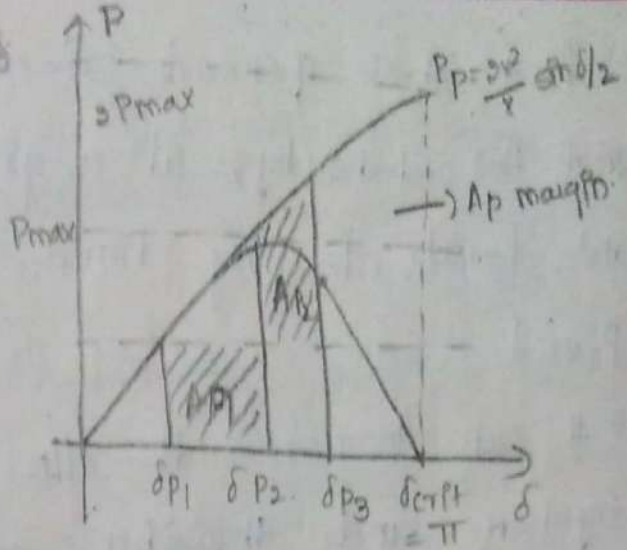

(d)

energy represented by area A_1

→ After fault clearing without line segment "1" the degraded system is characterized by P vs δ curve "c". At one angle δ_2 on curve "c" the transmitted power exceeds the mechanical \dot{V}_P power P_1 and the sending end generator starts to decelerate forever angle δ further increase due to the kinetic energy stored in the m/c.

→ The max angle reached at $\delta_3 = \delta_{critical}$, beyond which the decelerating energy would not balance the accelerating energy and synchronism b/w the sending end and receiving end could not be restored.

The area "A margin" between δ_3 & $\delta_{critical}$ represent the transient stability margin of the system.

⇒ From above general discussion, it is evident that the stability, at a given power t/n level and fault clearing time is determined by P vs d.

→ It can increase the t/n capability of post-fault system and thereby enhance transient stability.


→ Comparison of fig "c" & "d" shows increase in the transient stability to the ideal mid point compensation with not restricted var q/p can provide by effective segmentation of the t/n line. If uncompensated sys has transient stability margin, shunt comp sys has increase the transmittable without decreasing this margin.

→ 23/4/22. Methods of Controller VAR Generation.

In this 2 types of controllers is there.

i) static VAR compensator.

ii) static VAR generators

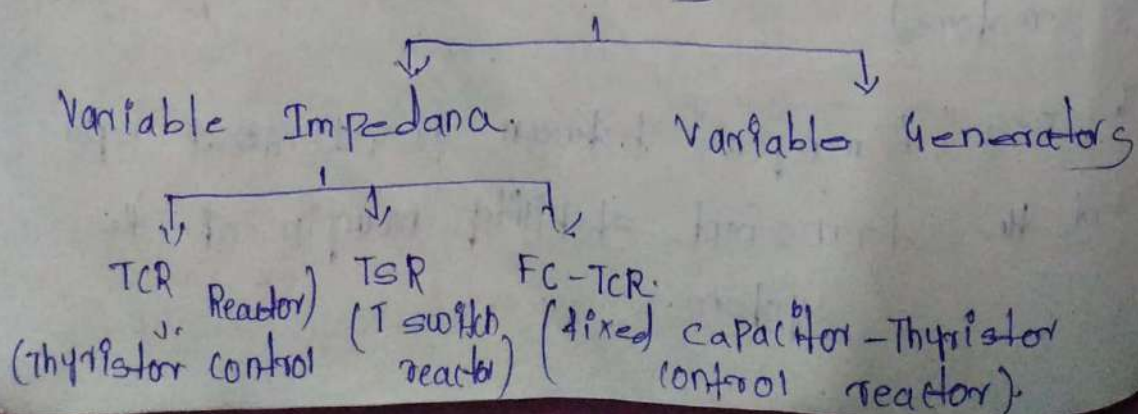

i) SVG :-

whose o/p is varied so, has to maintain/control the specific parameters of the electrical power system.


→ It is a sufficiently functioning device it will draw a Reactive current from an Alternating power source.

→ The control I/P of VAR Gen's can be arbitrary (within in the operating range). Reactive current Impedance/ power to the

Reference the SVG delivers at it's o/p → the SVG is used as power amplifier it faithfully produces the Required signal at the desired power levels.

Variable Impedance type.

Static VAR Generator :-

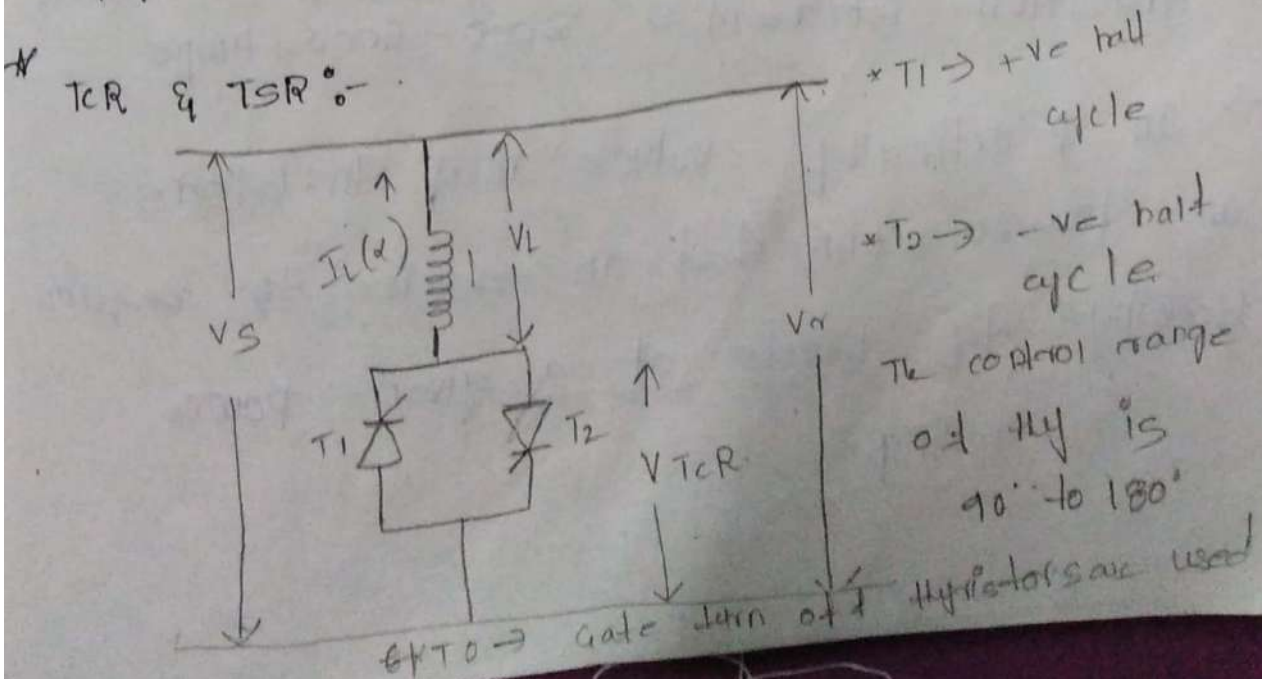

- two thyristors are connected in the anti parallel (T_1 & T_2) GTO (Gate turnoff thyristor)
- series connected with air cored Reactor is shown in fig.
- T_1 will conduct during the +ve half cycle & T_2 will conduct during the -ve half cycle.
- the control Range of thyristors is 90° to 180°
- fig ① shows single phase, thyristor controlled Reactor it consists of fixed air cored Reactor of Inductance (L). In a bidirectional thyristor valves (switches)
- currently available thyristor are drawn Vtg range $400V - 900V$
- conduction currents $3000 - 6000$ Amps.
- In practically valves may thyristors are 10-20 connected in series to require blocking Vtg levels at a given power rating.

operation:-

→ Thyristor valve coming into the conduction by applying gate pulses to same polarity.

→ The valve automatically blocks after the AC current crosses to 0, unless the gate signal is re applied.

→ It will operate on natural commutation (or) line commutation the current in the reactor can be controlled from max to zero by the method of thyristor delay angle control.

→ The thyristor valve is delay with respect to the heat of applied voltage in each half cycle, at the duration of current control.

$$V_s = V_L + V_{TcR} \quad \text{--- (1)}$$

$$V_s = V_L \quad \text{--- (2)}$$

V_{TcR} = There is no drop voltage


$$\therefore V_s = V_L = L \frac{di}{dt} \quad \text{--- (3)}$$

$$V_s(t) = V \cos \omega t$$


$$\begin{aligned}
 i_L(t) &= \frac{1}{L} \int_{\alpha}^{\omega t} v_S(t) dt \\
 &= \frac{1}{L} \int_{\alpha}^{\omega t} V \cos \omega(t) dt \\
 &= \frac{V}{L} \int_{\alpha}^{\omega t} \cos \omega t dt \\
 &= \frac{V}{L} \left[\frac{\sin \omega t}{\omega} \right]_{\alpha}^{\omega t}
 \end{aligned}$$

$$i_L(t) = \frac{V}{\omega L} [\sin \omega t - \sin \alpha]$$

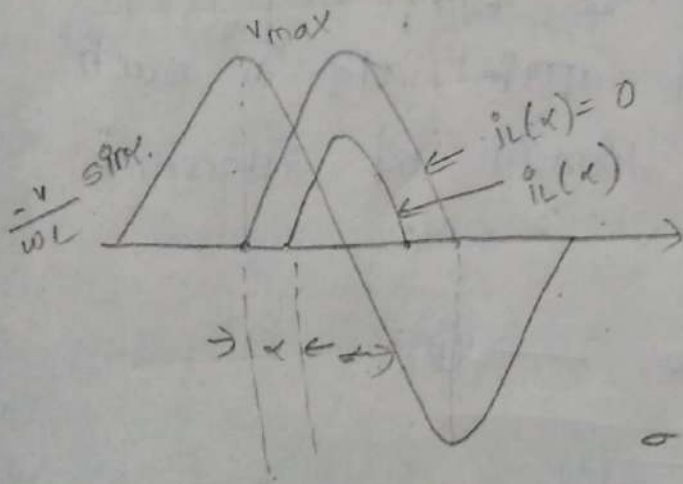If current flowing inductor is 1 sec the absorption capacity of VAR ↑ sec




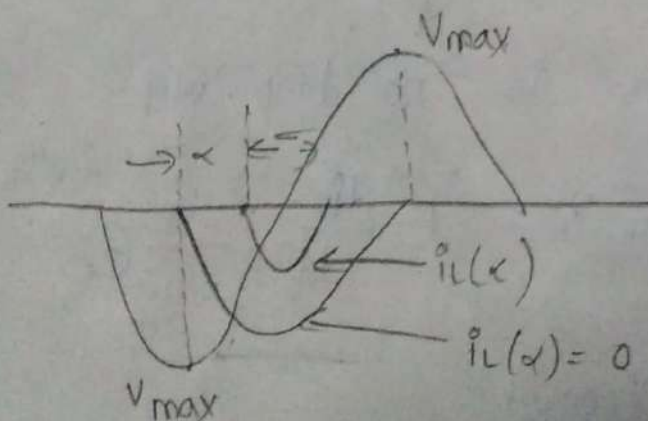$\omega t \frac{V}{\omega L} \sin \alpha$
 $\alpha \rightarrow$ firing angle
 \rightarrow conduction angle
 $\pi - \alpha \rightarrow +ve$ half cycle



Above fig shows delay angle firing angle controlled for +ve & -ve half cycles the method of current controlled during the +ve & -ve half cycles shown in above figure. when the v_d is max. at fig (\downarrow max) at that current in the inductor $i_L(\alpha) = 0$ still not stop to absorb the reactive power.

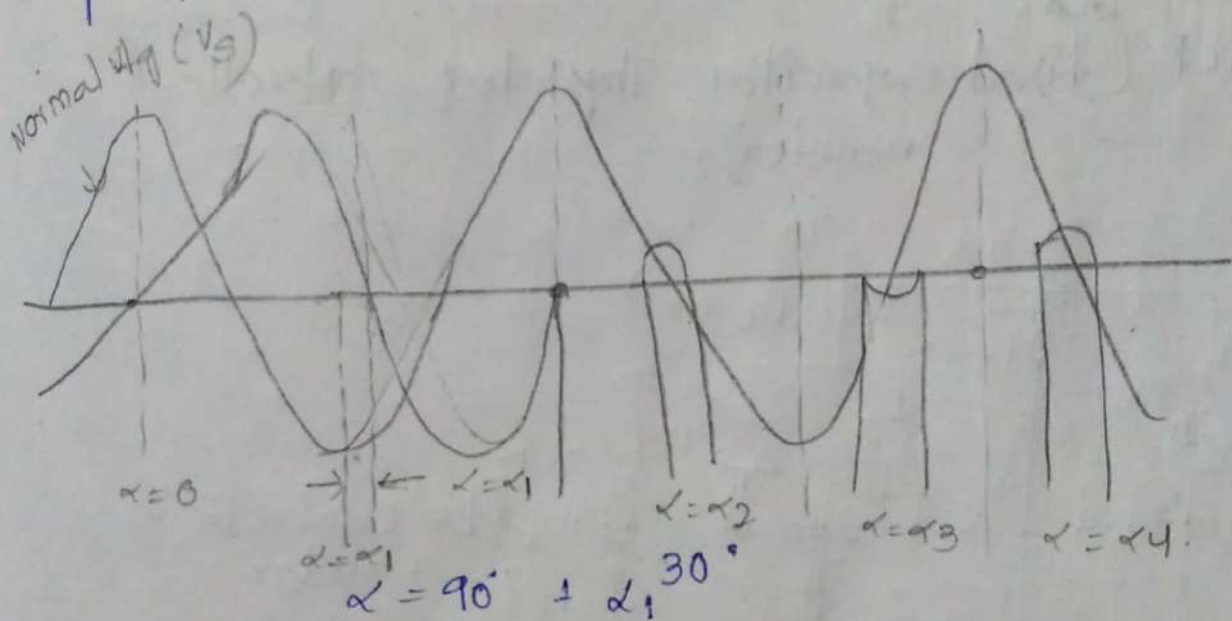It starts from $\alpha = 90^\circ$ to 180° upto that period only inductor. It stores the reactive power



Positive half cycle $\rightarrow (\alpha \leq \omega t \leq \pi - \alpha)$

Negative half cycle $\rightarrow (\pi + \alpha \leq \omega t \leq 2\pi - \alpha)$

When ever $\alpha \rightarrow \uparrow$ ses from 0° to max value


$$\alpha = 0, \alpha = \alpha_1, \alpha = \alpha_2, \alpha = \alpha_3, \alpha = \alpha_4$$

* By \uparrow ses the ' α ' the conduction angle
 \downarrow ses and also current flowing inductor
 is \downarrow ses the amplitude

$$I_{CF}(\alpha) = \frac{V}{\omega L} \left(1 - \frac{2}{\pi} - \frac{1}{\pi} \sin 2\alpha \right) \quad \text{--- (3)}$$

31/5/22 from eqn $\frac{V}{\omega L} [\sin \omega t - \sin \alpha]$

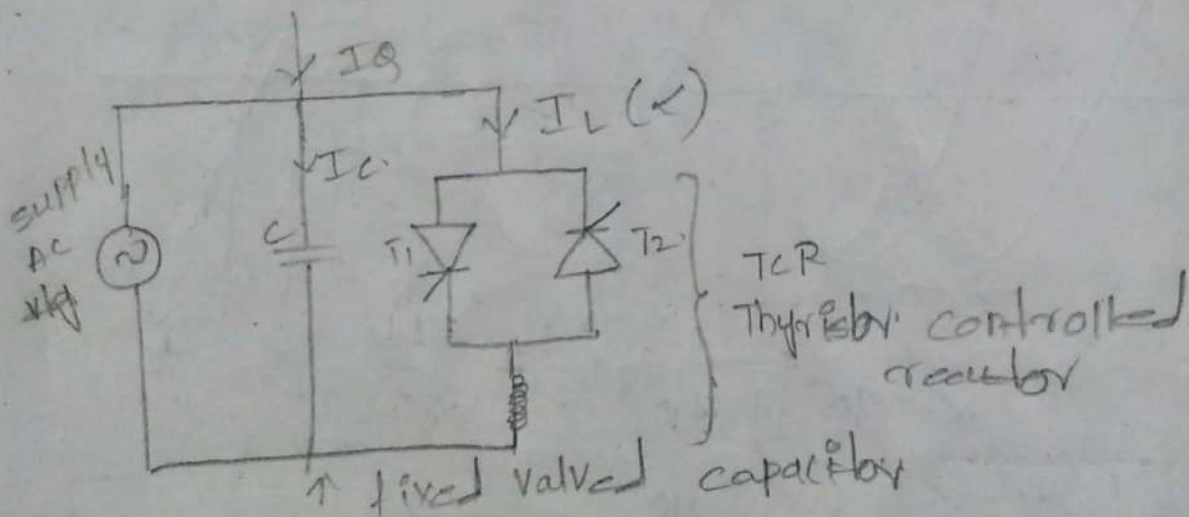FC-TCR (fixed capacitor Thyristor controlled reactor).



$$I_Q = I_C + I_L(\alpha)$$

Above fig shows the fixed capacitor - TCR.

* Above fig shows

(a) without using coupling ILL.

f.c. "Qc" oppose the variable. var generation (Qc). absorption to provide required total

var of $Q = Q_{LF}(\alpha) - Q_c$

1) when ever $\alpha = 180^\circ$ TCR is fully off state in this cond'n. The capacitor only generate reactive power in to the bus


$\therefore Q = 0 - Q_c$


2) under the vpf cond'n there is no absorption and gen of RP.

$\rightarrow Q_{LF}(\alpha) = Q_c$, the resultant $Q = 0$. There is no gen, no absorption of RP.

3) when ever $\alpha = 90^\circ$ in this cond'n TCR is in fully on state. The absorption of RP is maximum.

functional controlled of f.c.-TCR.

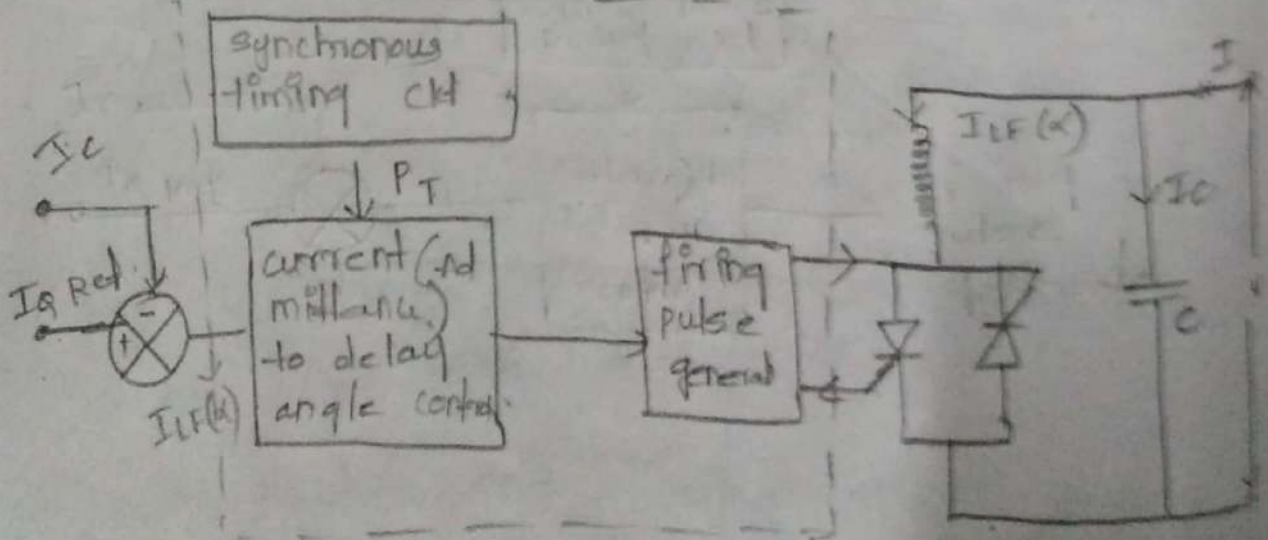

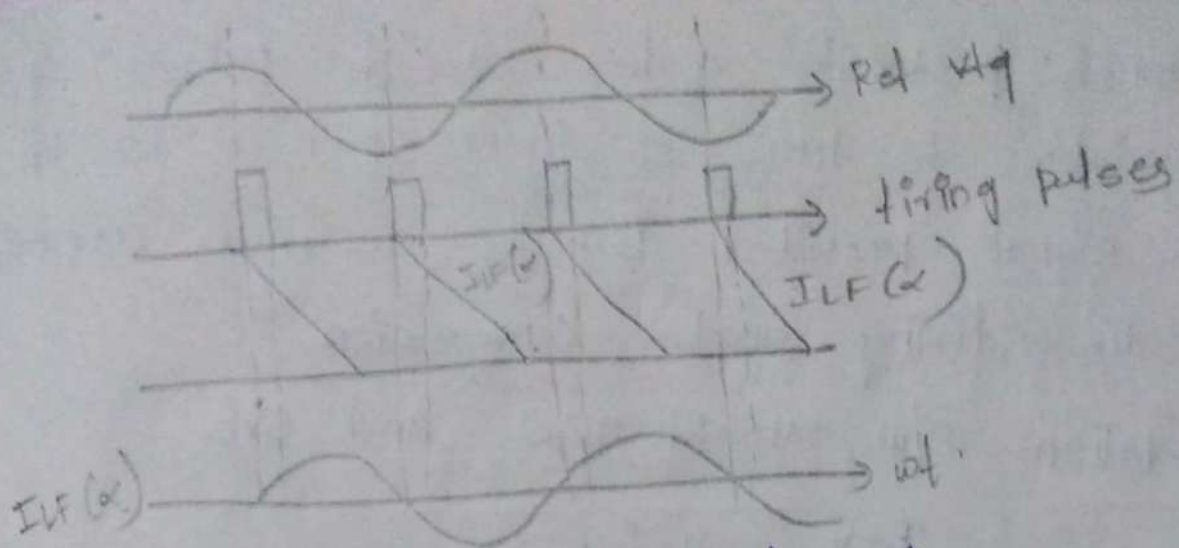

→ The control of Thyristor control in FC-TCR VAR generator need to provide 4 basic

1) synchronous timing:

This can be provided by phase locked loop ckt, that turns in synchronism with AC sys V_g and gen timing pulses wrt to V_g .

2) Reactive current (or) admittance) to firing angle conversion.

3) computation of reactor current $ILF(\alpha)$ from total o/p current,

$$I_Q = I_c - ILF(\alpha)$$

→ In this +ve → inductive o/p current
 -ve → capacitive o/p current.

4) Thyristor pulse generation. This is done by the firing pulse generator.

→ which produces gate current pulses for thyristor to turn on in response to the o/p signal provided by the reactive current to the firing angle conversion.

Relation B/w susceptance and SVC

$$I_{SVC} = V \cdot j B_{SVC}$$



$$B_{SVC} = B_c + B_{TCR}$$

$$B_{TCR} = 0$$

$$\alpha = 180^\circ$$

$$B_{SVC} = B_c$$

$$V = V_{ref}$$

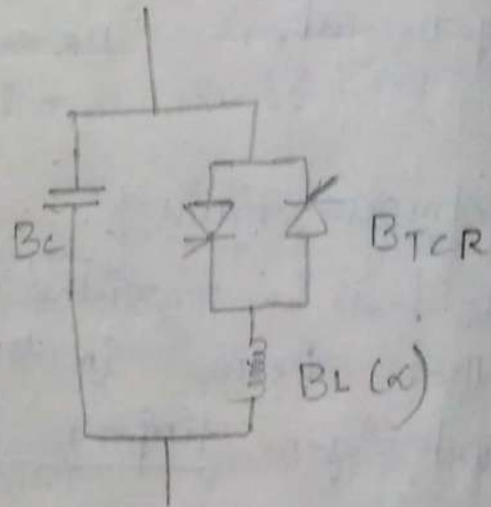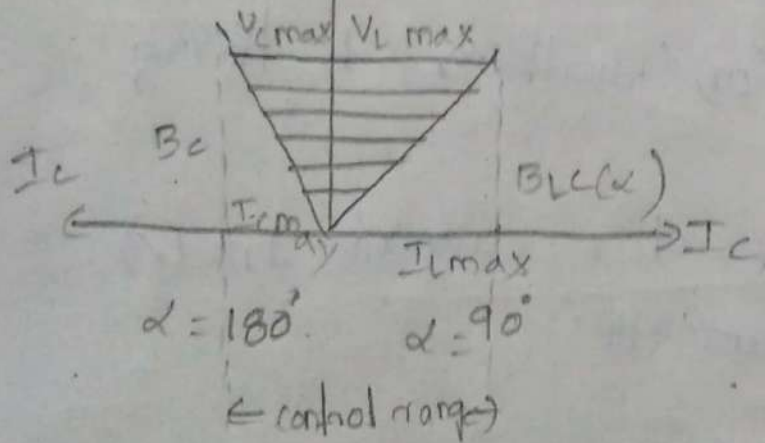

V-I char's of FC-TCR.

$B_c \rightarrow$ capacitive admittance.

$B_L \rightarrow$ maximum inductive admittance


$I_{Lmax} \rightarrow$ inductive current limit

$I_{Cmax} \rightarrow$ capacitive current limit.

$$\alpha = 90^\circ$$

$$B_{TCR} = \max$$

(b) FC-TCR with coupling TIT.

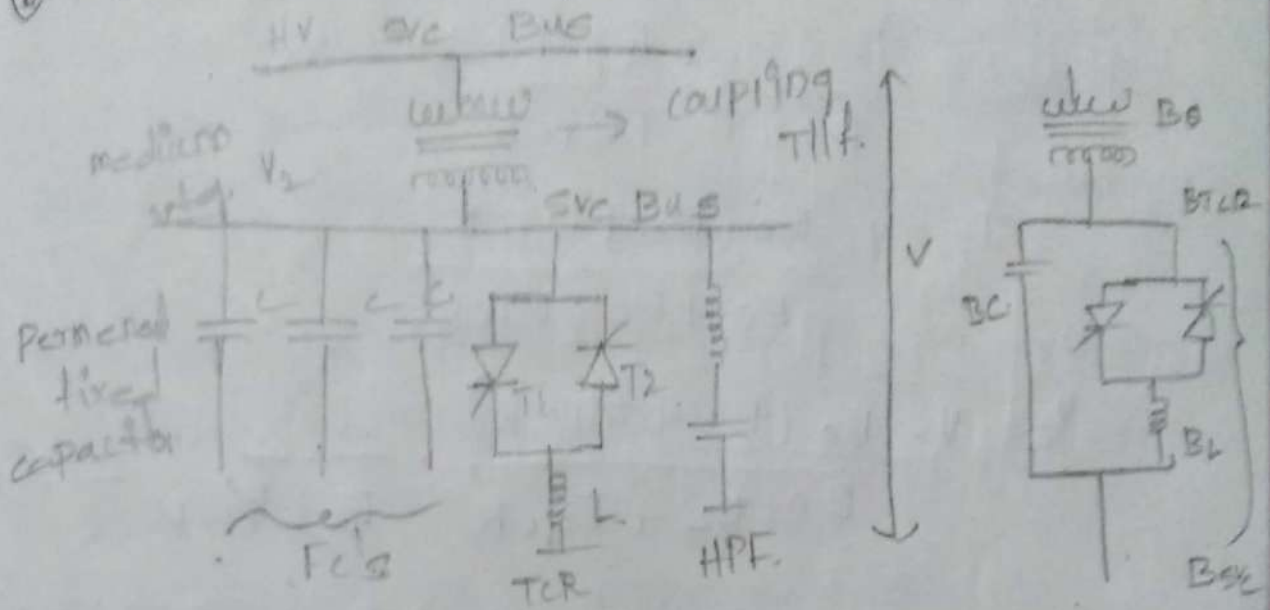

$$\Rightarrow B_{SVC} = \frac{B_0 (B_c + B_{TCR})}{B_0 + B_c + B_{TCR}} \quad \text{--- (1)}$$

divide Nr & Dr with B_0

$$B_{SVC} = \frac{1}{1 + \frac{B_c + B_{TCR}}{B_0}} (B_c + B_{TCR}) \quad \text{--- (2)}$$

$B_{SVC} \rightarrow$ maximum of fc-TCR.

$$\alpha = 180^\circ$$

$$B_{TCR} = 0$$

$$B_{SVC \max} = \frac{B_0 B_c}{B_0 + B_c} \quad \text{--- (3)}$$

$B_{SVC} \rightarrow$ minimum $\alpha = 90^\circ$

$$B_{SVC \min} = \frac{B_0 (B_c + B_{TCR})}{B_0 + B_c + B_{TCR}} \quad \text{--- (4)}$$

$$V_2 = I_2 \cdot j \frac{1}{B_c + B_{TCR}}$$

$$I_2 = V_2 \cdot j B_{SVC}$$

$$B_{SVC} = \frac{B_0 (B_c + B_{TCR})}{B_0 + B_c + B_{TCR}}$$

$$I_2 = V_2 \cdot \frac{B_0 (B_c + B_{TCR})}{B_0 + B_c + B_{TCR}}$$

$$V_2 = V_2 \cdot \frac{B_0 (B_c + B_{TCR})}{B_0 + B_c + B_{TCR}} \cdot \frac{1}{B_c + B_{TCR}} \quad \text{--- (5)}$$

$$V_2 = V_2 \cdot \frac{B_0}{B_0 + B_c + B_{TCR}}$$


when ever to design fc-TCR the coupling
T/F of secondary Wg must be know.

~~So~~


UNIT-IV
SVC and STATCOM

①

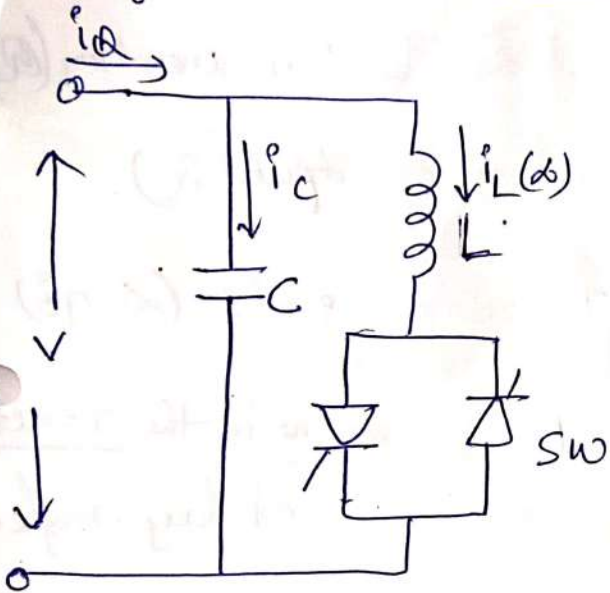Fixed Capacitor - Thyristor Controlled Reactor (FC-TCR)



(a) $I_Q = I_C + I_L(\alpha)$

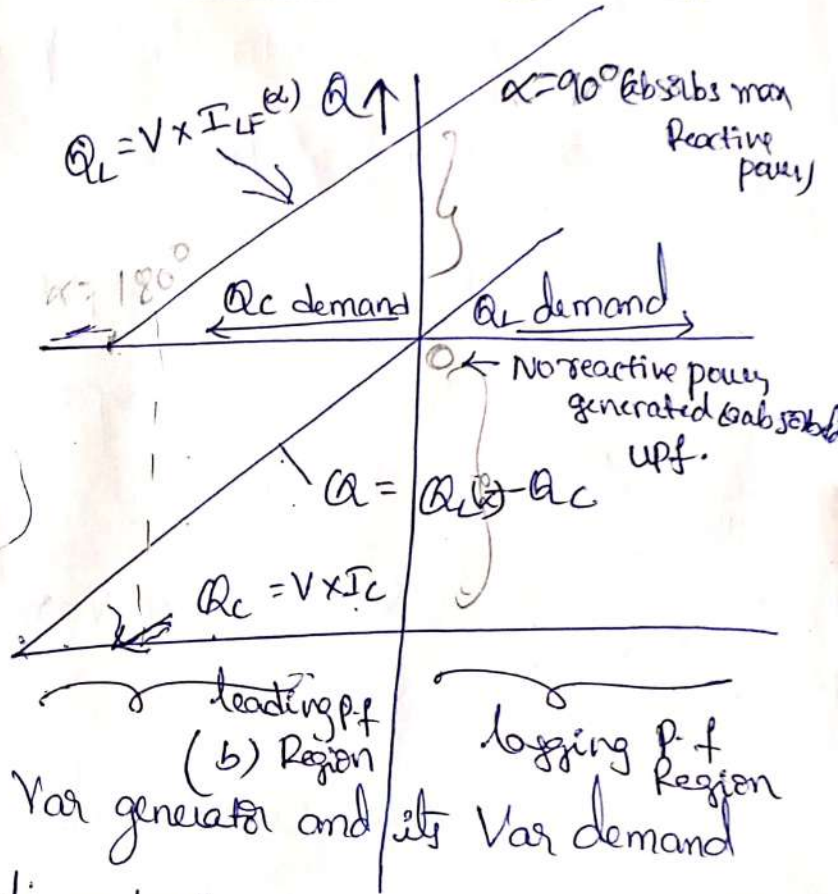

Basic FC-TCR type static Var generator and its Var demand Versus Var output characteristics.

→ Above fig shows fixed capacitor thyristor controlled reactor (FC-TCR). The current in the reactor is varied by firing angle control.

→ The capacitor value is fixed with the help of filter network to generate reactive power required, but it provides a low impedance at selected frequencies.

→ This FC-TCR consists Variable reactor (Inductor) (controlled by delay angle α) and fixed valued Capacitor.

→ Var demand vs output char shown in fig.

→ Fixed Capacitor (C_c) opposes the Variable Var generation (C_v) absorption to provide req total ϕ Var output (ϕ).

→ At max Var output TC reactor is off ($\alpha = 90^\circ$)

→ To decrease the Capacitive o/p, the Current in the reactor is increased by decreasing the delay angle α .

$C_c \downarrow$
 $I_L \uparrow$



→ At 'Zero' o/p Var, the Capacitive & Inductive Currents become equal, and Capacitive & Inductive Vars Cancel out.

$V_{arc} = V_{arL}$
 $\Rightarrow 0$ o/p

→ further decreasing the delay angle the Inductive Current becomes larger than the Capacitive Current, the resultant Var output is Inductive.

→ at zero delay angle, the thyristor-controlled reactor

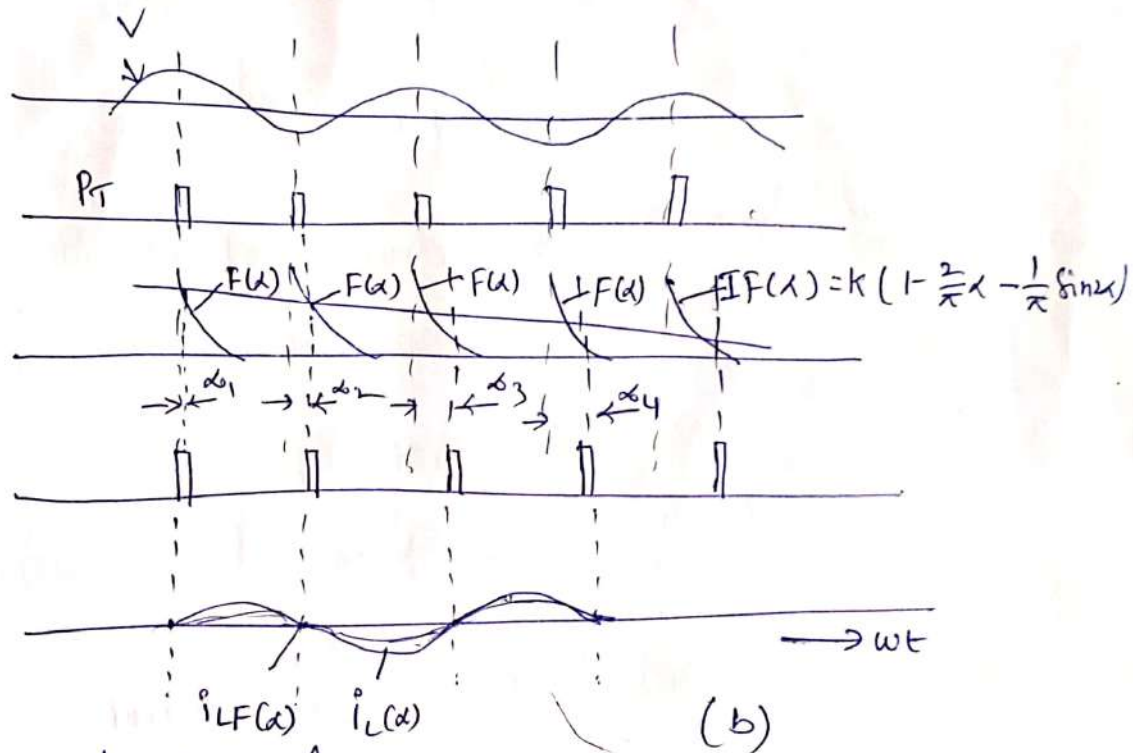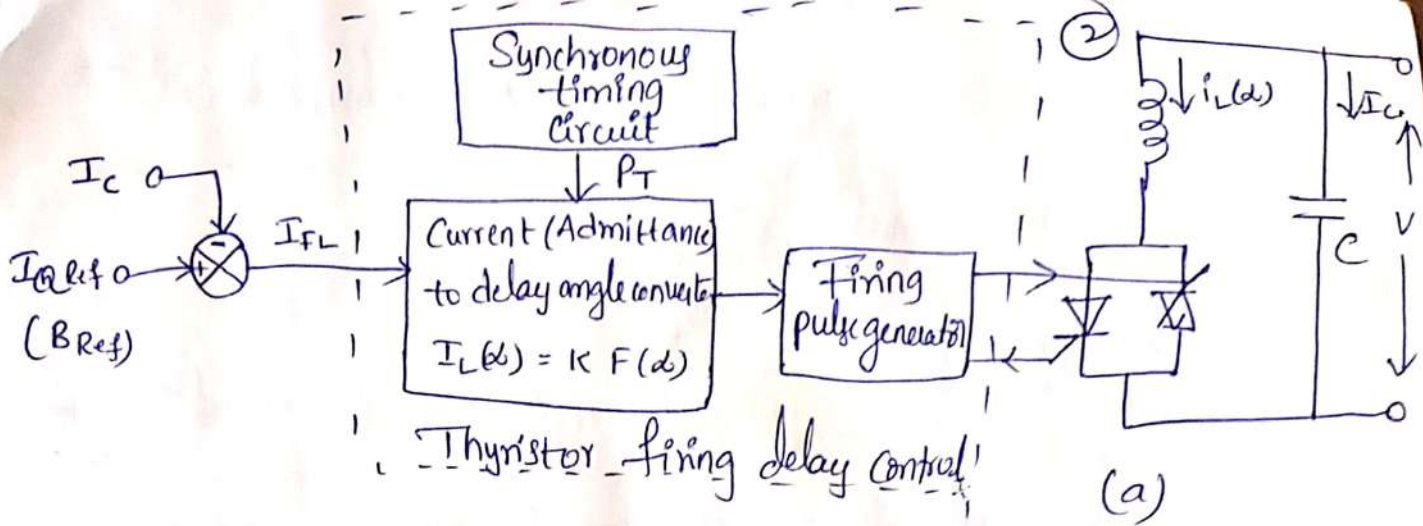conducts current over the full 180° interval, results Inductive Var o/p is equal to diff b/w the Var generated by the Capacitor & those absorbed by the fully conducting reactor.



(a) Functional control scheme for the FC-TCR type static Var generator.
 (b) waveform.

→ The Control of the thyristor-Controlled reactor in FC-TCR type Var generator need to provide four basic functions.

1) is Synchronous timing:- This function is provided by phase locked loop ckt that runs in Synchronism with the ac system voltage and generates timing pulses with voltage

→ Second function is reactive current (or admittance) to firing angle conversion.

→ 3rd function is Computation of reactive current I_L from total output current I_a .

i.e. $I_L = I_a - I_{a \text{ ref}}$. Subtracting Capacitive Current.

+ve polarity means Inductive o/p current

-ve " " Capacitive o/p current

→ 4th function is Thyristor firing pulse generation. This is done by the firing pulse generator.


which produces the necessary gate current pulse for thyristor to turn on in response to the output signal provided by the reactive current to firing angle conversion.

→ Taking a block box view point of FCR type VSC generator can be considered as a Controllable reactive admittance connected to the ac system.

Relation b/w Susceptance and I_{svc} .


$$I_{svc} = V \cdot j B_{svc}$$

Where $B_{svc} = B_c + B_{TCR}$

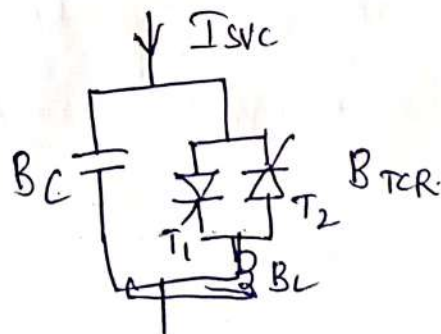

FCVC


(3)

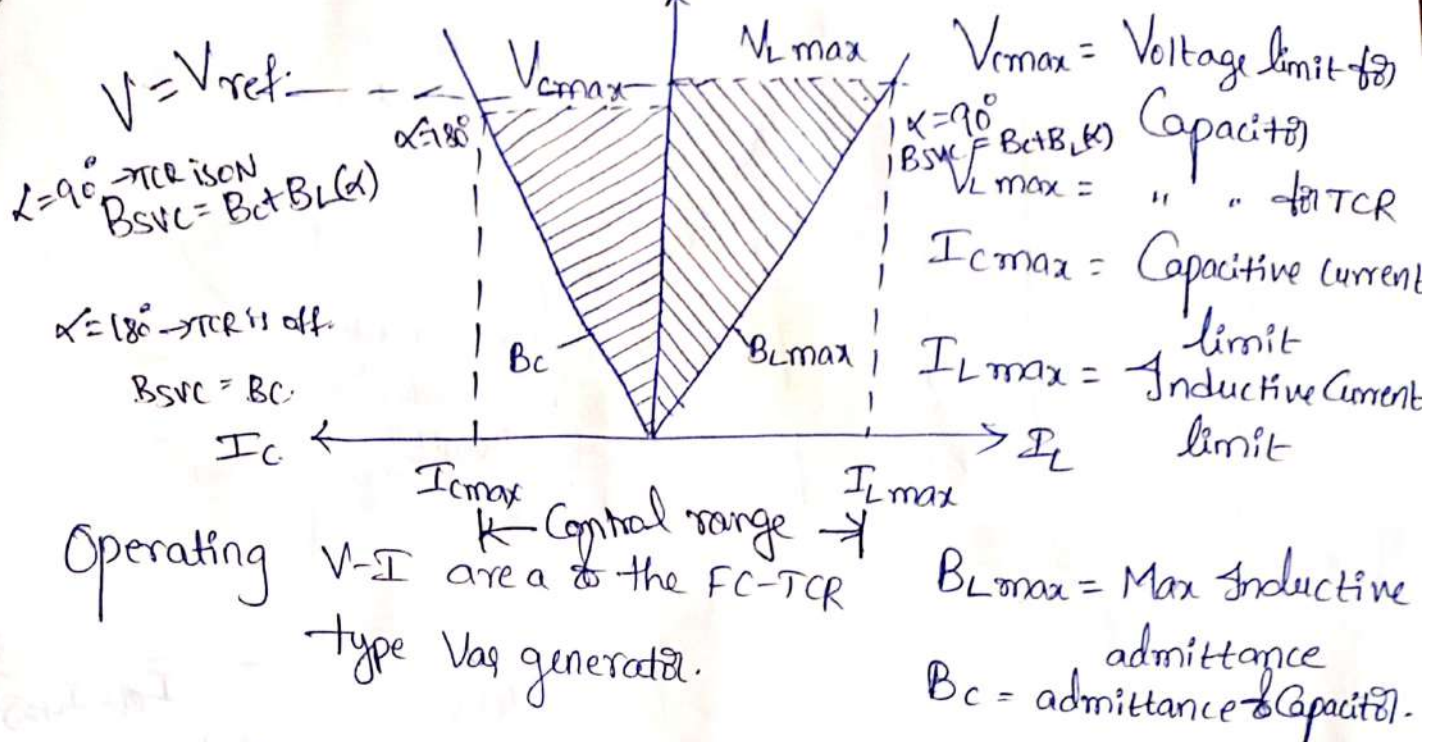


Operating V-I area of the FC-TCR type Vargenerator.

→ above V-I operating area of the FC-TCR Vargenerator is defined by maximum Capacity of Capacitive & Inductive admittance and Voltage, current ratings of Capacitor, Inductor & Thyristor.

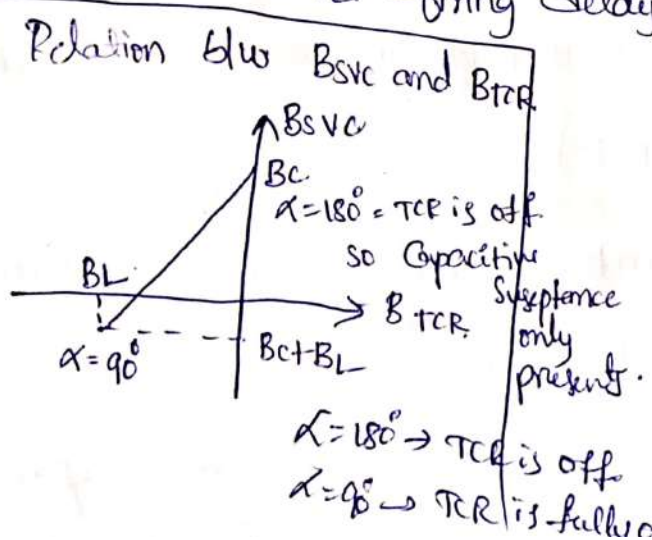→ Transfer function of FC-TCR is $G(s) = k e^{-T_d s}$
 (s) is Laplace transform operator
 k is a gain constant
 T_d firing delay angle (s)



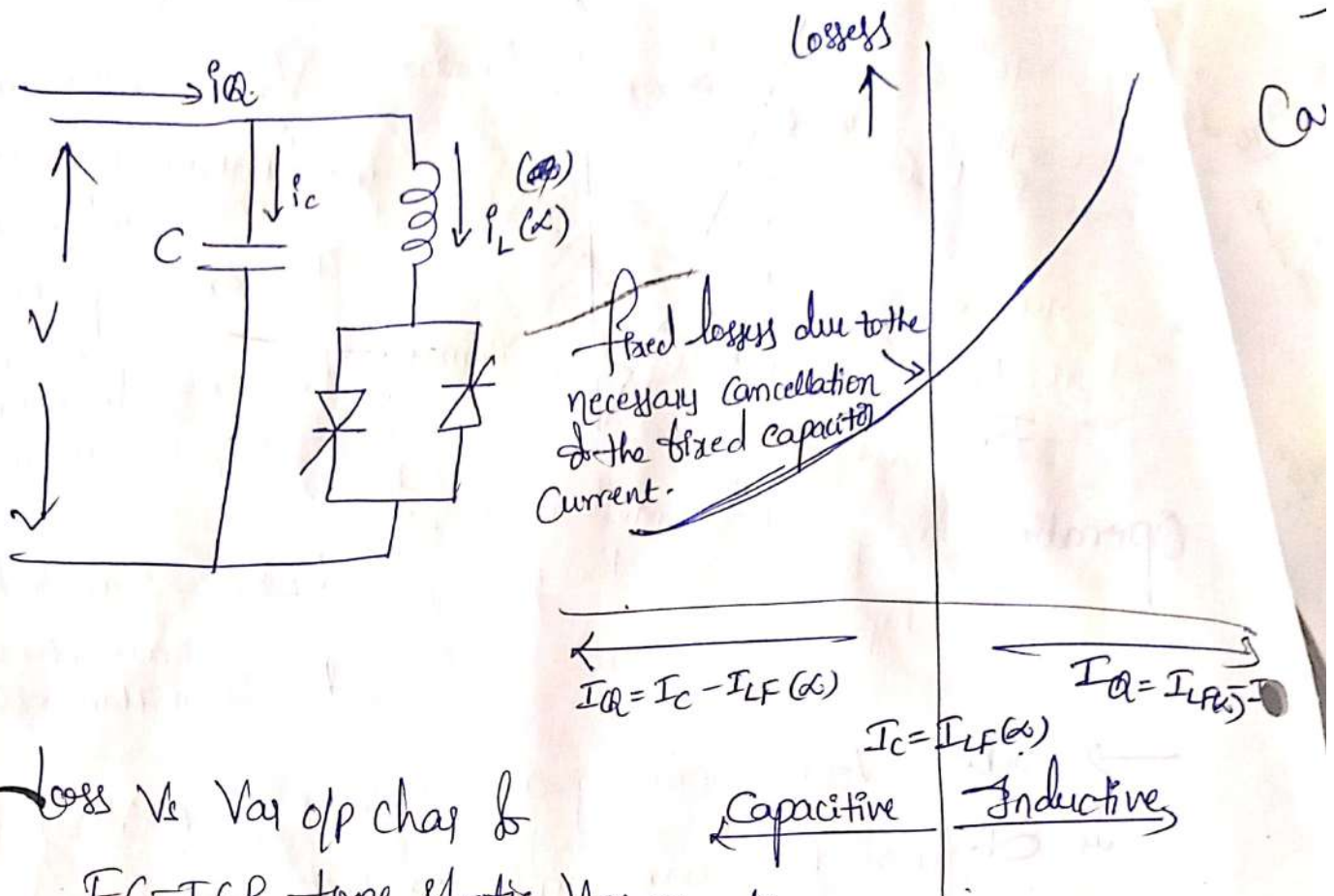

Loss vs Var o/p char for FC-TCR type static Var generator.

In FC-TCR type Var generator, there are 3 major losses occurred

- ① The Capacitor losses (small)
- ② Reactor losses (these increase with square of current)
- ③ Thyristor losses (these are almost linear with current)

→ Thus total losses increase with increasing in current


and decrease with decreasing the Capacitive Var output. Shown in fig (a).

→ Zero o/p is obtained by cancelling capacitive loss with inductive ($I_c = I_L$)

→ Their loss char Curve is, advantageous when avg Capacitive Var o/p is relatively high this type is applications req Industrial p.f Correction.

and its advantageous when avg var o/p is low,
Dynamic Compensation & Power transmission system.

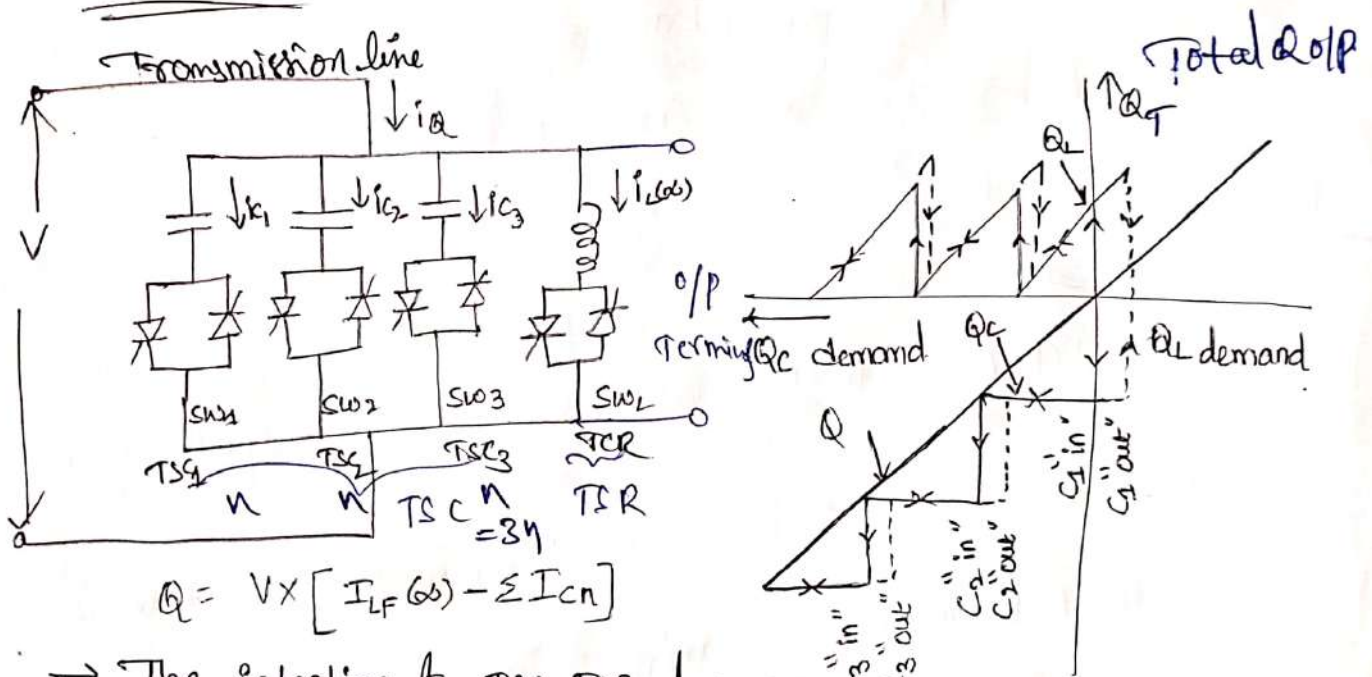Thyristor-Switched Capacitor - Thyristor-Controlled Reactor (TSC-TCR) :-



$$Q = V \times [I_{LF}(\omega) - \sum I_{cn}]$$

→ The intention of TSC-TCR design is minimizing stand by losses and increasing operating flexibility
 ↳ wastage & fuel losses

→ For a given Capacitive output range, it consists of 'n' TSC branches and one TCR. The 'n' number of branches determines operating voltage level, maximum var output, current rating of the thyristor valves, bus work and installation cost. etc.

of course, inductive range also can be expanded to any maximum rating by employing additional TCR branches.

operation:-

→ The total Capacitive output range is divided into 'n' intervals. In the first interval, the o/p of the var generator is controllable.

The zero to Q_{cmax}/n range, where Q_{cmax} is the total rating provided by all TSC branches.

In this one capacitor bank is switched in (by firing, for example, thyristor valve sws,) and simultaneously the current in the TCR is set by appropriate firing delay angle so that the sum of the var output of TSC (negative) and that of TCR (positive) equals the Capacitive output required.

→ In 2nd, 3rd, ... nth intervals, the output is controlled in the Q_{cmax}/n to $2Q_{cmax}/n$, $2Q_{cmax}/n$ to $3Q_{cmax}/n$... and $(n-1)Q_{cmax}/n$ to Q_{cmax} range by switching absorb the supply Capacitive vars.

Ex

$n=5 \quad Q_{cmax} = 10 \text{ MVAR}$

Introduce 5 branches

our req is 9MVAR.

$2 \times 5 = 10 \text{ MVAR} - \Delta \text{TCR} = 9 \text{ MVAR}$

absorb supply Capacitive var.

⑤
→ By being able to switch the Capacitor banks in and out within one cycle of the applied ac voltage, the maximum Supply Capacitive Var in the total output range can be restricted to that produced by one Capacitor bank, and thus, theoretically, the TCR should have the same Var rating as the TSC.

⇒ Var demand Versus the output characteristics of the TSC-TCR type Var generator is shown in fig (b).

The Capacitive Var output, Q_c is charged in step-like manner by the TSC, and the relatively small Inductive Var output of the TCR, Q_L , is used to

Cancel the surplus Capacitive Vars.
Ex: Explained
⇒ Hence theoretically the TCR should have the same Var rating as the TSC.
A functional Control scheme of TSC-TCR shown below

It provides 3 major functions-

→ 1) Determines the no. of TSC branches needed to be switched in to approximate the req Capacitive output current and computes the amplitude of Inductive current needed to cancel the surplus Capacitive current.

→ 2) Controls the switching of the TSC branches in a "transient-free" manner.


→ 3) Varies the current in the TCR by firing delay angle control.

Supply
ex

Req = 7 MVAR
 Capable C_{each} = C = 2 MVAR
 $\frac{7}{2} = 3.5 \rightarrow$ no. of capacitor banks first switched in at appropriate peak values
 $\frac{7}{2} = 3.5 \rightarrow$ supply vtg so once capacitor supply in in since of p dia of capacitor 8 MVAR
 $\frac{7}{2} = 3.5 \rightarrow$ req firing angle is adjusted to 1 MVAR
 $10 - 1 = 9 \text{ MVAR}$

Required Capacitor & reactor current computation

Req. like 9 MVAR

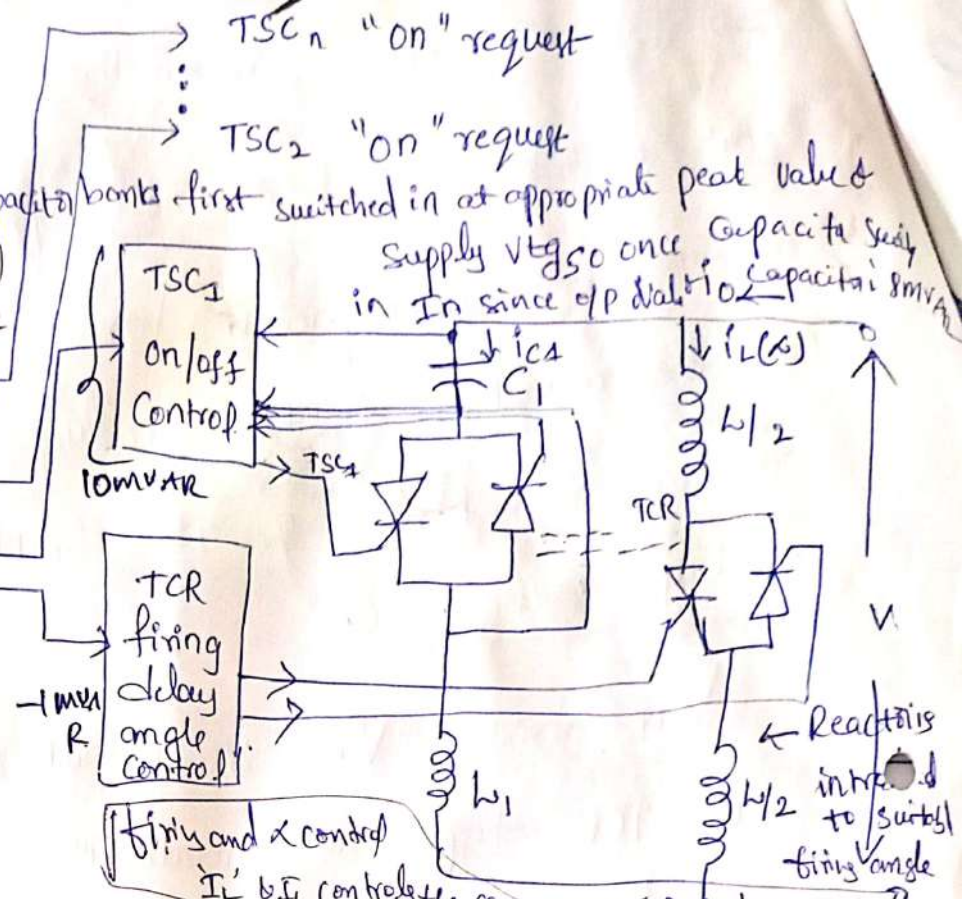

1st function → The input current I_{aRef} represents the magnitude of the requested output current. The magnitude of the current that a TSC branch would draw at the given amplitude V of the ac voltage. The result, gives the no. of capacitor banks needed.

→ The difference in magnitude b/w activated capacitor currents ΣI_{cn} and the reference current I_{aRef} giving the amplitude of I_{LF} of fundamental reactor current req.

2nd function → basic logic for 2nd function (Switching for TSC branches) is shown in fig 5.24 (e). This follows two simple rules for "transient-free" manner.


Switching Summary.

$V_o = V_c$ when it is transient free
 Supply vtg = Capacitor vtg. manner.

→ That is, To Switch the Capacitor bank. (6)

When the V_{tg} across the thyristor valve becomes zero & when thyristor valve voltage is at a minimum.

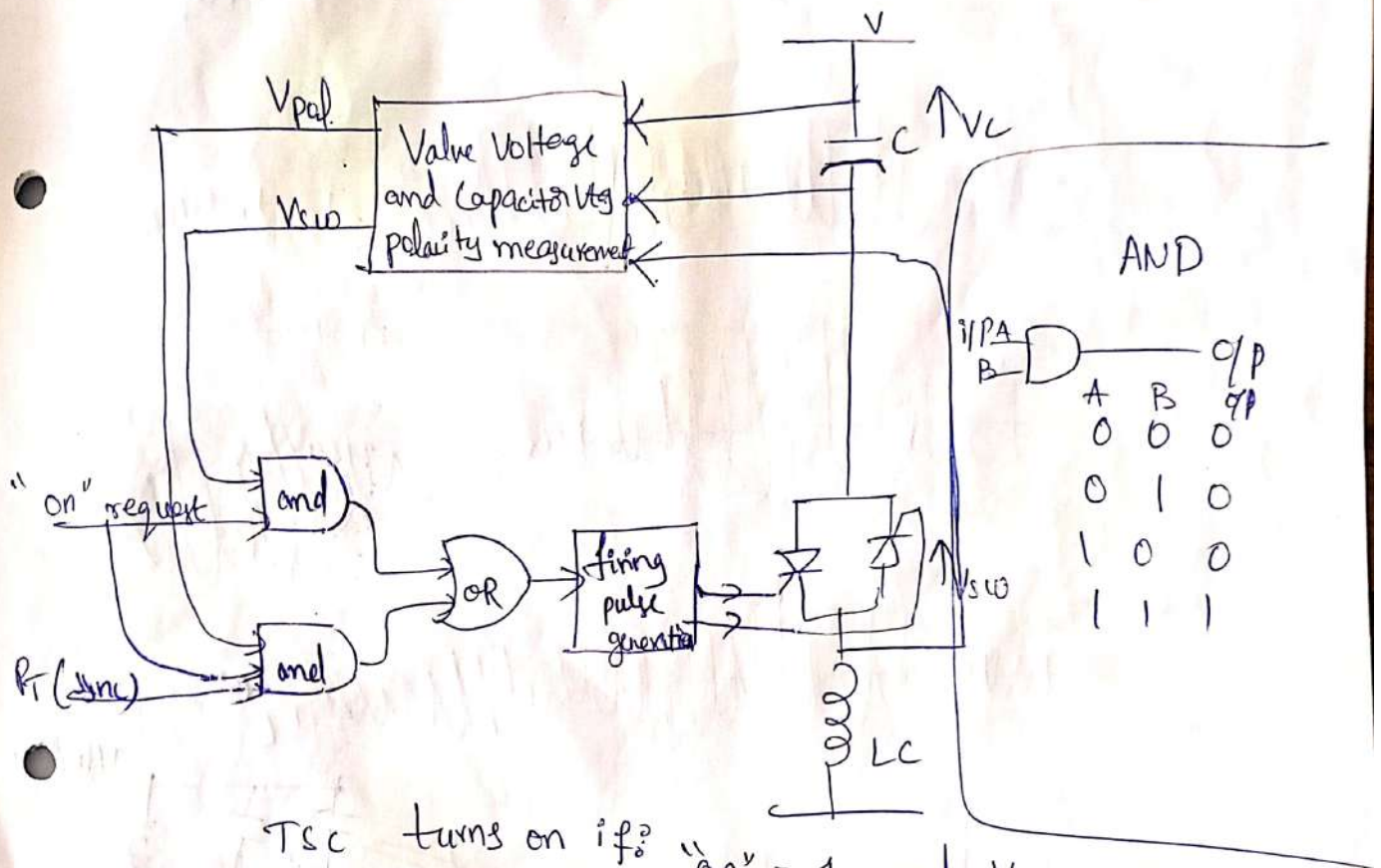→ The actual firing pulse generation for the thyristor in TSC valve is similar to that used for the TCR.



TSC turns on if:

Case (i) - $V_c < V$ ← peak V_{tg} . "On" = 1 and $V_{sw} = 1$

Case (ii) - $V_c = V$ ← instantaneous ac vltg. "On" = 1 and $P_T = 1$ and $V_{pol} = 1$

$V_{sw} = 0$ $V_{sw} = 1$ when $V_c = V$


$P_T = 1$ when $v = V$

$V_{pol} = 1$ when $\text{sign } v = \text{sign } V_c$

Case (iii) $V_c < V$






$\alpha = 0$



$V_{sw} = \text{min}$

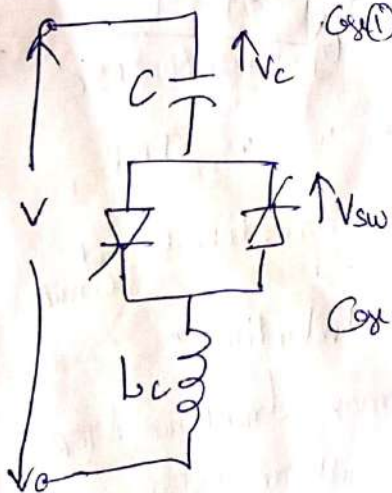

→ The third function (TCR during delay angle control) is similar to FC-TCR. The operation of TSC-TCR type VAr generator with 3 Capacitor banks is shown below.

$$I_{Q\text{ref}} = I_{Qc} = I_c + I_L$$

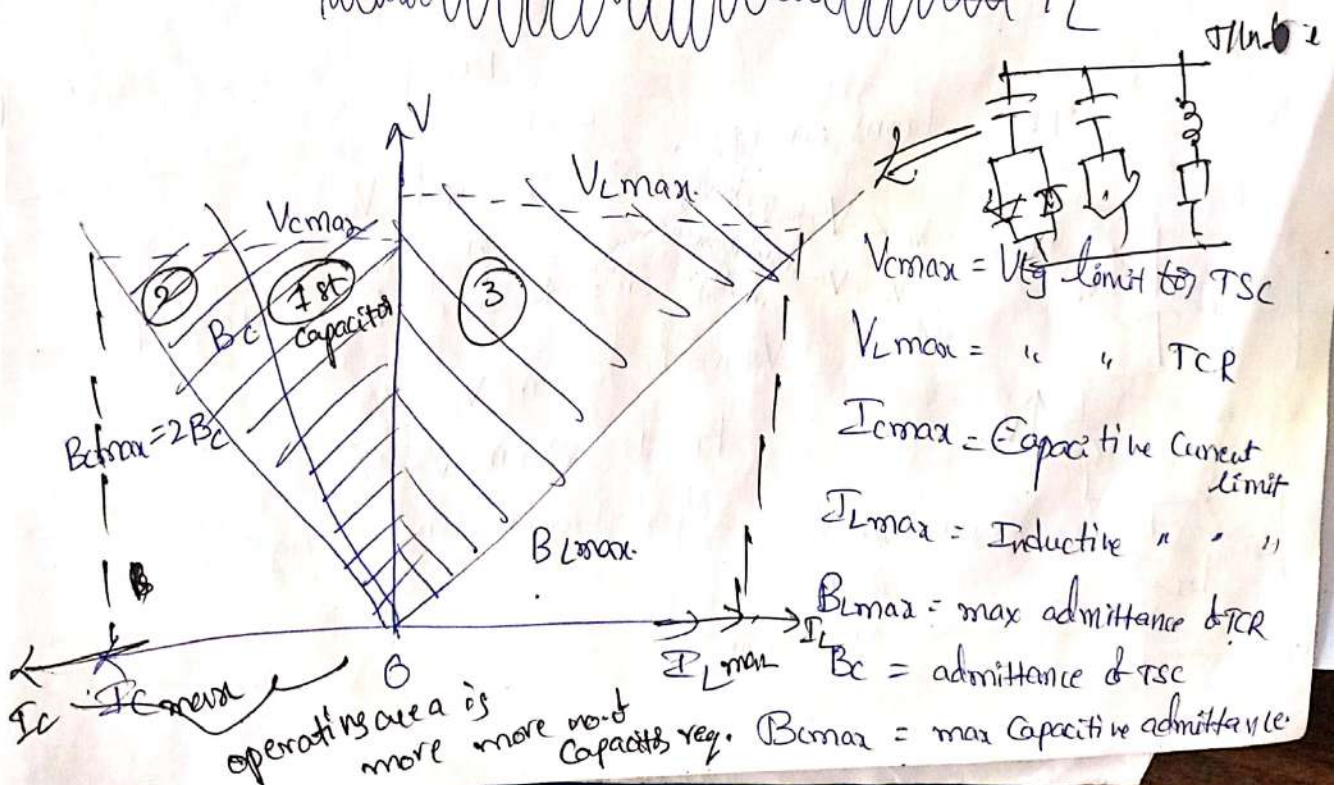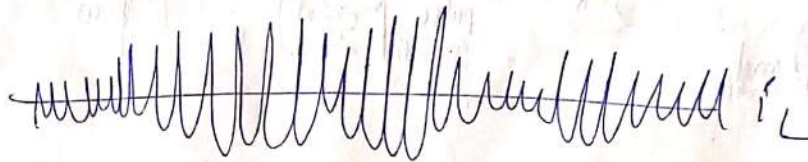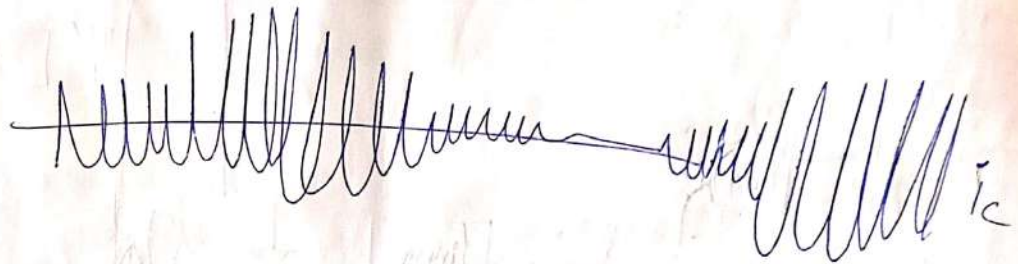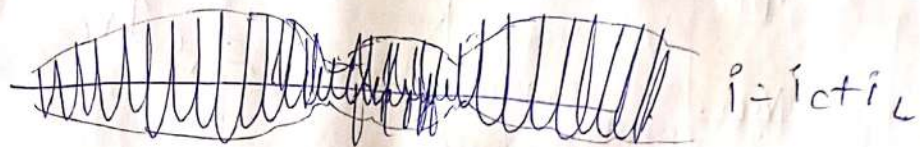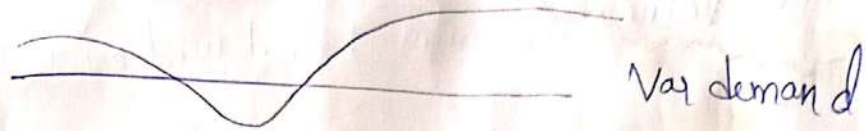

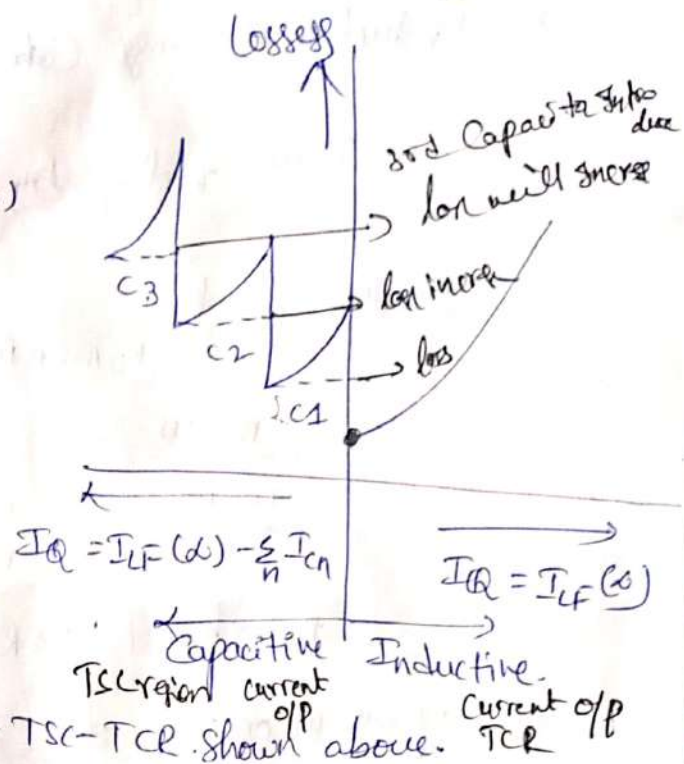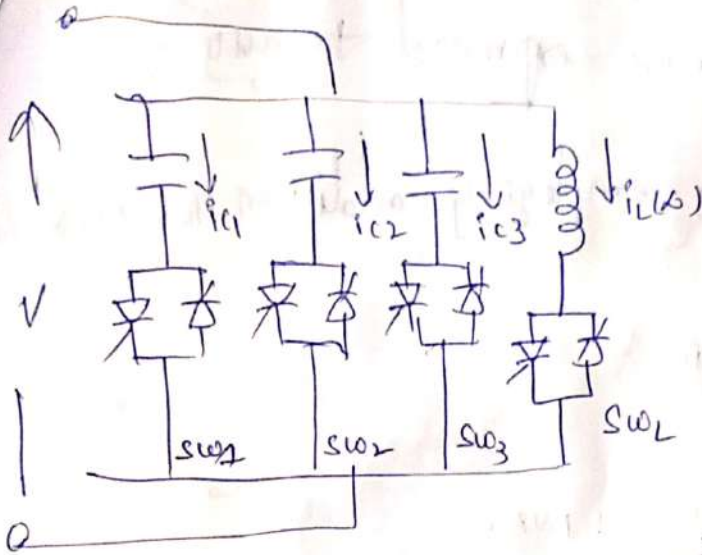

Losses vs off chg & TSC-TCR shown above.

At a slightly below zero var output, all capacitor banks are switched out, the TCR current is zero or negligibly small, and consequently, the losses are zero or almost zero.

→ as the Capacitive output is increased, an increasing no. of TSC banks are switched in with the TCR absorbing the supply Capacitive vars.

→ More over, losses & TCR vary from max to zero b/w switching of TSC banks are also success.

→ The main design intuition is to reduce the stand by losses

→ It consists of 'n' no. of TSC branches & one TCR.

→ 'n' no. of branches determine operating Vtg.

→ either connected in star or delta

$$Q = V \times [I_{LF}(\omega) - \sum I_{Cn}]$$



Get var off this scheme

↓ Inductive Cur

↓ 'n' no. of Capacitive Currents.

UNIT-5

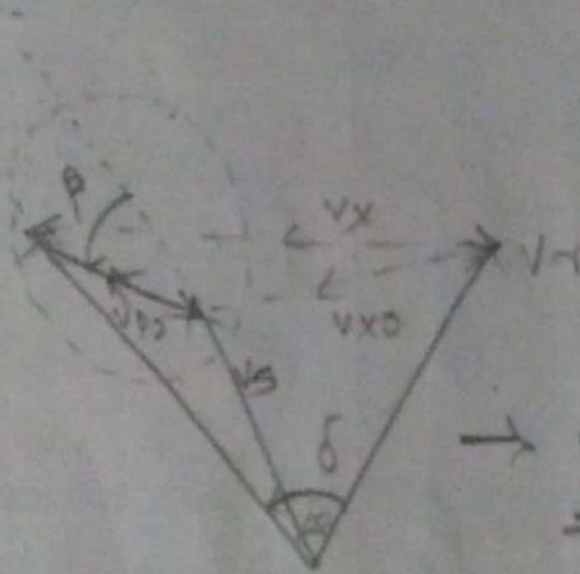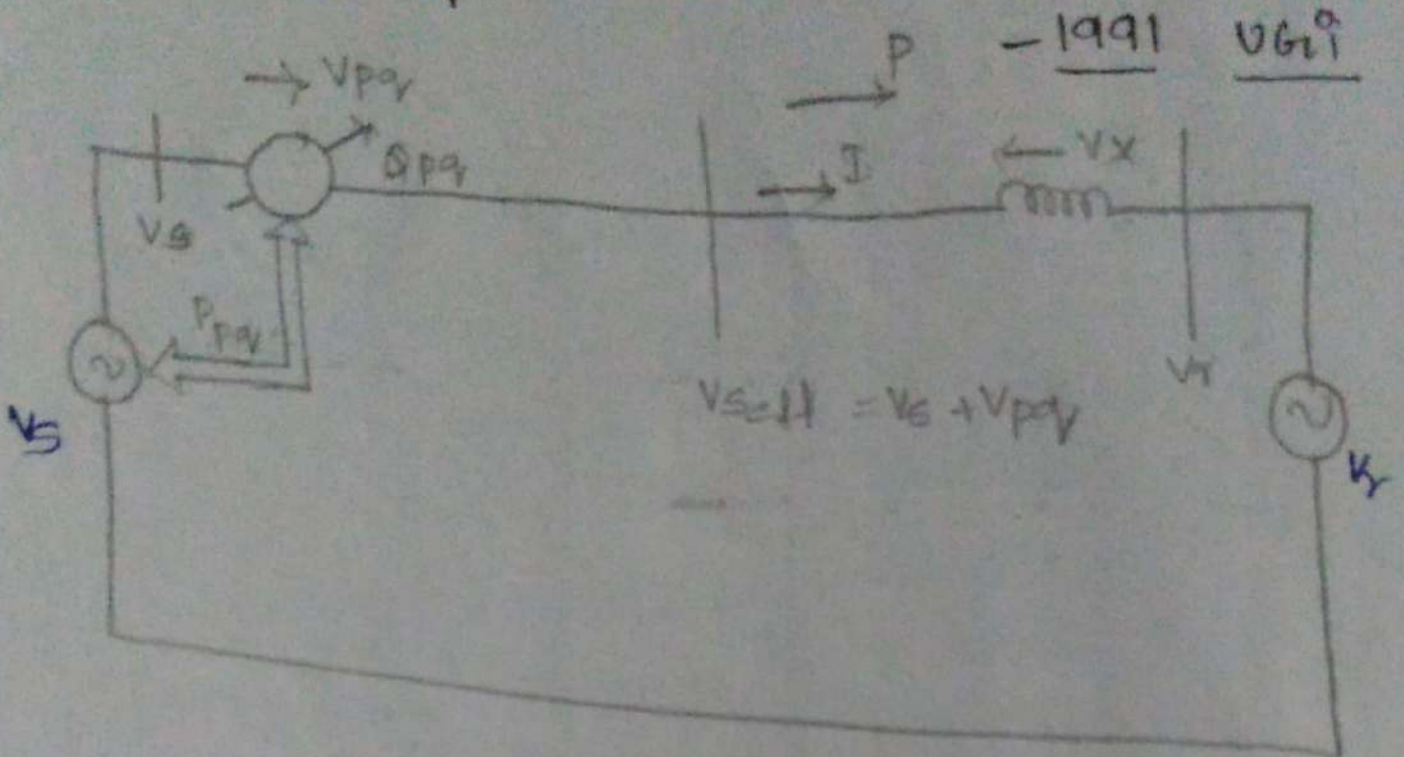→ Unified power flow controller :- (UPFC)



→ Phasor diagram

→ TO control active & Reactive power

↓
Real term

V_{PFC} → injected v_g.

Introduction of UPFC:

The UPFC concept was introduced by Gyugui in 1991

→ UPFC was introduced for the real time control & dynamic compensation of AC tln system

→ UPFC was able to control simultaneously or selectively all the parameters affecting power flowing. Tln line (i.e. vtg, impedance, phase angle)


active power & Reactive power

→ alternatively, independently control both the real & reactive power flow in the line. → 294

→ The UPFC can operate under balanced sine wave condition.

→ Basic operating principle

1) UPFC is

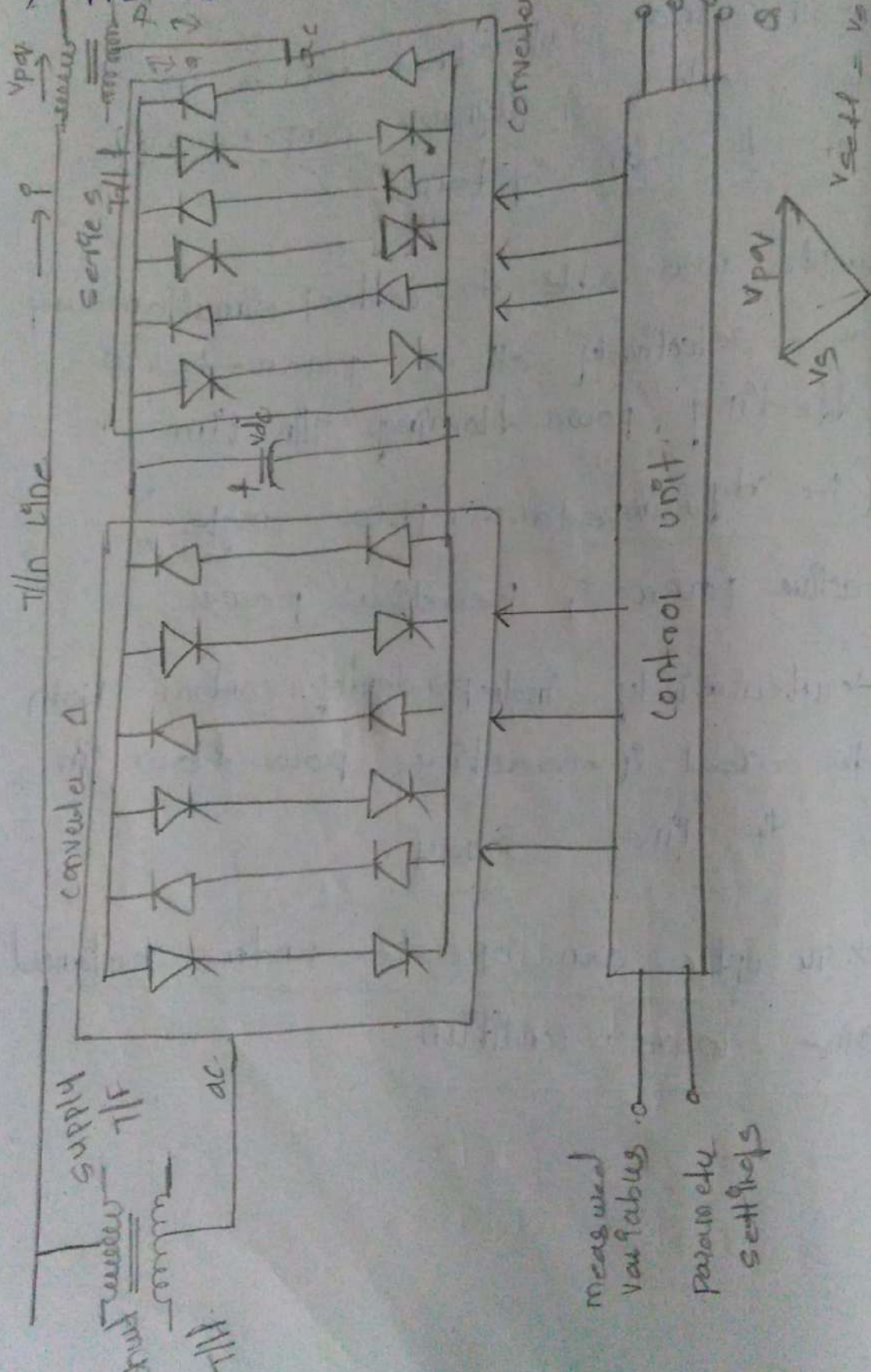

→ fig ③ shows VFTC controller by
2 Back to Back Vtg source converter

1) VFTC is a generalised synchronous
Vtg source (SVS), represented at the
fundamental freq by Vtg phasor

V_{pq}

② It controllable magnitude V_{pq}

$$V_{pq} (0 \leq V_{pq} \leq V_{pq \max})$$

and angle $\phi (0 \leq \phi \leq 2\pi)$ 0 to 360°

In series with Tln line.

2) VFTC consists of 2 voltage source
converters, converter-1 (STATCOM)

and converter-2 (SSSC) with common DC

link. V_{dc} provided by DC storage

capacitor.

→ fig shows Ideal ac to ac Power
converter in which the real power

can freely flow in either dire-

ction b/w the ac terminals of

the converter and each converter

Can independently generate or absorb
reactive power as its own ac o/p
terminals,

→ Converter 2 provides main fun of
o/pfc by injecting a v_{pq} (V_{pq}) and
with controllable magnitude " V_{pq} " & angle
" ϕ " in series with the line via

series (Injection T/T) T/T. This injection
 v_{pq} acts like synchronous AC v_{pq}
source.

→ The H/n line current flows to
this v_{pq} source. results in reactive
and the real power exchange b/w
it and ac source.

→ The Reactive power exchange and
the ac terminals i.e at the terminals
of series injection T/T is generated
internally by the converter.

→ The Real power exchange at the ac
terminals is converted in to DC power

which appears at the dc link as a positive or negative real power demand.

Basic operation of converter - 1

It is to supply ~~and~~ absorb the real power demand by converter - 2 at a common dc link, to support the real power exchange resulting from the series the VVVF injection.

→ The dc link power demand of con-2 is converted to back to ac by

con-1 and it coupled to the thn line. with a shunt connected VVVF

→ In addition to the real power 'P' of con-2, con-1 also generates or absorbs controllable reactive power by

providing shunt reactive compensation of line.


Note: There can be no reactive power flow to the VVVF dc link.

Conventional Transmission control capabilities


control capabilities are mainly 4 types

- 1) voltage regulation
- 2) line impedance compensation
- 3) phase shifting
- 4) simultaneous control of V_L , impedance and phase angle.

-ve about
+ve ahead

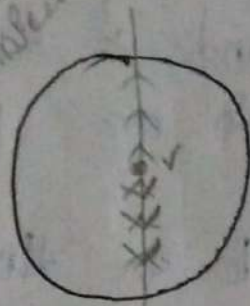


fig(1)

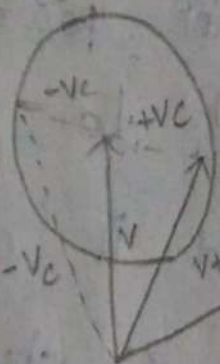

fig(2)



fig(3)

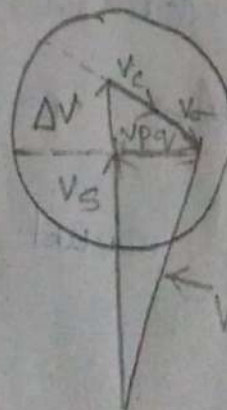

fig(4)

Fig ① shows v_{pq} regulation with continuously variable inphase/anti-phase v_{pq} injection for v_{pq} increment.

$$v_{pq} = V \pm \Delta V$$

→ This is obtain by tap changing TTT
→ Fig ② shows v_{pq} is the injected in quadrature with line current 'I'
This is similar to series capacitive and inductive line compensation attain by SSSC.

→ The injected series compensator v_{pq} can be kept constant. It is independent of line current variations

→ Fig ③ shows phase angle regulation, where $v_{pq} = V$ is injected with an angular induction. worst supply v_{pq} relation that achieves design phase shift without any change in magnitude.

→ Fig ④ shows multiple power flow control executed by simultaneously terminal v_{pq} regulation. $(\pm \Delta V)$ series capacitive

Line compensation (V_{pq}), Phase shifting (δ)

$$V_{pq} = \Delta V + V_q + V_c$$

$$P - jQ = \frac{V_s V_r}{X} \sin \delta \Rightarrow V_{pq} = 0 \text{ --- (1) without any compensator}$$

$$P - jQ = V_r \left[\frac{V_s + V_{pq} - V_r}{X} \right]^* \sin \delta \Rightarrow \text{with opt.c.}$$

$$V_{pq} \neq 0$$

$$P - jQ = V_r \left[\frac{V_s - V_r}{X} \right]^* + \frac{V_r V_{pq}}{-jX}^*$$

Independent. Real and Reactive power flow control.

V_{pq} = injected compensating V_{pq}

$$V_{pq} = 0 \text{ --- (1)}$$

There is no injected V_{pq} .

No compensator using.

$$P_o(\delta) = \frac{V_s V_r}{X} \sin \delta \text{ --- (2)}$$

$$Q_o(\delta) = \frac{-V_s V_r}{X} (1 - \cos \delta) \text{ --- (3)}$$


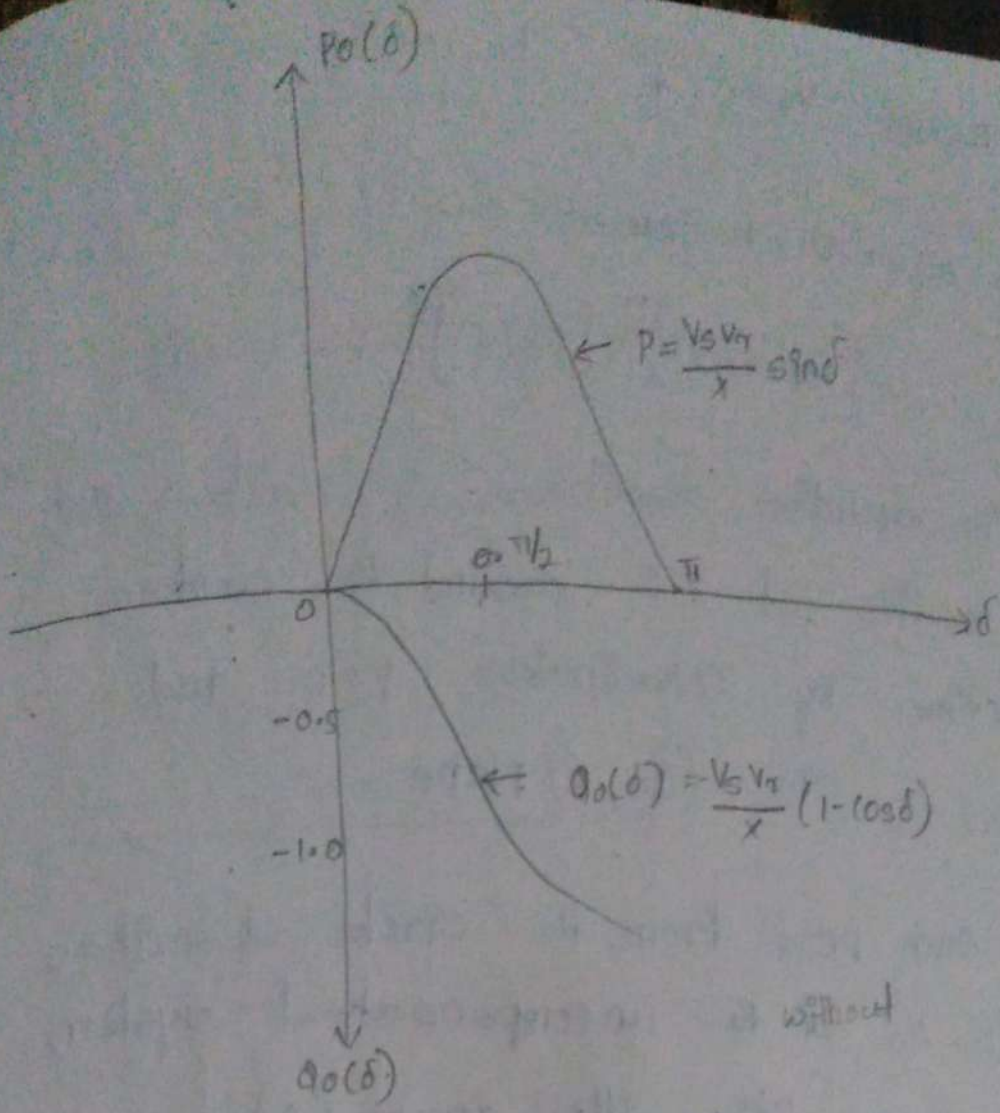


Fig (c) shows the relation b/w Real power $P_o(\delta)$, Reactive power with respect to phase angle.

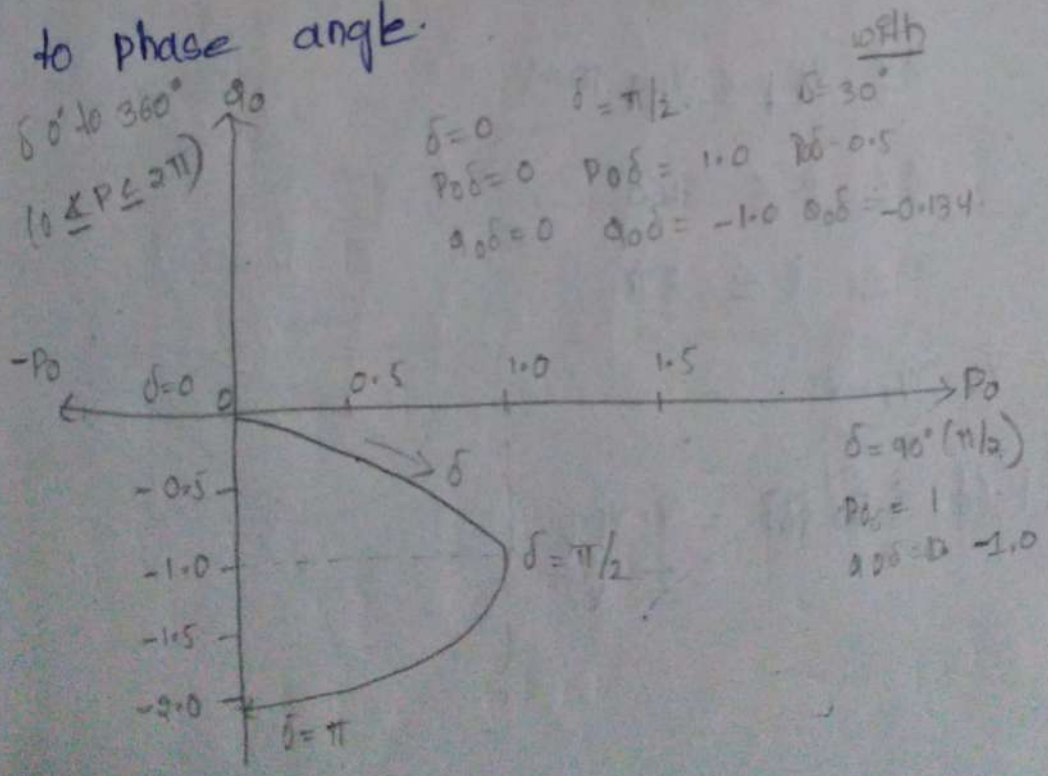

→ Assume $\frac{V_s \cdot V_r}{x} = 1$

The equation becomes.

$$[Q_0(\delta) + 1]^2 + [P_0(\delta)]^2 = 1 \quad \text{--- (4)}$$

This equation describes a circle with a radius of 1.0 around the centre defined by coordinates $P=0$ and $Q_r = -1$ in (Q_r, P) plane.

→ Each point from the circle describes P_0, Q_0 of the uncompensated system at a specific T/n angle (δ)

$$\therefore V_{pq} \neq 0$$

$$0 \leq V_{pq} \leq V_{pq} \text{ max.}$$

$$0 \leq \rho \leq 360^\circ$$

$$0 \leq \rho \leq 2\pi$$



$$V_s = V_r = V$$



$$P_0(\delta) \text{ \& \ } Q_0(\delta) = \frac{V_r V_{pq}}{x}$$

→ this is the radius of circle.

$$[P(\delta, P) - P_0(\delta)]^2 + [Q(\delta, P) - Q_0(\delta)]^2 = \left[\frac{V \cdot V_{pq \max}}{x} \right]^2$$

con

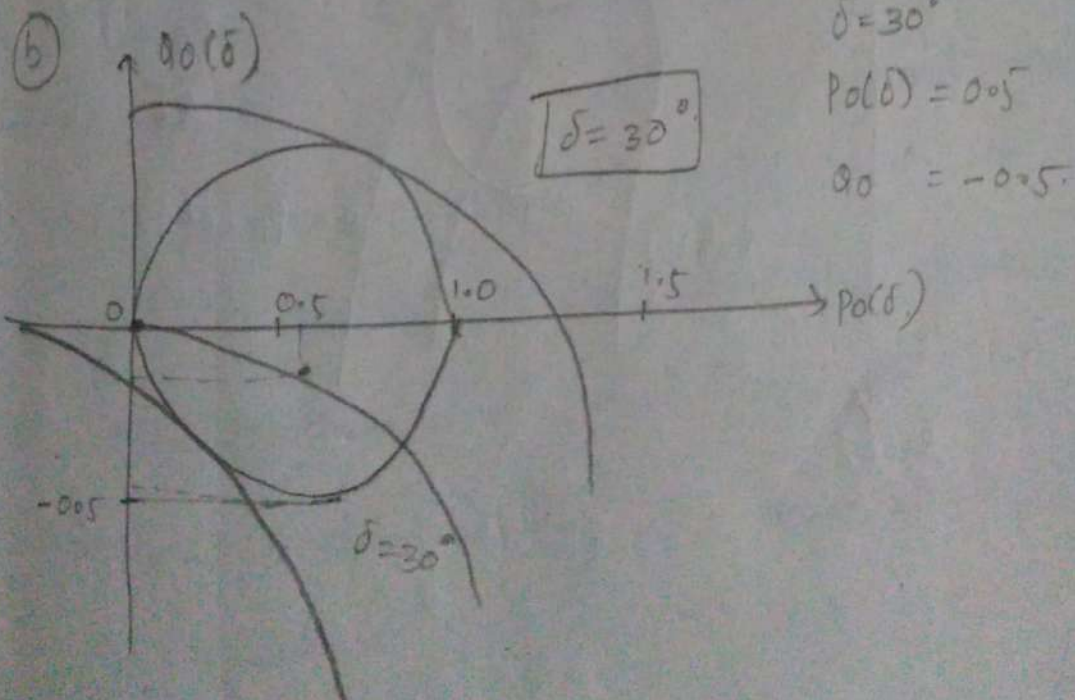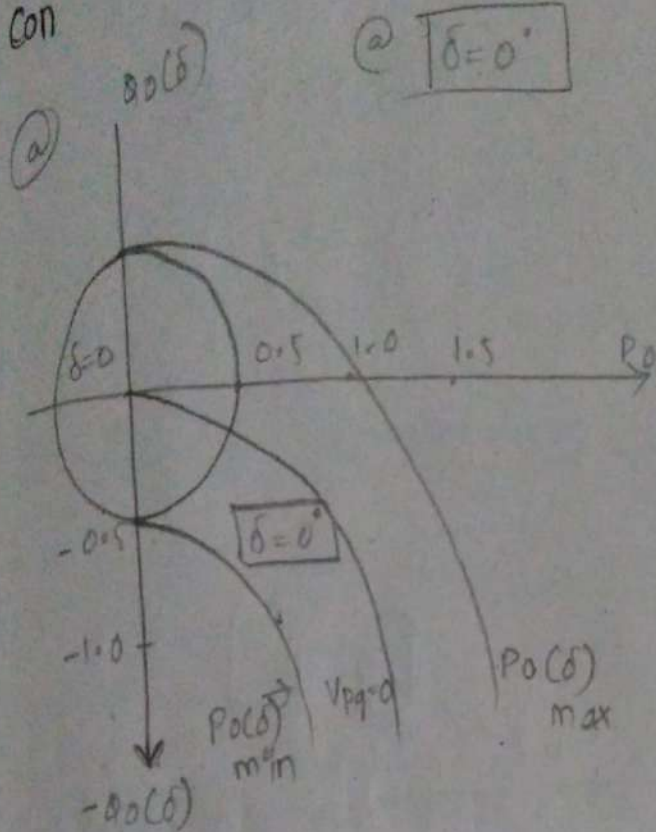

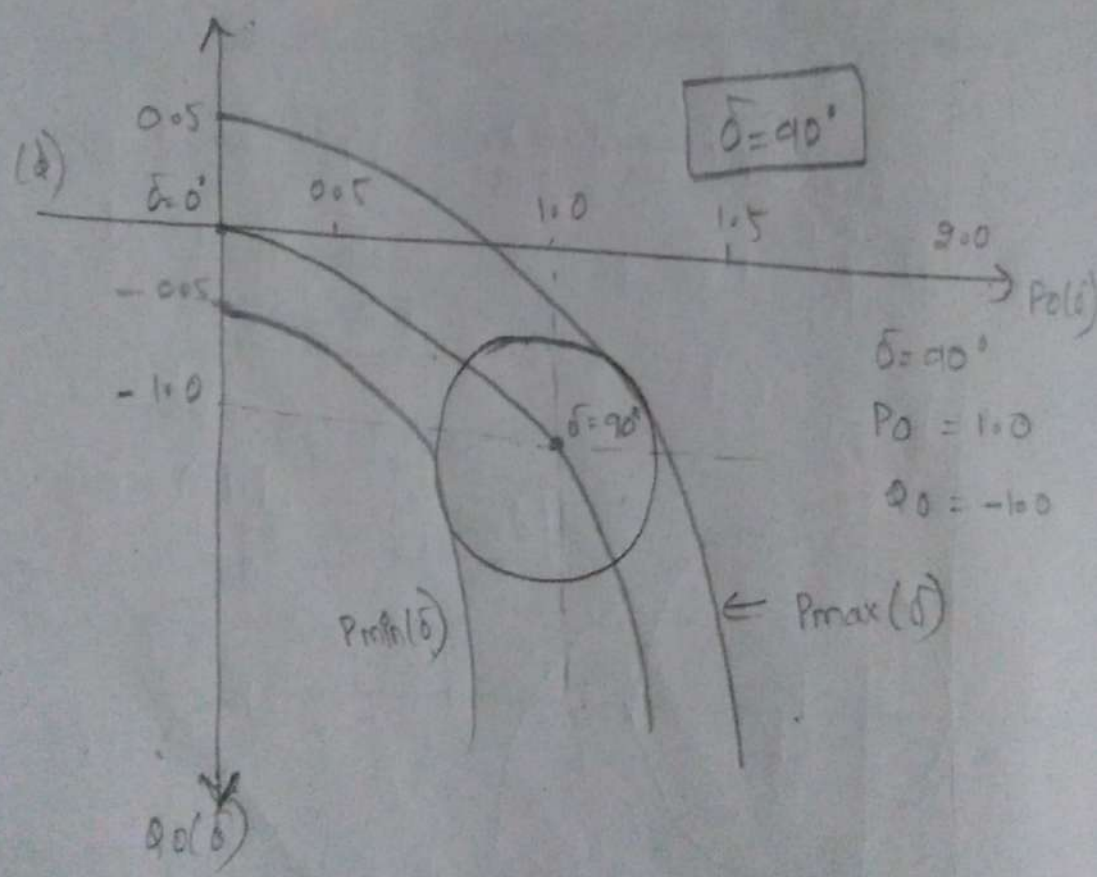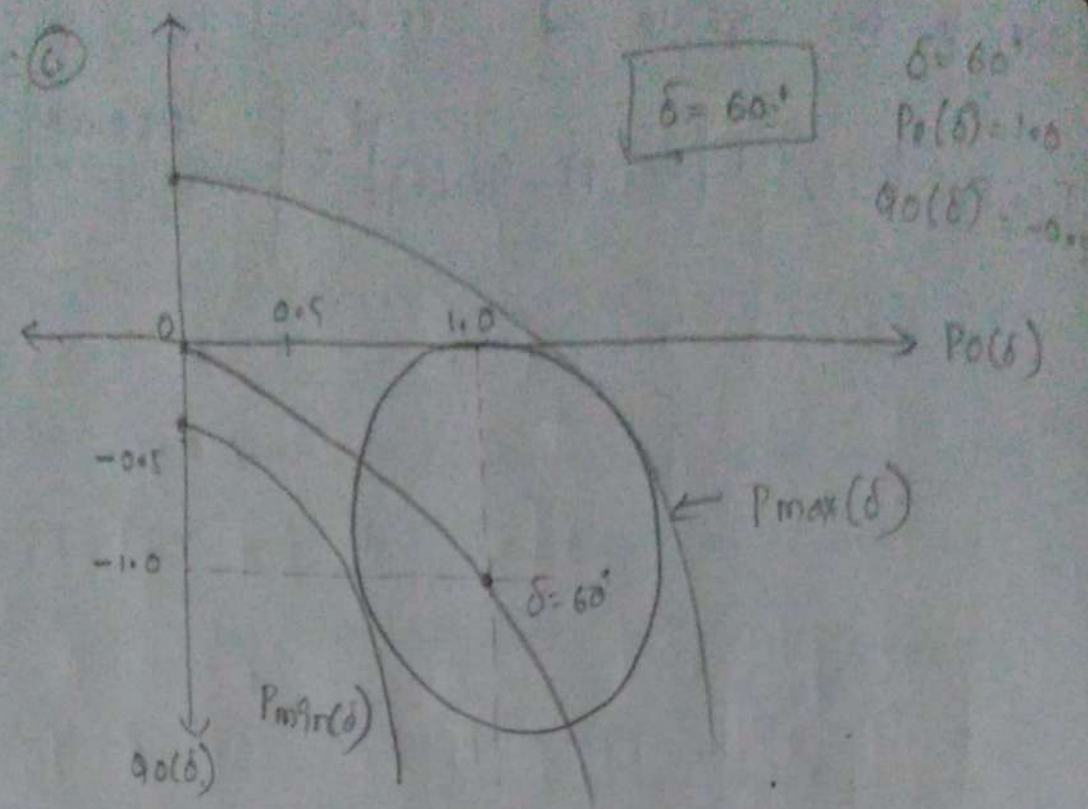

control region of the attainable power and Receiving & reactive power 'QR' with upfc control with a tln line,

$$\rightarrow \delta = 0^\circ, \text{ fig (a)}$$

$$\delta = 30^\circ, \text{ fig (b)}$$

$$\delta = 60^\circ, \text{ fig (c)}$$

$$\delta = 90^\circ, \text{ fig (d) shown above.}$$

\rightarrow In fig (a) illustrates, tln angle = 0

$$\delta = 0$$

$$V_{pq} = 0$$

$$P_0 = 0$$

$$Q_0 = 0$$

that means the system is at stand still at the origin of Q_r, P coordinates

\rightarrow This circle around origin at the

Q_r, P , gives the corresponding values of Real power and Reactive power.

\rightarrow similar control ch's for real power 'P' & reactive power 'Q' can be

absorbed at angles $0^\circ, 30^\circ, 60^\circ, 90^\circ$, shown
in fig (a), (b), (c), (d),

→ At any t/n angle ' δ ' (0 to 360°), the
transmitted power ' P ' as well as real
power ' P_r ' can be controlled
freely by the vpf.c.

→ It is a unique capability to
control the real & reactive power
flow at any t/n angle.

UNIT-II


Transmission lines and Series/shunt Reactive power Compensation.

Basics of AC Transmission: - Electrical energy is generated in TPS, HPS, NPS etc. This generated electrical energy is transmitted to the Consumers for utilisation.

Generally generating stations are usually situated away from the load centres. The network that transmits and delivers power from generating station to the consumers is called Transmission System. This energy can be transmitted in AC or DC form.

Traditionally, AC has been used for years now, but HVDC is rapidly gaining popularity.

Single line diagram

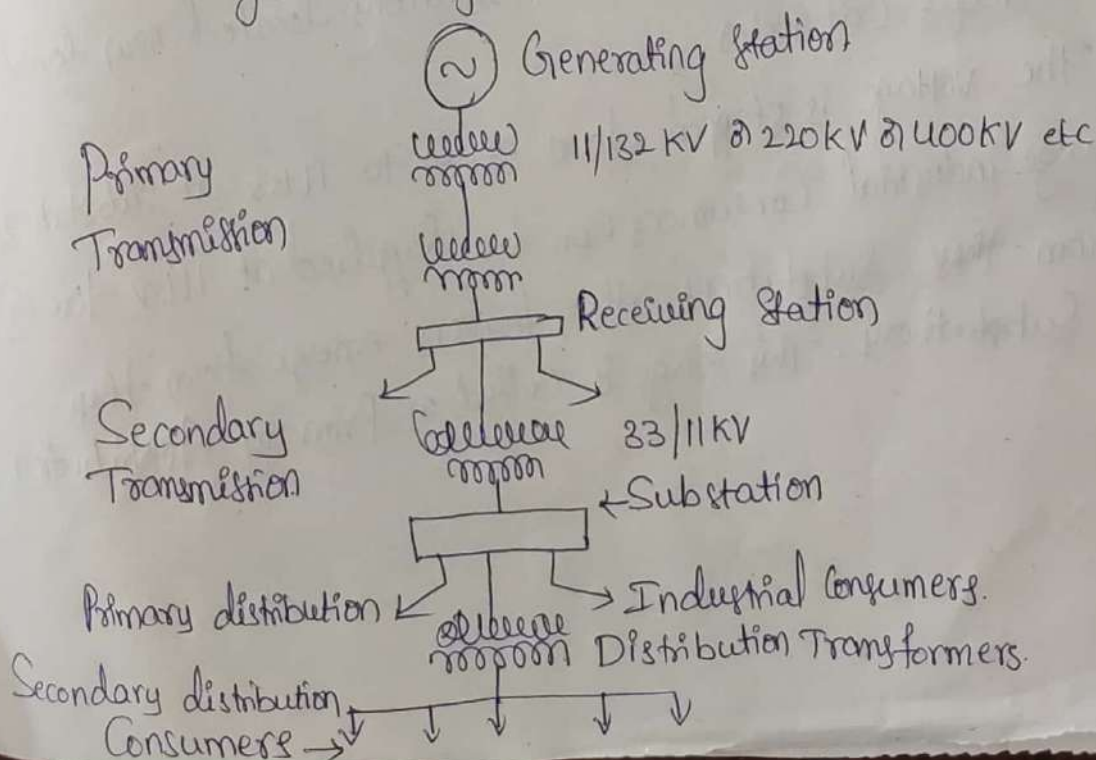

→ Electric power is commonly generated at 11 kV in generating station in India and Europe. While in some cases, generating voltage might be higher or lower. Generating machines, to be used in power stations, are available between 6 kV to 25 kV from some big mfgs.

→ This generating voltage is then stepped up to 132 kV, 220 kV, 400 kV or 765 kV etc. Stepping up the voltage level depends upon the distance at which power is to be transmitted.

→ Longer the distance, higher will be the voltage level. Stepping up the voltage is to reduce the I^2R losses in T/L lines. This stage is called primary transmission.

→ The voltage is then stepped down at receiving station to 33 kV or 66 kV. Secondary transmission lines emerge from this receiving station to connect substations located near load centres (cities etc).

→ The voltage is stepped down again to 11 kV at substations. Large industrial consumers can be supplied at 11 kV directly from these substations. Also, feeders emerge from these substations. This stage is called as Primary Distribution.



→ Feeders are either overhead lines or under ground cables which carry power close to the load points up to a couple of kilometers. finally the voltage is stepped down to 415 volts by a pole mounted distribution transformer

Main Elements of a T/M lines:

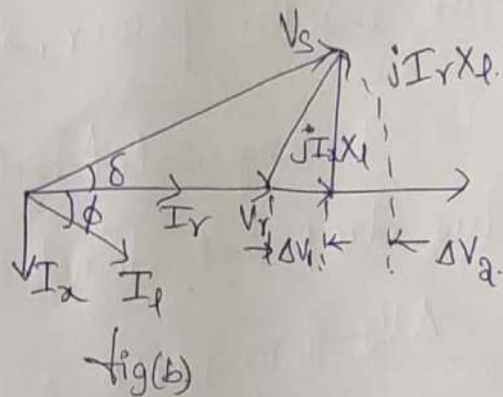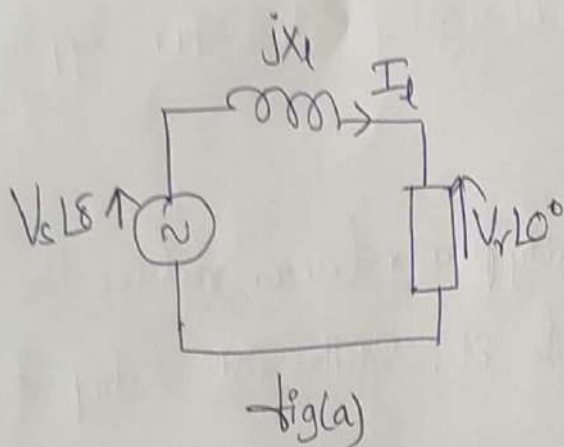- 1) Conductors:- ACSR, 3- ϕ wire, 3- ϕ wire
- 2) T/P's:- Step-up & Step-down
- 3) Line insulators:- To give mech support for the line conductors
- 4) Support towers:- To support line conductors.
- 5) Prot devices:- to protect the T/M sys. and to ensure reliable operations. They include ground wires, LA's CB's relays etc.
- 6) Vtg Regulators:- to keep the Vtg within permissible limits at the receiving end.

Analysis of uncompensated AC transmission lines:-

Introduction:- For simplicity assume the load is inductive.



→ From the above fig, It is clear that between the sending and receiving end voltages and magnitude variation as well as a phase difference is created and the most significant part of the voltage drop in the line reactance is due to the reactive component of the load current and to keep the voltages in the network nearly at the rated value.

→ There are two compensation methods are.

1. Load Compensation
2. System Compensation.

Load Compensation:-

→ It is possible to compensate for the reactive current of the load by adding a parallel capacitive load so that $I_c = I_x$ and the effective power factor to become unity.

→ 2). absence of I_x eliminates the voltage drop ΔV_1 , bringing V_r closer in magnitude to V_s , this condition is called load compensation and actually by changing extra for supplying the reactive power, x_p

→ 3) loads compensated to the unity power factor reduce the line drop but do not eliminate it. Still exist a drop of ΔV_2 from $jI_x X_L$.

System Compensation:-

→ To regulate the receiving end voltage at the rated value a power utility may install a reactive power compensator as shown in fig. and this compensator draws a reactive current to overcome both components of the voltage drop ΔV_1 and ΔV_2 as a consequence of the load current I_L through the line reactance X_L .

→ To compensate for ΔV_2 (drop in the line) an additional capacitive current ΔI_c over and above I_c that compensates for I_x is drawn by the compensator.

→ When $\Delta I_c X_L = \Delta V_2$ the receiving end voltage V_r equals the sending end voltage V_s . This method is employed by power utilities to ensure the quality of supply to the consumers.

Load Compensation in power Systems:-

- Load Compensation is the management of reactive power to improve power quality i.e. Voltage and P.f profile.
- Here the reactive power flow is controlled by installing Shunt Compensating Devices (Capacitors / reactor) at the load end bringing about proper balance between generated and consumed reactive power.
- This is most effective in improving the power transfer capability of the system and its voltage stability. It is desirable both economically and technically to operate the system near unity power factor.

Lossless Distributed parameter lines:-

- Most power transmission lines are characterized by distributed parameters. Series Resistance, Series Inductance, Shunt Conductance and Shunt Capacitance all are distributed in per unit length. Depends upon Conductor size, spacing, and clearance above the ground, frequency and temperature of operation.
- In addition these parameters depends on the bundling arrangement of the line conductors and the spacing b/w parallel lines.

UNIT-III

static shunt compensators SVC & STATCOM.

objectives of shunt compensation:-

→ The main function of reactive shunt compensator is to improve the steady-state transmittable power and voltage stability along the line.

→ The purpose of reactive compensation is to change natural electrical characteristics of the transmission line and improve the line performance to meet the load demand.

→ shunt compensators or fixed or mechanically switched reactors are used for minimise line over voltage under light load conditions, capacitor controllers is used to minimise voltage ~~under~~ levels under heavy load conditions.


→ The main objective of shunt compensation is a t/n on system is to increase the transmittable power. This may improve

steady-state transmission characteristics as well as stability of the system.



→ var compensation is used for voltage regulation at the mid point to the line and at the end of the line to prevent Vtg instability, dynamic voltage control to improve transient stability and damp power oscillations.

End of line voltage support to prevent voltage


instability :-

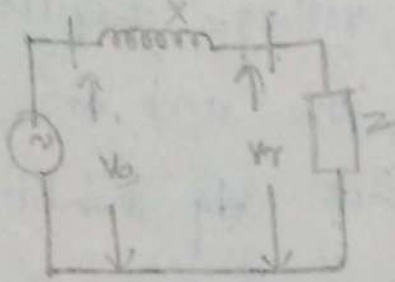

fig(a) without using any compensator

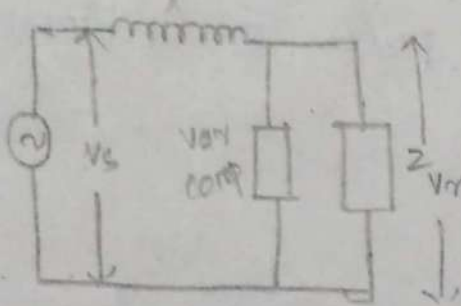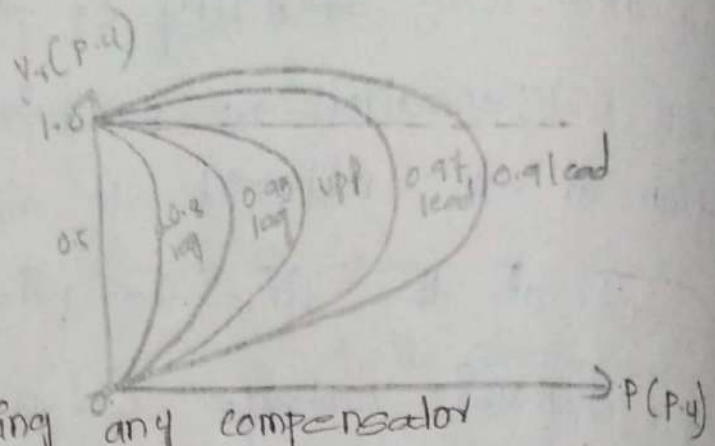

fig(b) with using compensator.

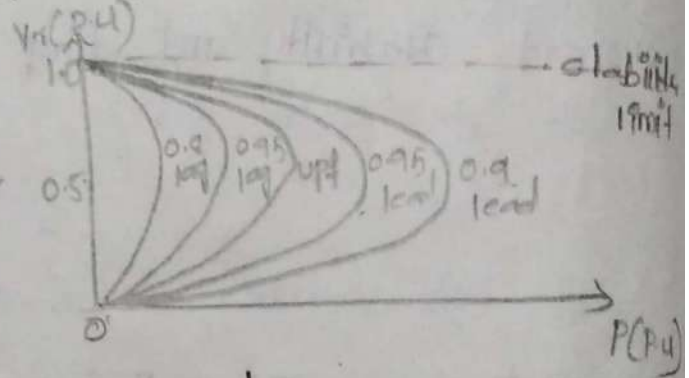

fig(i) shows without using any compensator, the

fig(i) shows sim

with line reactance " X " and load impedance " Z "

The plot is drawn b/w terminal vlg and power at various load p.f ranging from 0.8 lag to 0.9 lead.

→ The nodes point at each plot given for a specific p.f represents vlg & instability.

→ WKT vlg stability limit decreases with inductive load and ↑ with capacitive load

fig (b) shows that using shunt reactive compensator of radial line is to be connected \parallel to the load



→ shunt reactive compensation can effectively increase the V_L stability limit by supplying reactive load. & resulting terminal V_L .

$V_s - V_r = 0$ shown in fig b.

→ Reactive shunt compensation is used in practice to regulate the voltage at a given bus against load variation.

→ Improvement of transient stability:

(a)

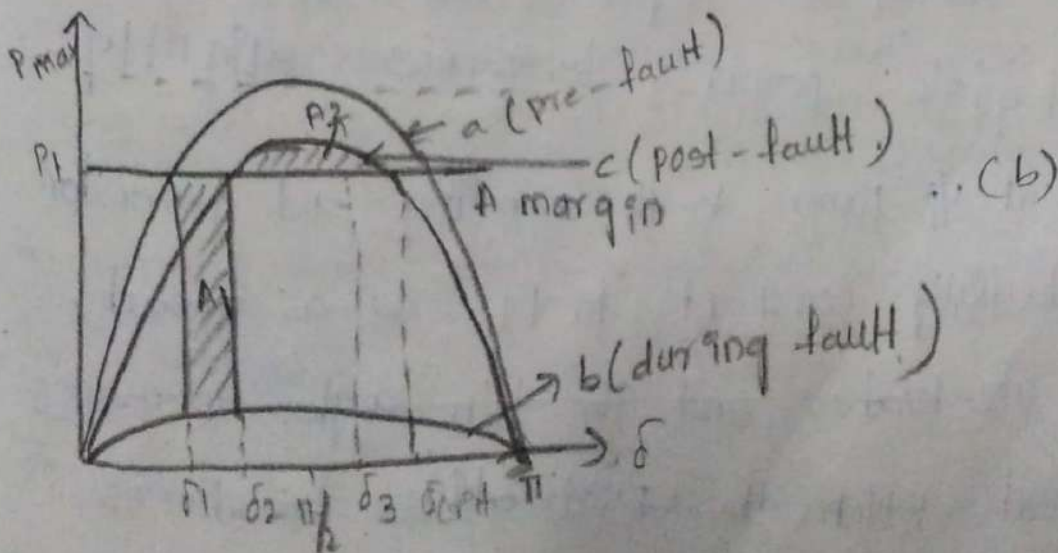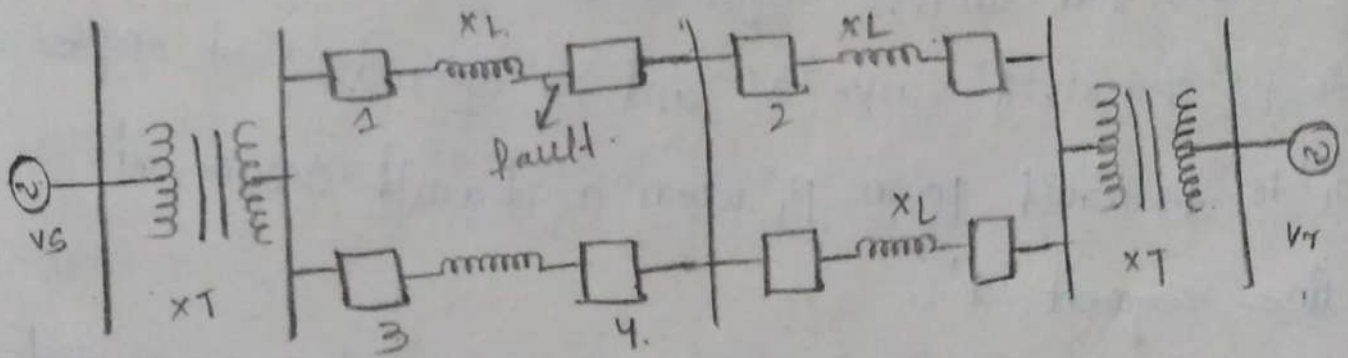


→ Illustration of the equal area criteria for transient stability of a two m/c, two-line power system

→ shunt compensation will be able to change the power flow in the system during and following disturbances is as to increase the transient stability limit and provide effective power oscillation damping


The potential effectiveness of shunt on transient stability improvement can be conveniently evaluated by the "equal area criteria".

→ Assume that complete system is characterised by the "P" versus δ curve "a" and is operating at angle δ_1 to transmit power P_1 when a fault occurs at line segment "1".

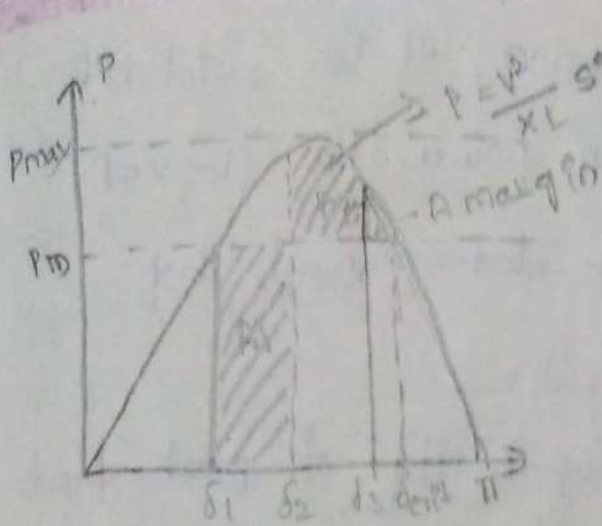→ During the fault the system is characterised by the "p" electric power decreases slightly while mechanical \dot{p} power to the sending end generator remains substantially constant to P_1 . as a result, the generator accelerates and the δ angle increases from δ_1 to δ_2 at which the protective breakers disconnect the faulted line segment "1" and the sending end generator 'absorbs' accelerating



(c)

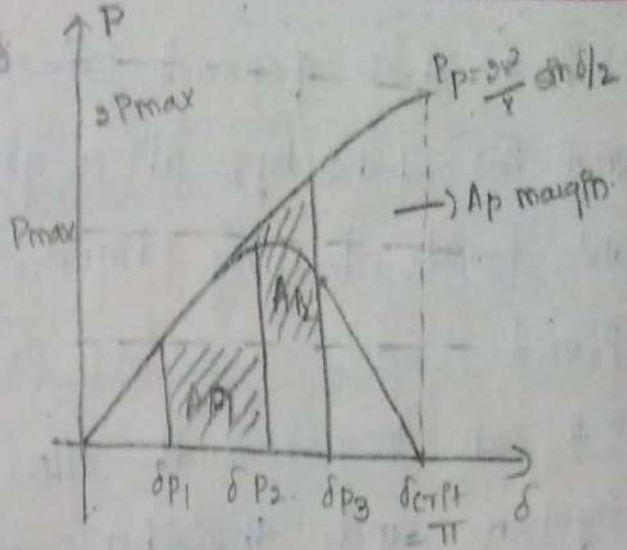

(d)

energy represented by area A_1

→ After fault clearing without line segment "1" the degraded system is characterized by P vs δ curve "c". At one angle δ_2 on curve "c" the transmitted power exceeds the mechanical $\dot{V}P$ power P_1 and the sending end generator starts to decelerate forever angle δ further increase due to the kinetic energy stored in the m/c.

→ The max angle reached at $\delta_3 = \delta_{critical}$, beyond which the decelerating energy would not balance the accelerating energy and synchronism b/w the sending end and receiving end could not be restored.

The area "A margin" between δ_3 & $\delta_{critical}$ represent the transient stability margin of the system.

⇒ From above general discussion, it is evident that the stability, at a given power t/n level and fault clearing time is determined by P vs d.

→ It can increase the t/n capability of post-fault system and thereby enhance transient stability.


→ Comparison of fig "c" & "d" shows increase in the transient stability to the ideal mid point compensation with not restricted var q/p can provide by effective segmentation of the t/n line. If uncompensated sys has transient stability margin, shunt comp sys has increase the transmittable without decreasing this margin.

→ 23/4/22. Methods of Controller VAR Generation.

In this 2 types of controllers is there.

i) static VAR compensator.

ii) static VAR generators

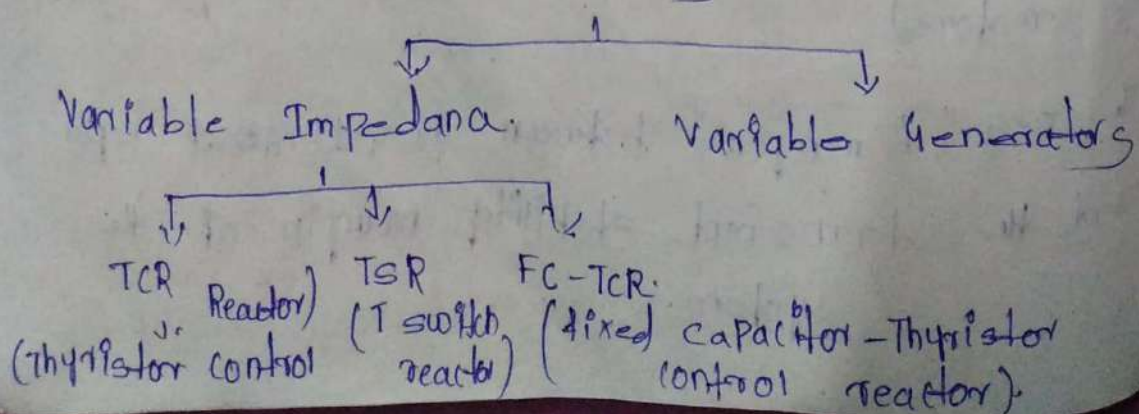

i) SVG :-

whose o/p is varied so, has to maintain/control the specific parameters of the electrical power system.

→ It is a sufficiently functioning device it will draw a Reactive current from an Alternating power source.


→ The control I/P of VAR Gen's can be arbitrary (within in the operating range). Reactive current Impedance/ power to the

Reference the SVG delivers at it's o/p

→ The SVG is used as power amplifier it faithfully produces the Required signal at the desired power levels.

Variable Impedance type.

Static VAR Generator :-

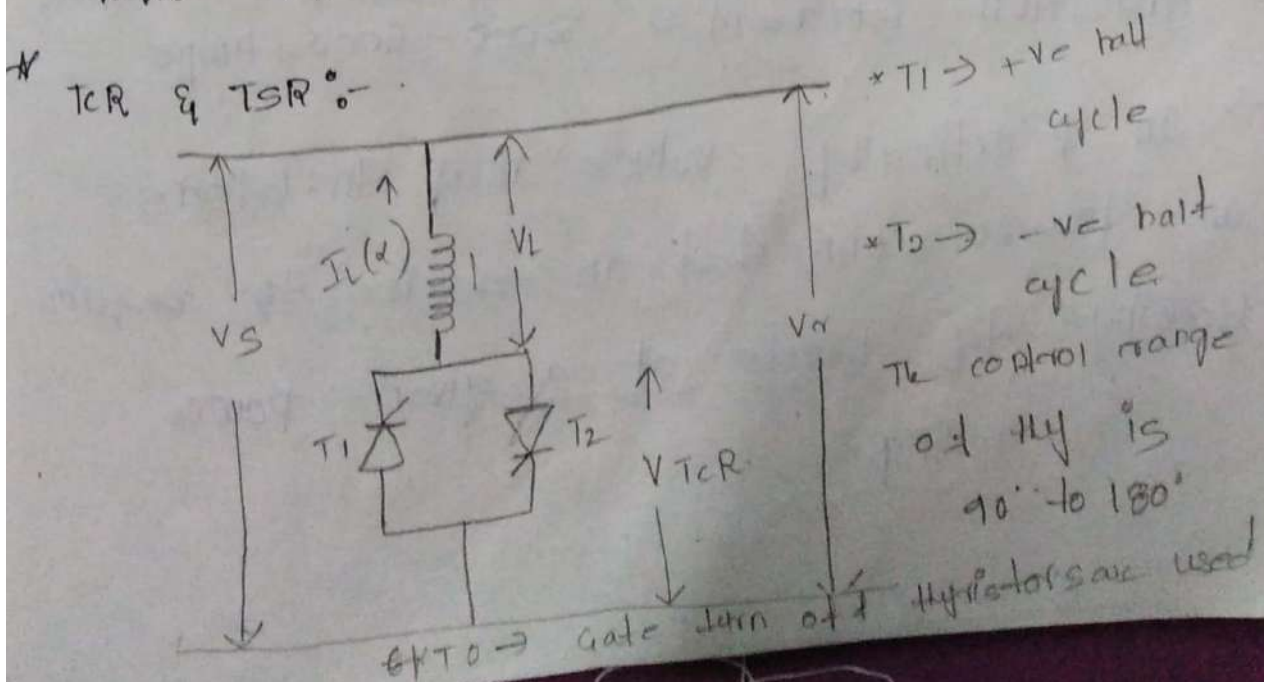

- two thyristors are connected in the anti parallel (T_1 & T_2) GTO (Gate turnoff thyristor)
- series connected with air cored Reactor is shown in fig.
- T_1 will conduct during the +ve half cycle & T_2 will conduct during the -ve half cycle.
- the control range of thyristors is 90° to 180°
- fig ① shows single phase, thyristor controlled reactor it consists of fixed air cored reactor of Inductance (L). In a bidirectional thyristor valves (switches)
- currently available thyristor are drawn Vtg range $400V - 900V$
- conduction currents $3000 - 6000$ Amps.
- In practically valves may thyristors are 10-20 connected in series to require blocking Vtg levels at a given power rating.

operation:-

→ Thyristor valve coming into the conduction by applying gate pulses to same polarity.

→ The valve automatically blocks after the AC current crosses to 0, unless the gate signal is re applied.

→ It will operate on natural commutation (or) line commutation the current in the reactor can be controlled from max to zero by the method of thyristor delay angle control.

→ The thyristor valve is delay with respect to the heat of applied voltage in each half cycle, at the duration of current control.

$$V_s = V_L + V_{TCR} \quad \text{--- (1)}$$

$$V_s = V_L \quad \text{--- (2)}$$

V_{TCR} = There is no drop voltage


$$\therefore V_s = V_L = L \frac{di}{dt} \quad \text{--- (3)}$$

$$V_s(t) = V \cos \omega t$$


$$\begin{aligned}
 i_L(t) &= \frac{1}{L} \int_{\alpha}^{\omega t} v_S(t) dt \\
 &= \frac{1}{L} \int_{\alpha}^{\omega t} V \cos \omega(t) dt \\
 &= \frac{V}{L} \int_{\alpha}^{\omega t} \cos \omega t dt \\
 &= \frac{V}{L} \left[\frac{\sin \omega t}{\omega} \right]_{\alpha}^{\omega t}
 \end{aligned}$$

$$i_L(t) = \frac{V}{\omega L} [\sin \omega t - \sin \alpha]$$

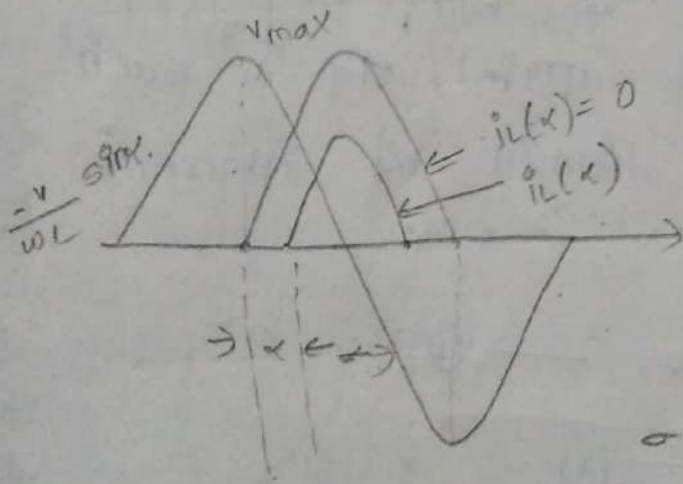If current flowing inductor is 1 sec the absorption capacity of VAR ↑ sec




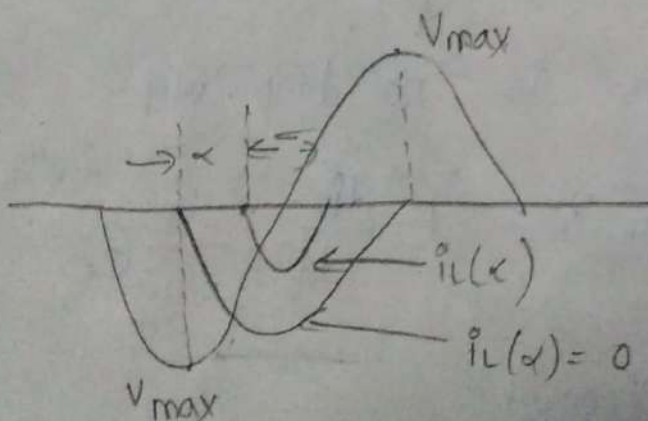$\omega t \frac{V}{\omega L} \sin \alpha$
 $\alpha \rightarrow$ firing angle
 \rightarrow conduction angle
 $\pi + 2\alpha \rightarrow$ +ve half cycle



Above fig shows delay angle firing angle controlled for +ve & -ve half cycles the method of current controlled during the +ve & -ve half cycles shown in above figure. when the v_d is max. at fig (\downarrow max) at that current in the inductor $i_L(\alpha) = 0$ still not stop to absorb the reactive power.

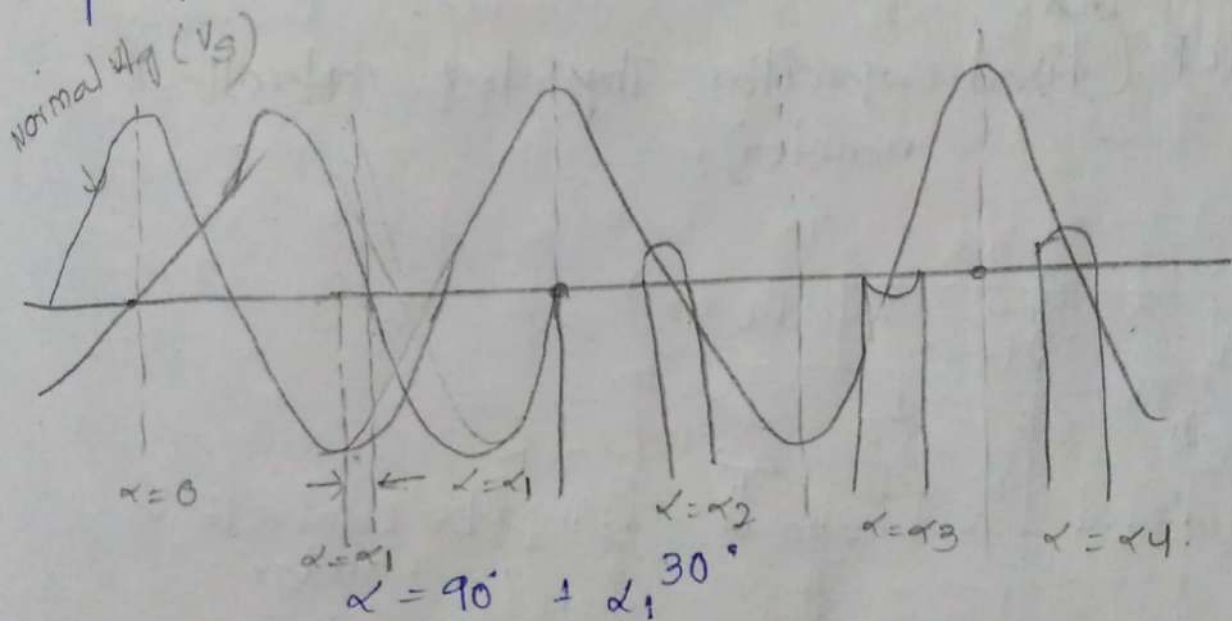It starts from $\alpha = 90^\circ$ to 180° upto that period only inductor. It stores the reactive power



$$\alpha = 90^\circ + \alpha_2^{40^\circ}$$

$$\alpha = 90^\circ + \alpha_3^{50^\circ}$$

$$\alpha = 90^\circ + \alpha_4^{60^\circ}$$

Positive half cycle $\rightarrow (\alpha \leq \omega t \leq \pi - \alpha)$

Negative half cycle $\rightarrow (\pi + \alpha \leq \omega t \leq 2\pi - \alpha)$

When ever $\alpha \rightarrow \uparrow$ ses from 0° to max value


$$\alpha = 0, \alpha = \alpha_1, \alpha = \alpha_2, \alpha = \alpha_3, \alpha = \alpha_4$$

* By \uparrow ses the ' α ' the conduction angle
 \downarrow ses and also current flowing inductor
 is \downarrow ses the amplitude

$$I_{CF}(\alpha) = \frac{V}{\omega L} \left(1 - \frac{2}{\pi} - \frac{1}{\pi} \sin 2\alpha \right) \quad \text{--- (3)}$$

31/5/22 from eqn $\frac{V}{\omega L} [\sin \omega t - \sin \alpha]$

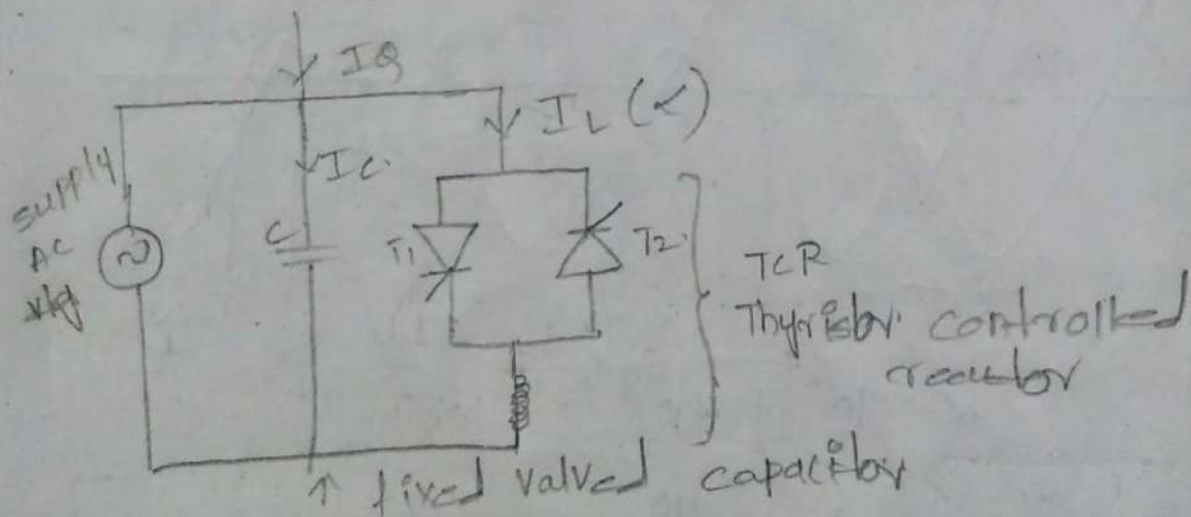FC-TCR (fixed capacitor Thyristor controlled reactor).



$$I_Q = I_C + I_L F(\alpha)$$

Above fig shows the fixed capacitor - TCR.

* Above fig shows

(a) without using coupling ILL.


The current in the reactor by varying firing angle (α) $\alpha = 90^\circ$ to 180°

$\alpha = 90^\circ$ TCR absorbs max reactive power
 $\alpha = 180^\circ$ fully on state.

When $\alpha = 180^\circ$ There is no absorption of RP from bus. In this state TCR is in 'off' state.

→ The capacitor value is fixed with the help of filter n/w to generate RP required but it provides a low impedance at selected frequencies

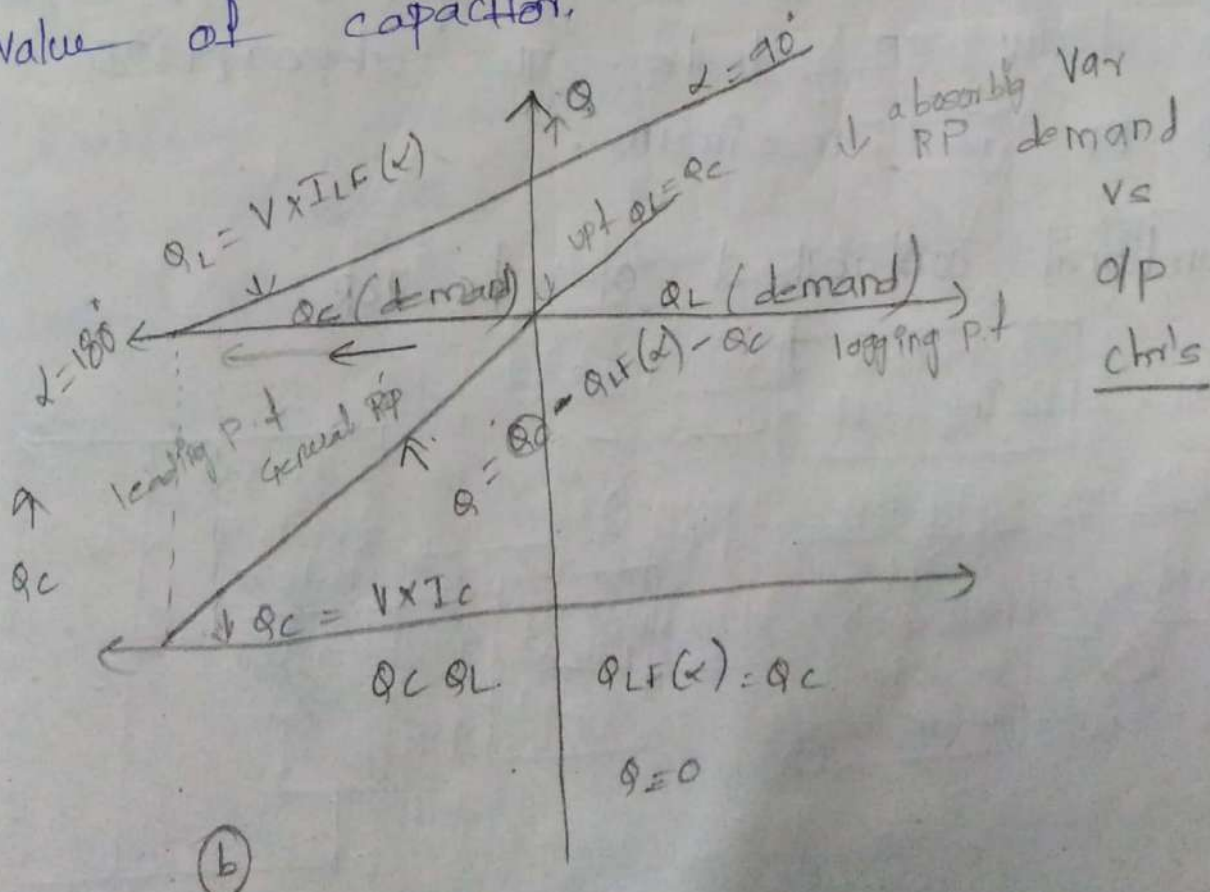→ This TC-TCR consists of variable reactor (Ind) (controlled via delay angle α) and fixed value of capacitor.



f.c. "Qc" oppose the variable. Var generation (Q_g). absorption to provide required total

Var of $Q = Q_{LF}(\alpha) - Q_c$

1) when ever $\alpha = 180^\circ$ TCR is fully off state in this cond'n. The capacitor only generate reactive power in to the bus


$\therefore Q = 0 - Q_c$


2) under the vpf cond'n there is no absorption and gen of RP.

$\rightarrow Q_{LF}(\alpha) = Q_c$, The resultant $Q = 0$. There is no gen, no absorption of RP.

3) when ever $\alpha = 90^\circ$ in this cond'n TCR is in fully on state. The absorption of RP is maximum.

functional controlled of f.c.-TCR.

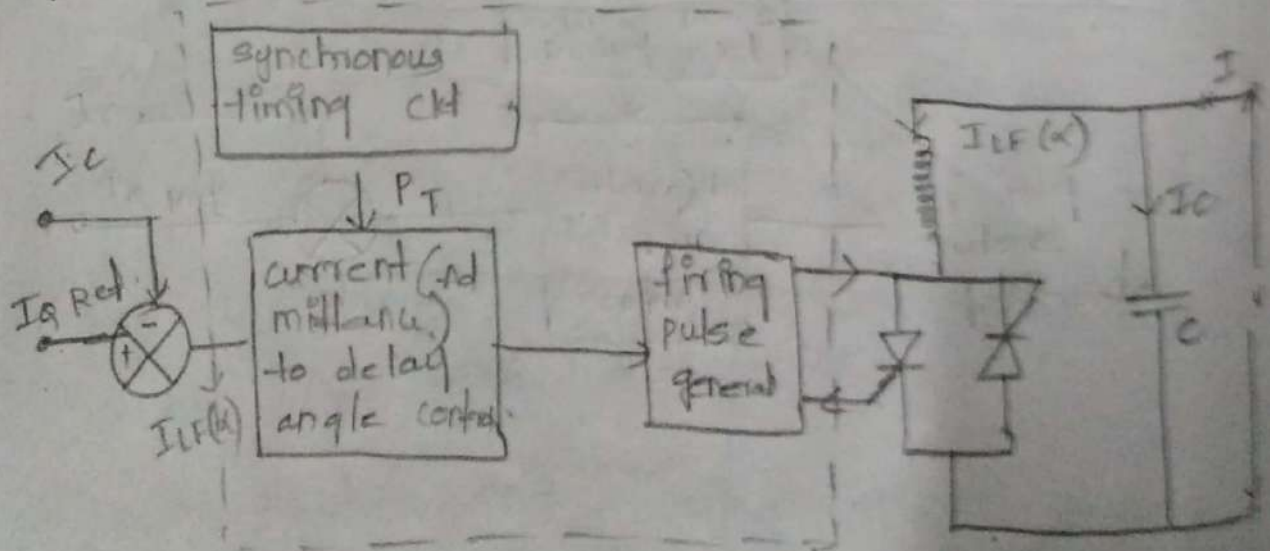

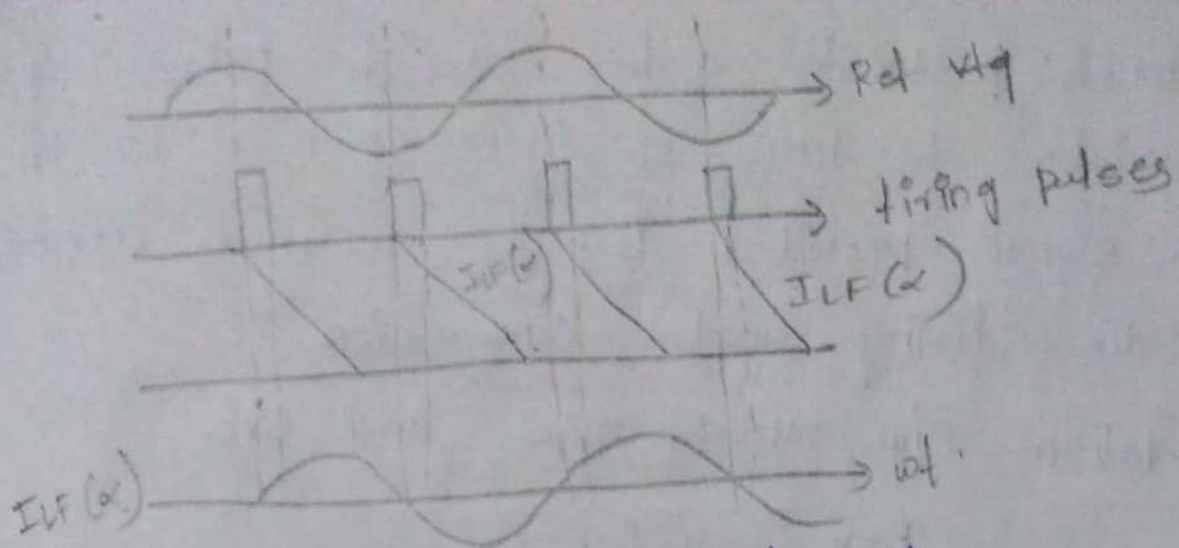

→ The control of Thyristor control in FC-TCR VAR generator need to provide 4 basic

1) synchronous timing:

This can be provided by phase locked loop ckt, that turns in synchronism with AC sys V_g and gen timing pulses wrt to V_g .

2) Reactive current (or) admittance) to firing angle conversion.

3) computation of reactor current $ILF(\alpha)$ from total o/p current,

$$I_Q = I_C - ILF(\alpha)$$

→ In this +ve → inductive o/p current
-ve → capacitive o/p current.

4) Thyristor pulse generation. This is done by the firing pulse generator.

→ which produces gate current pulses for thyristor to turn on in response to the o/p signal provided by the reactive current to the firing angle conversion.

Relation B/w susceptance and SVC

$$I_{SVC} = V \cdot j B_{SVC}$$



$$B_{SVC} = B_c + B_{TCR}$$

$$B_{TCR} = 0$$

$$\alpha = 180^\circ$$

$$B_{SVC} = B_c$$

$$V = V_{ref}$$

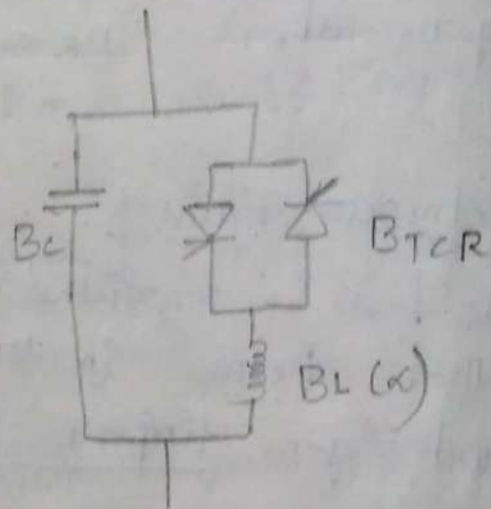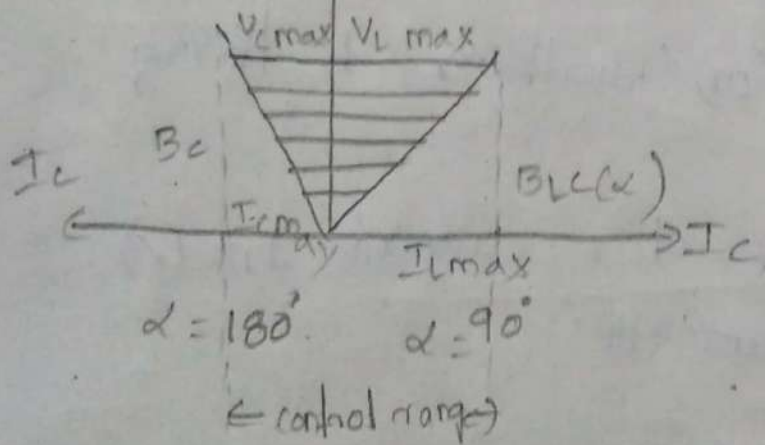

V-I char's of FC-TCR.

$B_c \rightarrow$ capacitive admittance.

$B_L \rightarrow$ maximum inductive admittance


$I_{Lmax} \rightarrow$ inductive current limit

$I_{Cmax} \rightarrow$ capacitive current limit.

$$\alpha = 90^\circ$$

$$B_{TCR} = \max$$

(b) FC-TCR with coupling TIT.

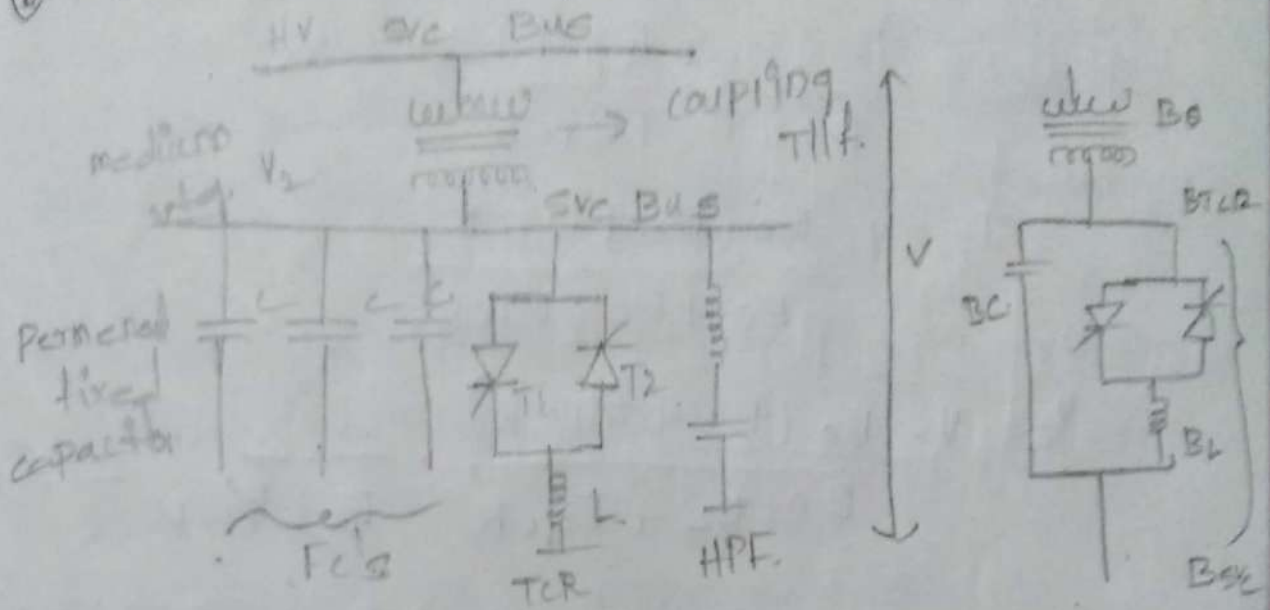

$$\Rightarrow B_{SVC} = \frac{B_0 (B_c + B_{TCR})}{B_0 + B_c + B_{TCR}} \quad \text{--- (1)}$$

divide Nr & Dr with B_0

$$B_{SVC} = \frac{1}{1 + \frac{B_c + B_{TCR}}{B_0}} (B_c + B_{TCR}) \quad \text{--- (2)}$$

$B_{SVC} \rightarrow$ maximum of fc-TCR.

$$\alpha = 180^\circ$$

$$B_{TCR} = 0$$

$$B_{SVC \max} = \frac{B_0 B_c}{B_0 + B_c} \quad \text{--- (3)}$$

$B_{SVC} \rightarrow$ minimum $\alpha = 90^\circ$

$$B_{SVC \min} = \frac{B_0 (B_c + B_{TCR})}{B_0 + B_c + B_{TCR}} \quad \text{--- (4)}$$

$$V_2 = I_2 \cdot j \frac{1}{B_c + B_{TCR}}$$

$$I_2 = V_2 \cdot j B_{SVC}$$

$$B_{SVC} = \frac{B_0 (B_c + B_{TCR})}{B_0 + B_c + B_{TCR}}$$

$$I_2 = V_2 \cdot \frac{B_0 (B_c + B_{TCR})}{B_0 + B_c + B_{TCR}}$$

$$V_2 = V_2 \cdot \frac{B_0 (B_c + B_{TCR})}{B_0 + B_c + B_{TCR}} \cdot \frac{1}{B_c + B_{TCR}} \quad \text{--- (5)}$$

$$V_2 = V_2 \cdot \frac{B_0}{B_0 + B_c + B_{TCR}}$$


when ever to design fc-TCR the coupling
T/F of secondary Wg must be know.

~~So~~


UNIT-IV
SVC and STATCOM

①

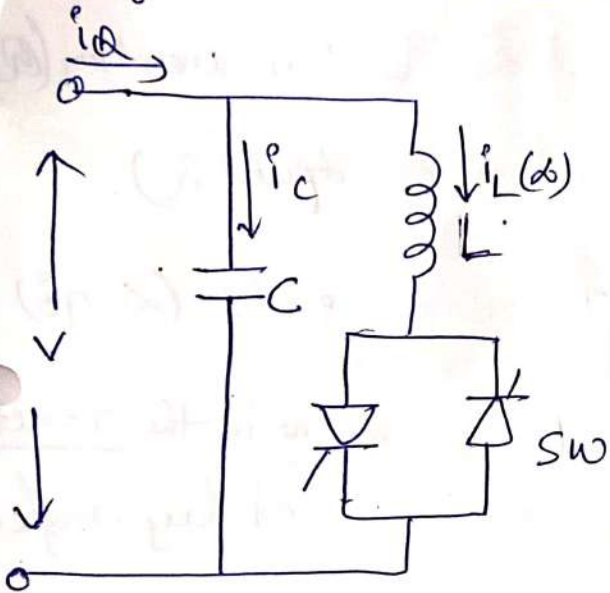Fixed Capacitor - Thyristor Controlled Reactor (FC-TCR)



(a) $I_Q = I_C + I_L(\alpha)$

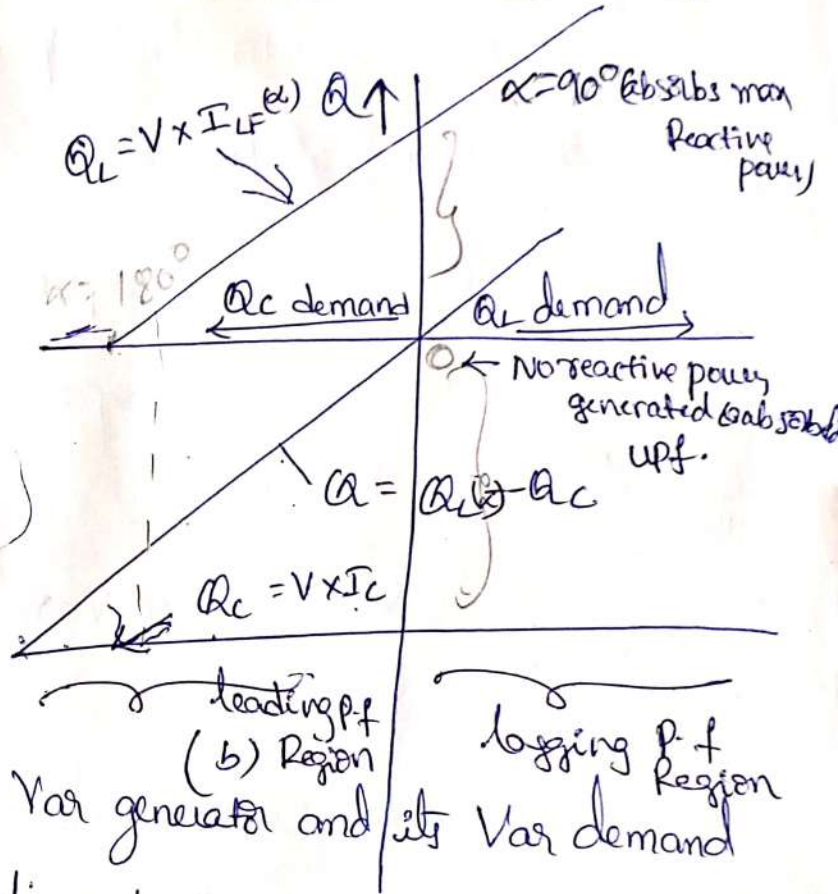

Basic FC-TCR type static Var generator and its Var demand Versus Var output characteristics.

→ Above fig shows fixed capacitor thyristor controlled reactor (FC-TCR). The current in the reactor is varied by firing angle control.

→ The capacitor value is fixed with the help of filter network to generate reactive power required, but it provides a low impedance at selected frequencies.

→ This FC-TCR consists Variable reactor (Inductor) (controlled by delay angle α) and fixed valued Capacitor.

→ Var demand vs output char shown in fig.

→ Fixed Capacitor (C_c) opposes the Variable Var generation (C_v) absorption to provide req total ϕ Var output (ϕ).

→ At max Var output TC reactor is off ($\alpha=90^\circ$)

→ To decrease the Capacitive o/p, the Current in the reactor is increased by decreasing the delay angle α .

$C_c \downarrow$
 $I_L \uparrow$



→ At 'Zero' o/p Var, the Capacitive & Inductive Currents become equal, and Capacitive & Inductive Vars Cancel out.

$V_{arc} = V_{arL}$
 $\Rightarrow 0$ o/p

→ further decreasing the delay angle the Inductive Current becomes larger than the Capacitive Current, the resultant Var output is Inductive.

→ at zero delay angle, the thyristor-controlled reactor

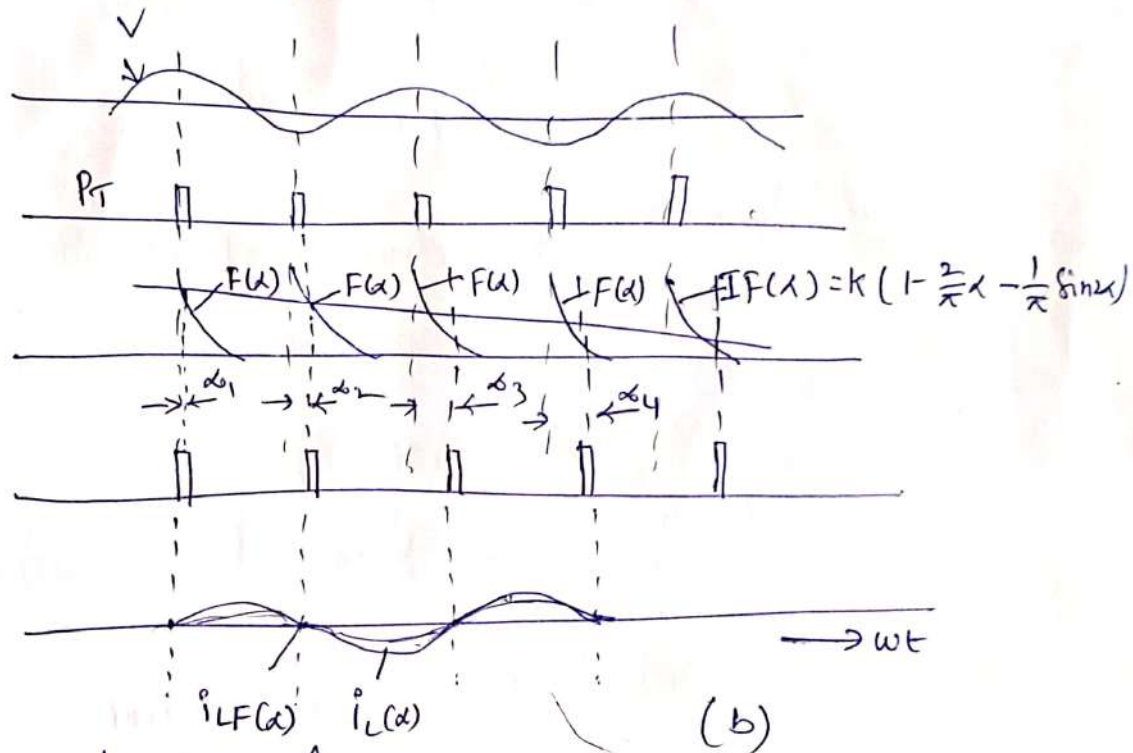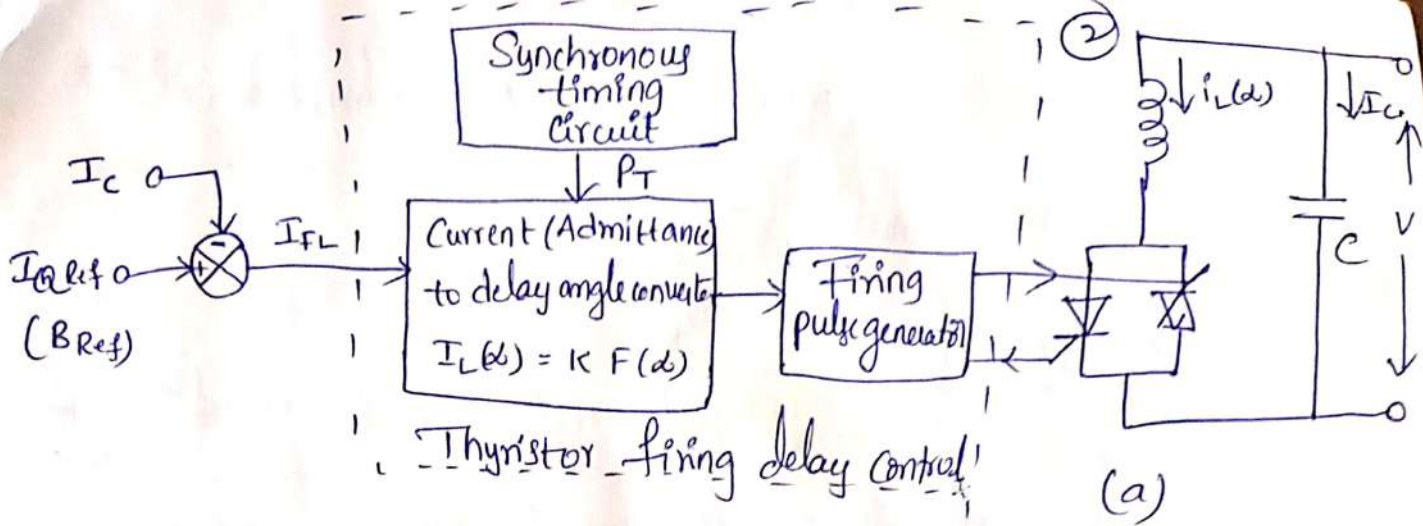conducts current over the full 180° interval, results Inductive Var o/p is equal to diff b/w the Var generated by the Capacitor & those absorbed by the fully conducting reactor.



(a) Functional control scheme for the FC-TCR type static Var generator.
 (b) waveform.

→ The Control of the thyristor-Controlled reactor in FC-TCR type Var generator need to provide four basic functions.

1) is Synchronous timing:- This function is provided by phase locked loop ckt that runs in Synchronism with the ac system voltage and generates timing pulses with voltage

→ Second function is reactive current (or admittance) to firing angle conversion.

→ 3rd function is Computation of reactive current I_L from total output current I_a .

i.e. $I_L = I_a - I_{a \text{ ref}}$. Subtracting Capacitive Current.

+ve polarity means Inductive o/p current

-ve " " Capacitive o/p current

→ 4th function is Thyristor firing pulse generation. This is done by the firing pulse generator.


which produces the necessary gate current pulse for thyristor to turn on in response to the output signal provided by the reactive current to firing angle conversion.

→ Taking a block box view point of FCR type VSC generator can be considered as a Controllable reactive admittance connected to the ac system.

Relation b/w Susceptance and I_{svc} .


$$I_{svc} = V \cdot j B_{svc}$$

Where $B_{svc} = B_c + B_{TCR}$

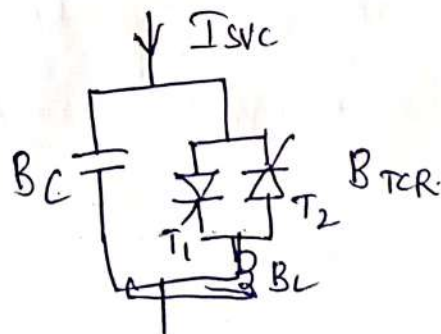


FCVC


(3)

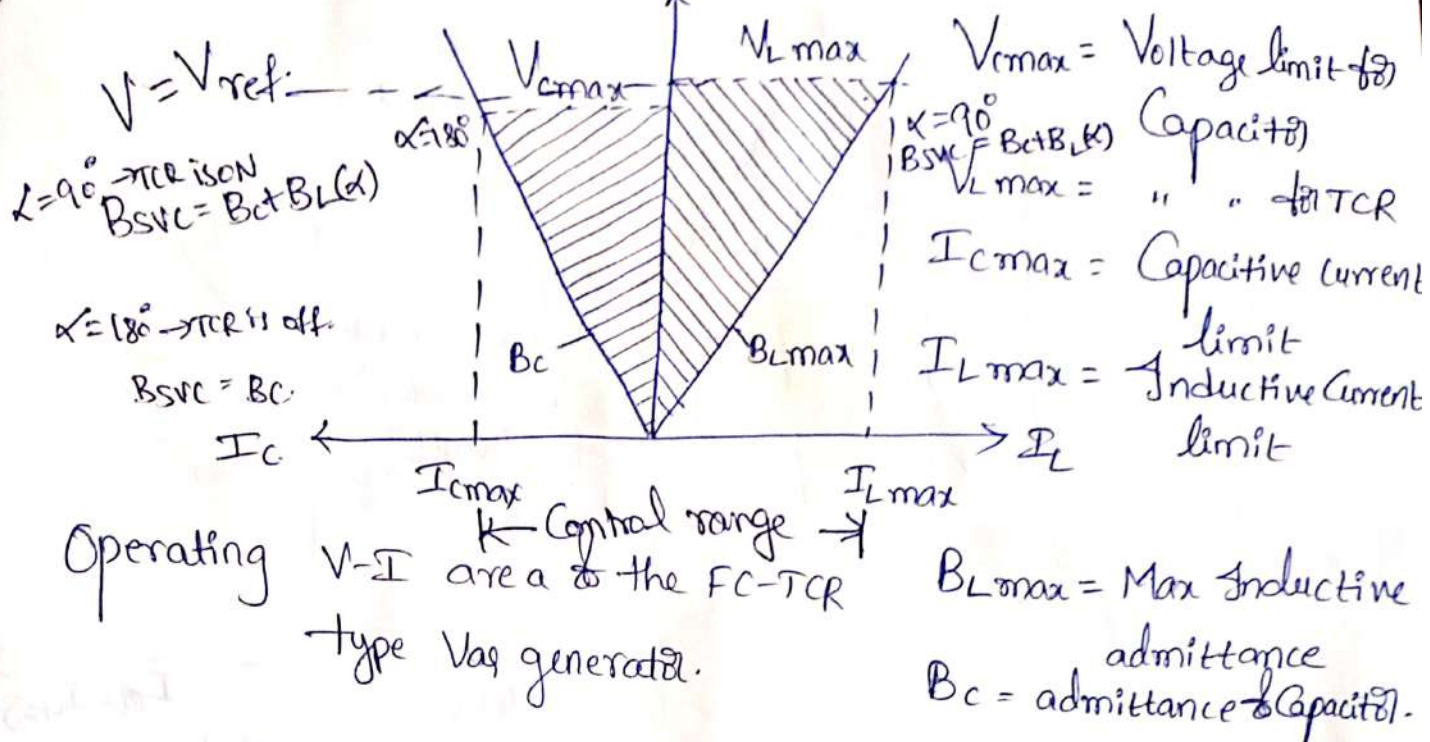

→ above V-I operating area of the FC-TCR Vargenerator is defined by maximum Capacity of Capacitive & Inductive admittance and Voltage, current ratings of Capacitor, Inductor & Thyristor.

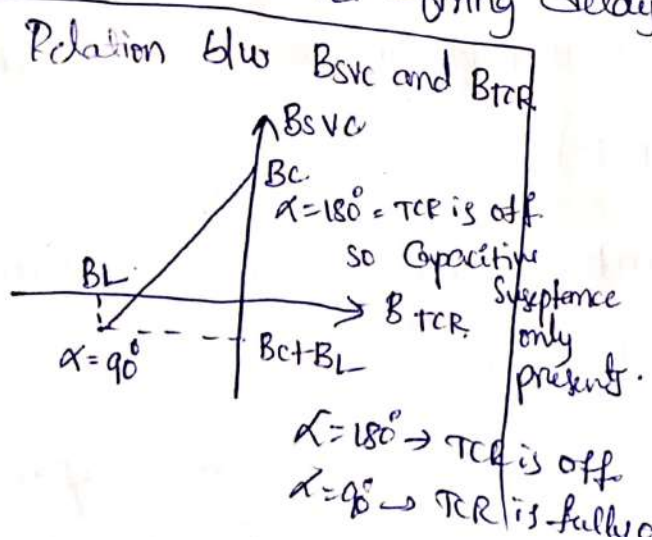→ Transfer function of FC-TCR is $G(s) = k e^{-T_d s}$
 (s) is Laplace transform operator
 k is a gain constant
 T_d firing delay angle (s)



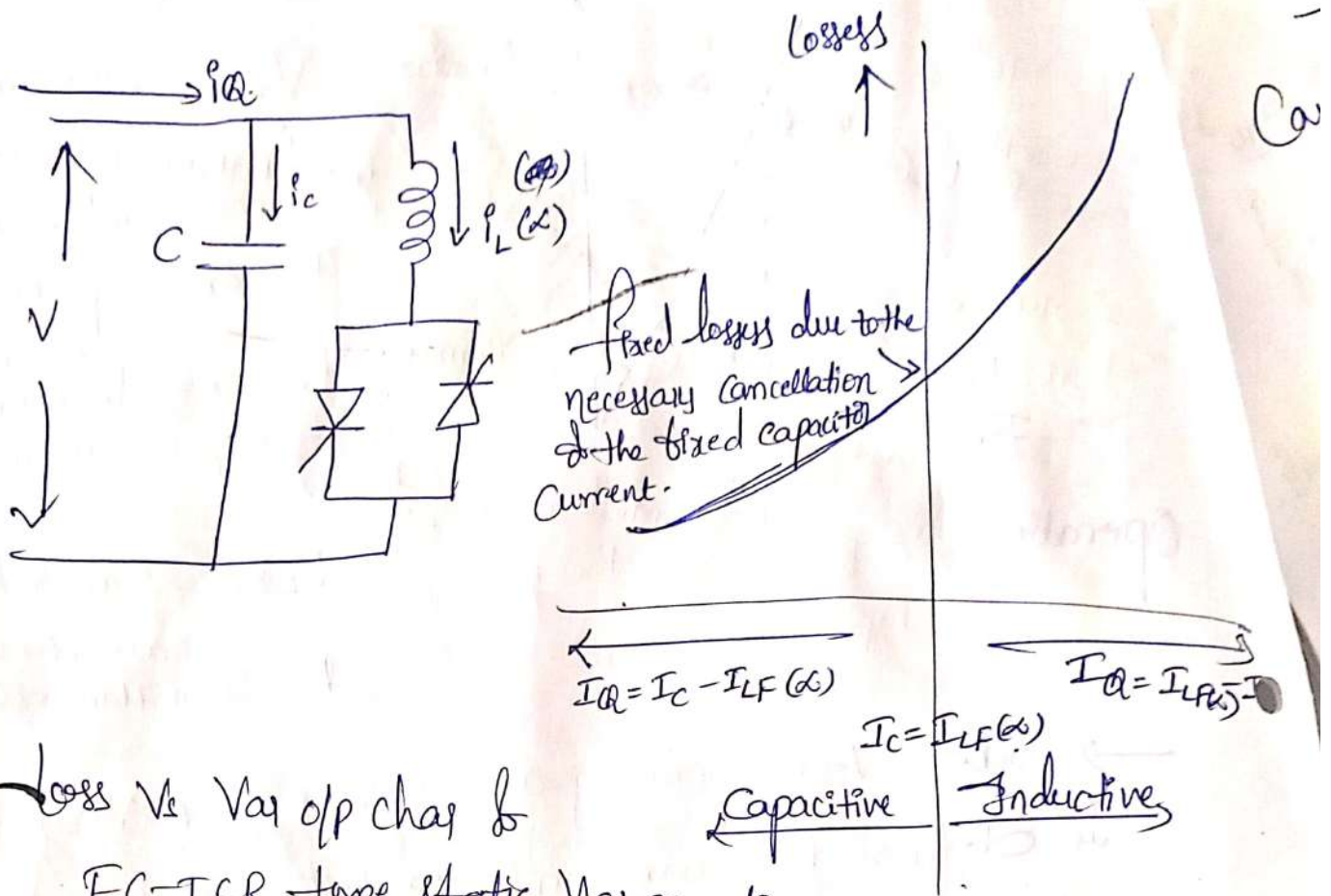

Loss vs Var o/p char for FC-TCR type static Var generator.

In FC-TCR type Var generator, there are 3 major losses occurred

- ① The Capacitor losses (small)
- ② Reactor losses (these increase with square of current)
- ③ Thyristor losses (these are almost linear with current)

→ Thus total losses increase with increasing in current


and decrease with decreasing the Capacitive Var output. Shown in fig (a).

→ Zero o/p is obtained by cancelling Capacitive loss with Inductive ($I_c = I_L$)

→ Their loss char Curve is, advantageous when avg Capacitive Var o/p is relatively high this type is applications req Industrial p.f Correction.

and its advantageous when avg var o/p is low,
Dynamic Compensation & Power transmission system.

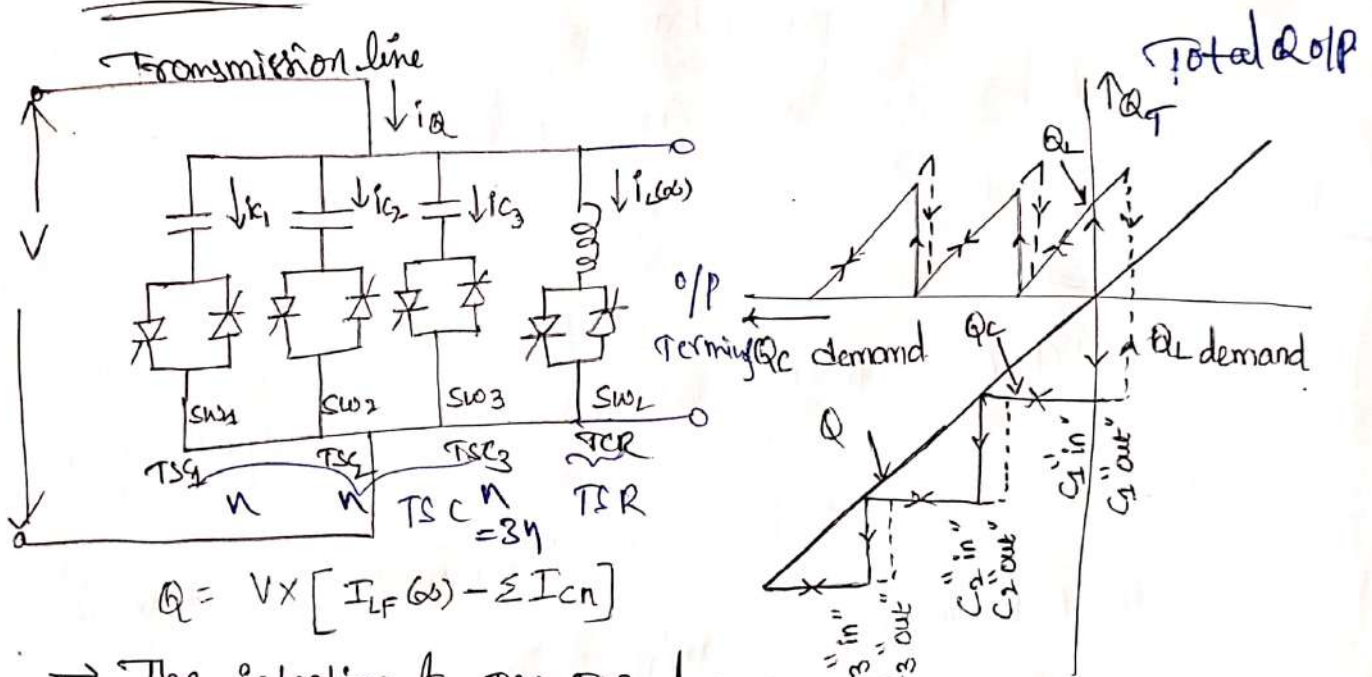Thyristor-Switched Capacitor - Thyristor-Controlled Reactor (TSC-TCR) :-



→ The intention of TSC-TCR design is minimizing stand by losses and increasing operating flexibility
 → wastage & fuel losses

→ For a given Capacitive output range, it consists of 'n' TSC branches and one TCR. The 'n' number of branches determines operating voltage level, maximum var output, current rating of the thyristor valves, bus work and installation cost. etc.

of course, inductive range also can be expanded to any maximum rating by employing additional TCR branches.

operation:-

→ The total Capacitive output range is divided into 'n' intervals. In the first interval, the o/p of the var generator is controllable.

The zero to Q_{cmax}/n range, where Q_{cmax} is the total rating provided by all TSC branches.

In this one capacitor bank is switched in (by firing, for example, thyristor valve sws,) and simultaneously the current in the TCR is set by appropriate firing delay angle so that the sum of the var output of TSC (negative) and that of TCR (positive) equals the Capacitive output required.

→ In 2nd, 3rd, ... nth intervals, the output is controlled in the Q_{cmax}/n to $2Q_{cmax}/n$, $2Q_{cmax}/n$ to $3Q_{cmax}/n$... and $(n-1)Q_{cmax}/n$ to Q_{cmax} range by switching absorb the supply Capacitive vars.

Ex

$n=5 \quad Q_{cmax} = 10 \text{ MVAR}$

Introduce 5 branches

our req is 9 MVAR.

$2 \times 5 = 10 \text{ MVAR} - \Delta \text{TCR} = 9 \text{ MVAR}$

absorb supply Capacitive var.

⑤
→ By being able to switch the Capacitor banks in and out within one cycle of the applied ac voltage, the maximum Supply Capacitive Var in the total output range can be restricted to that produced by one Capacitor bank, and thus, theoretically, the TCR should have the same Var rating as the TSC.

⇒ Var demand Versus the output characteristics of the TSC-TCR type Var generator is shown in fig (b).

The Capacitive Var output, Q_c , is charged in step-like manner by the TSC, and the relatively small Inductive Var output of the TCR, Q_L , is used to

Cancel the surplus Capacitive Vars.
Ex: Explained
⇒ Hence theoretically the TCR should have the same Var rating as the TSC.
A functional Control scheme of TSC-TCR shown below

It provides 3 major functions-

→ 1) Determines the no. of TSC branches needed to be switched in to approximate the req Capacitive output current and computes the amplitude of Inductive current needed to cancel the surplus Capacitive current.

→ 2) Controls the switching of the TSC branches in a "transient-free" manner.


→ 3) Varies the current in the TCR by firing delay angle control.

Supply
ex

Req = 7 MVAR
 Capable C_{each} = C = 2 MVAR
 $\frac{7}{2} = 3.5 \rightarrow$ no. of capacitor banks first switched in at appropriate peak values
 $\frac{7}{2} = 3.5 \rightarrow$ supply vtg so once capacitor supply in in since of p dia of capacitor 8 MVAR
 $\frac{7}{2} = 3.5 \rightarrow$ req firing angle is adjusted to 1 MVAR
 $10 - 1 = 9 \text{ MVAR}$

Required Capacitor & reactor current computation

Req. like 9 MVAR

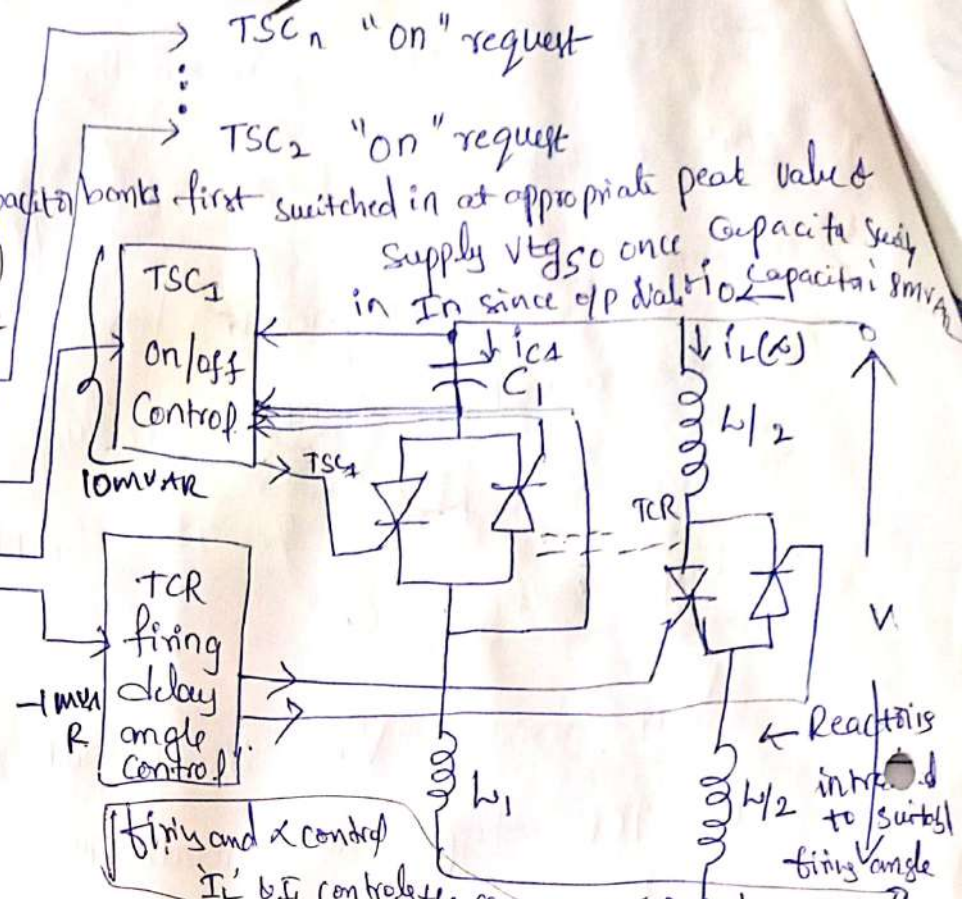

1st function → The input current I_{aRef} represents the magnitude of the requested output current. The magnitude of the current that a TSC branch would draw at the given amplitude V of the ac voltage. The result, gives the no. of capacitor banks needed.

→ The difference in magnitude b/w activated capacitor currents ΣI_{cn} and the reference current I_{aRef} giving the amplitude of i_{L1} of fundamental reactor current req.

2nd function → basic logic for 2nd function (Switching for TSC branches) is shown in fig 5.24 (e). This follows two simple rules for "transient-free" manner.


Switching Summary.

$V_o = V_c$ when it is transient free
 Supply vtg = Capacitor vtg. manner.

→ That is, To Switch the Capacitor bank. (6)

When the V_{tg} across the thyristor valve becomes zero & when thyristor valve voltage is at a minimum.

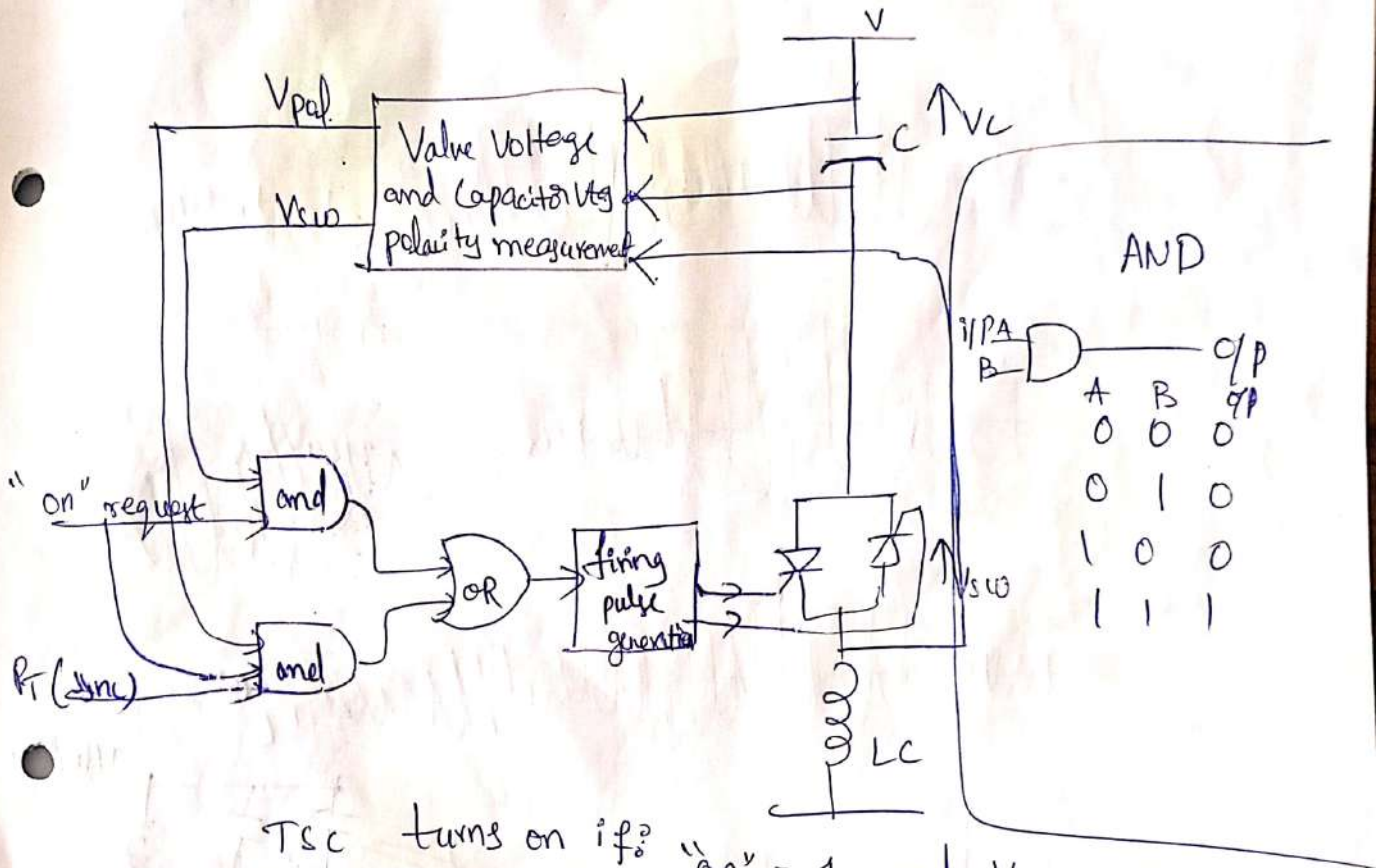→ The actual firing pulse generation for the thyristor in TSC valve is similar to that used for the TCR.



TSC turns on if:

Case (i) - $V_c < V$ ← peak V_{tg} . "On" = 1 and $V_{sw} = 1$

Case (ii) - $V_c = V$ ← instantaneous ac v_{tg}. "On" = 1 and $P_T = 1$ and $V_{pol} = 1$

$V_{sw} = 0$ $V_{sw} = 1$ when $V_c = V$


$P_T = 1$ when $v = V$

$V_{pol} = 1$ when $\text{sign } v = \text{sign } V_c$

Case (iii) $V_c < V$





$\alpha = 0$



$V_{sw} = \text{min}$

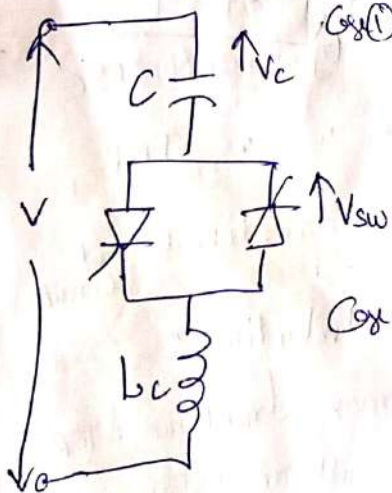

→ The third function (TCR during delay angle control) is similar to FC-TCR. The operation of TSC-TCR type VAr generator with 3 Capacitor banks is shown below.

$$I_{Qref} = I_{Qc} = I_c + I_L$$

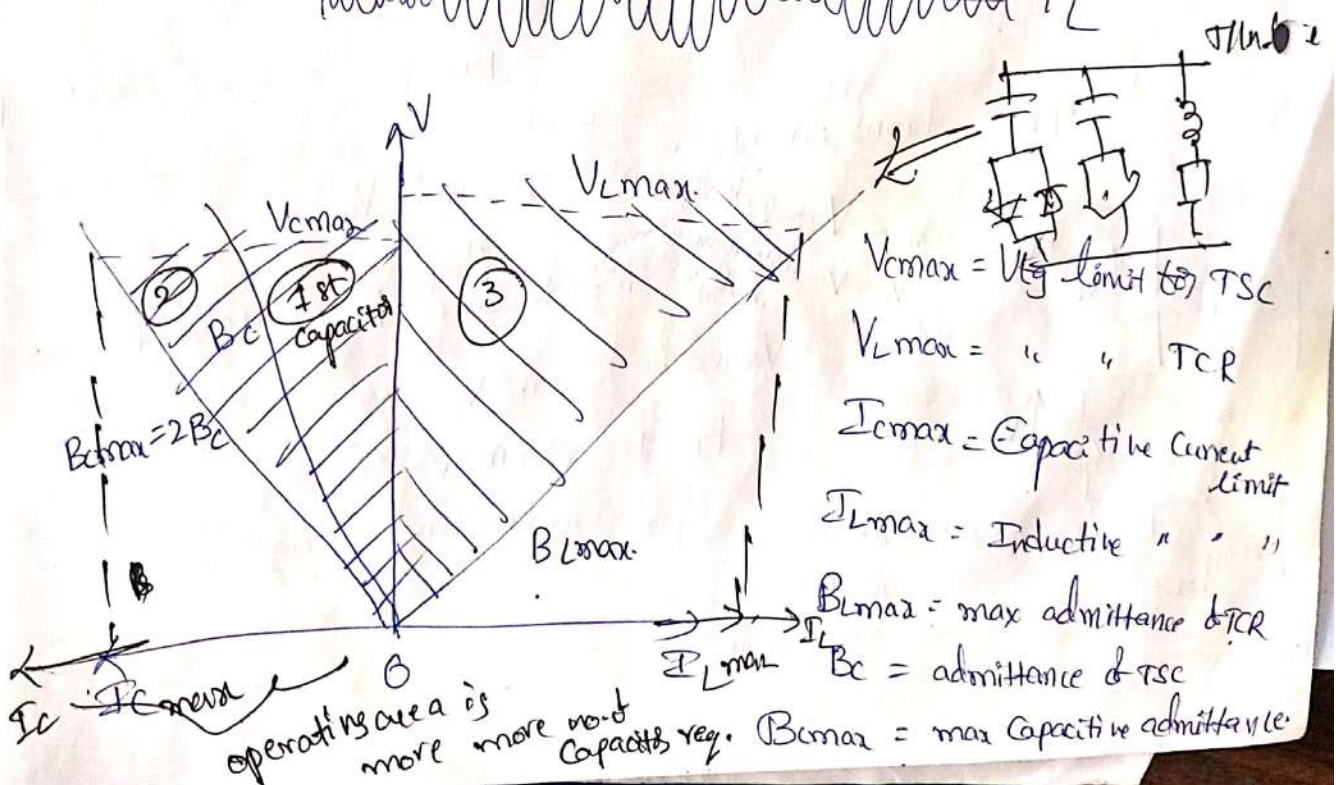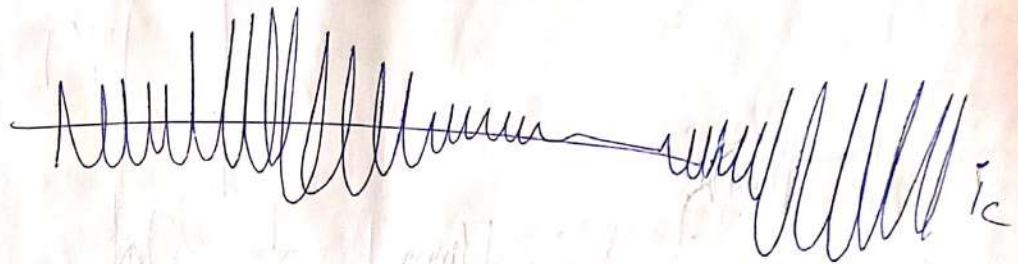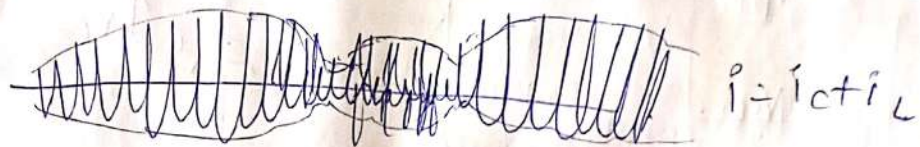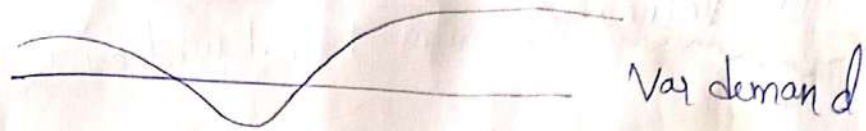

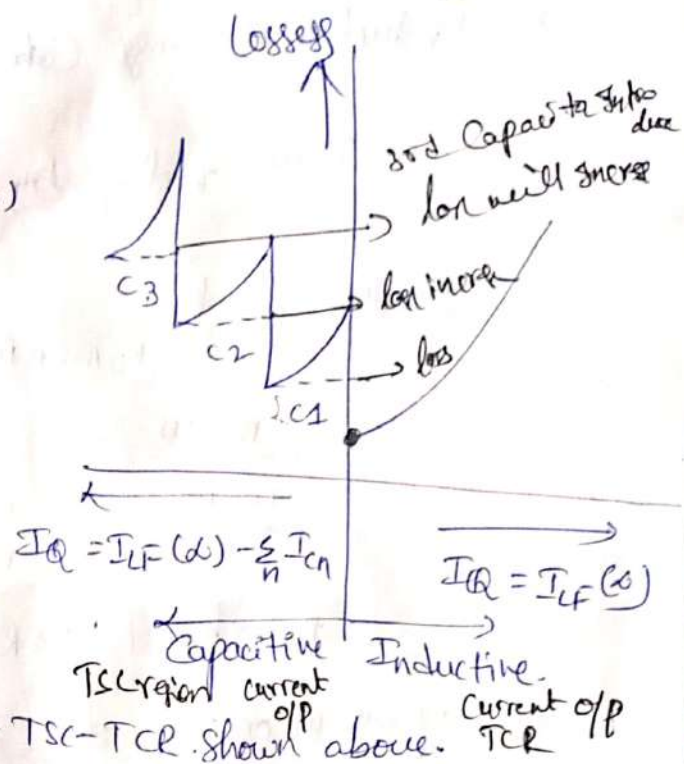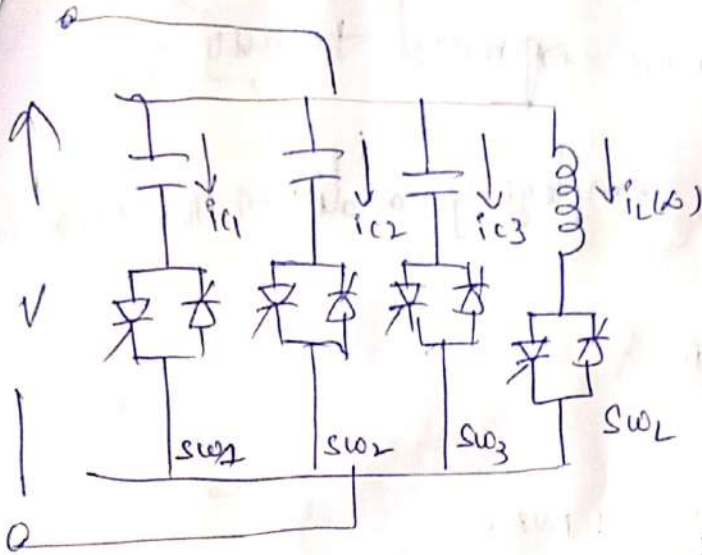

Loss vs off chg & TSC-TCR shown above.

At a slightly below zero var output, all capacitor banks are switched out, the TCR current is zero or negligibly small, and consequently, the losses are zero or almost zero.

→ as the Capacitive output is increased, an increasing no. of TSC banks are switched in with the TCR absorbing the supply Capacitive vars.

→ More over, losses & TCR vary from max to zero b/w switching of TSC banks are also success.

→ The main design intuition is to reduce the stand by losses

→ It consists of 'n' no. of TSC branches & one TCR.

→ 'n' no. of branches determine operating Vtg.

~~Supply~~ → either connected in star or delta

$$Q = V \times [I_L(\omega) - \sum I_{Cn}]$$

Get var off this scheme

↓ Inductive Cur

↓ 'n' no. of Capacitive Currents.

Introduction of UPFC:

The UPFC concept was introduced by Gyugui in 1991

→ UPFC was introduced for the real time control & dynamic compensation of AC transmission system

→ UPFC was able to control simultaneously or selectively all the parameters affecting power flowing. TLN line (i.e. vtg, impedance, phase angle)


active power & Reactive power

→ alternatively, independently control both the real & reactive power flow in the line. → 294

→ The UPFC can operate under balanced sine wave condition.

→ Basic operating principle

1) UPFC is

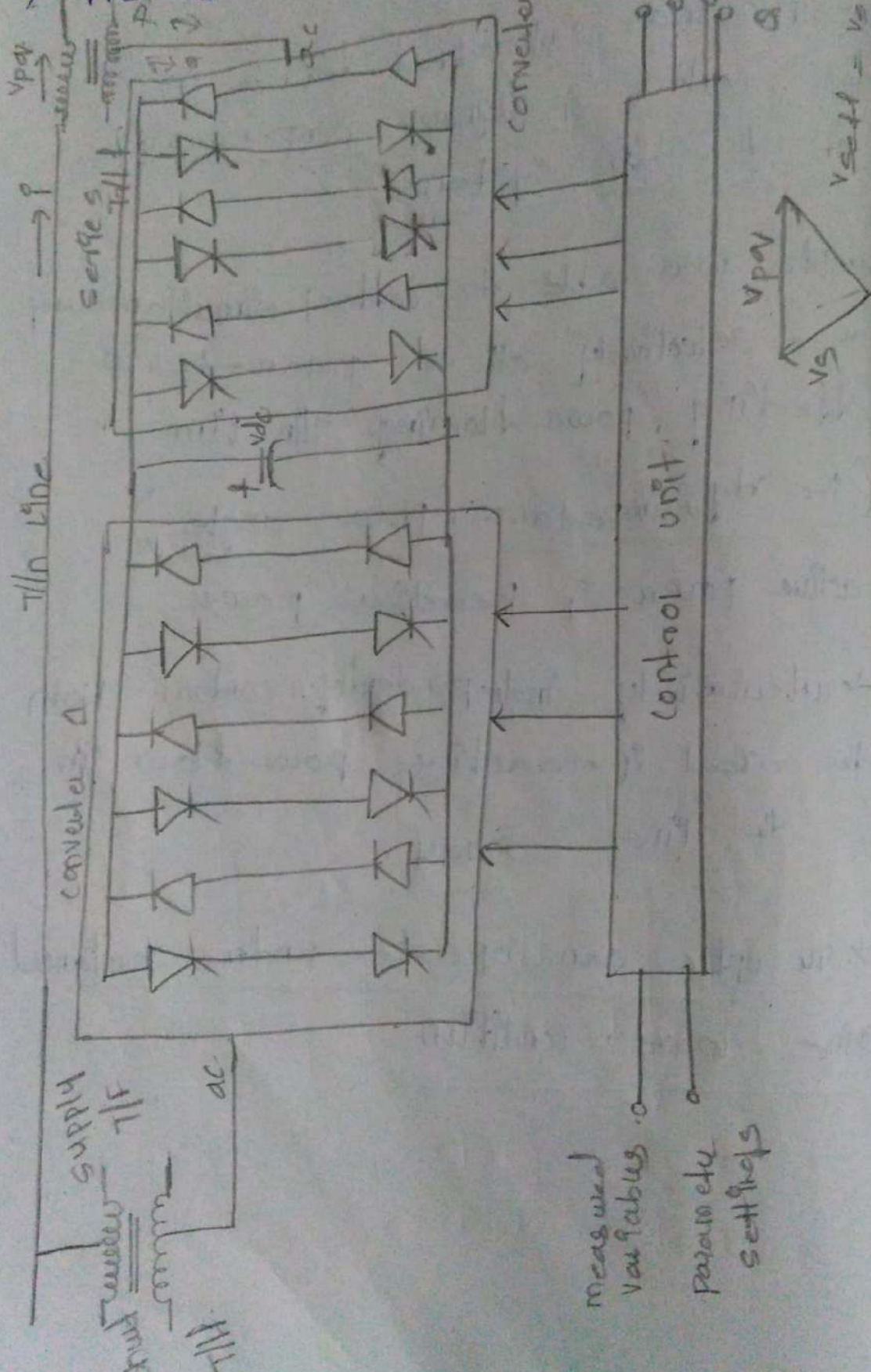

→ fig ③ shows VFTC controller by
2 Back to Back Vtg source converter

1) VFTC is a generalised synchronous
Vtg source (SVS), represented at the
fundamental freq by Vtg phasor

V_{pq}

② It controllable magnitude V_{pq}

$$V_{pq} (0 \leq V_{pq} \leq V_{pq \max})$$

and angle $\theta (0 \leq \theta \leq 2\pi)$ 0 to 360°

In series with Tln line.

2) VFTC consists of 2 voltage source
converters, converter-1 (~~STATCOM~~)

and converter-2 (SSSC) with common DC

link. V_{dc} provided by DC storage

capacitor.

→ fig shows Ideal ac to ac Power
converter in which the real power

can freely flow in either dire-

ction b/w the ac terminals of

the converter and each converter

Can independently generate or absorb reactive power as its own ac o/p terminals,

→ Converter 2 provides main fun of o/p ac by injecting a v_{pq} (V_{pq}) and with controllable magnitude " V_{pq} " & angle " ϕ " in series with the line via

series (Injection T/T) T/T. This injection v_{pq} acts like synchronous ac v_{pq} source.

→ The H/n line current flows to this v_{pq} source. results in reactive and the real power exchange b/w it and ac source.

→ The Reactive power exchange and the ac terminals i.e at the terminals of series injection T/T is generated internally by the converter.

→ The Real power exchange at the ac terminals is converted in to DC power

which appears at the dc link as a positive or negative real power demand.

Basic operation of converter - 1

It is to supply ~~and~~ absorb the real power demand by converter - 2 at a common dc link, to support the real power exchange resulting from the series the Vtg injection.

→ The dc link power demand of con-2 is converted to back to ac by

con-1 and it coupled to the thn line. with a shunt connected Vtg

→ In addition to the real power 'P' of con-2, con-1 also generates or absorbs controllable reactive power by

providing shunt reactive compensation of line.


Note: There can be no reactive power flow to the Vtg dc link.

Conventional Transmission control capabilities

control capabilities are mainly 4 types


- 1) voltage regulation
- 2) line impedance compensation
- 3) phase shifting
- 4) simultaneous control of V_{tg} , impedance and phase angle.

-ve about
+ve ahead

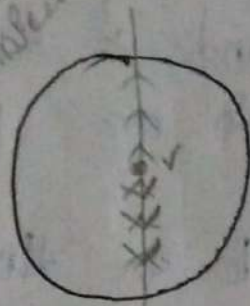

fig(1)


control the phase angle
about 360°

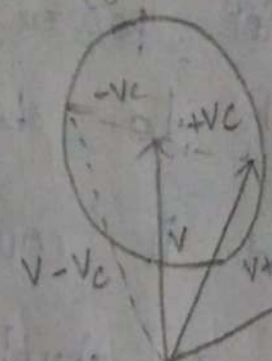

fig(2)



fig(3)

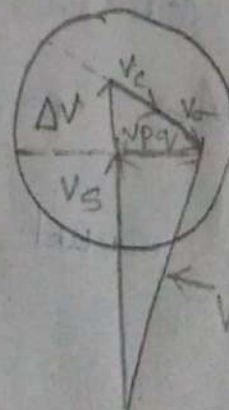

fig(4)

Fig ① shows v_{pq} regulation with continuously variable inphase/anti-phase v_{pq} injection for v_{pq} increment.

$$v_{pq} = V \pm \Delta V$$

→ This is obtain by tap changing TTT
→ Fig ② shows v_{pq} is the injected in quadrature with line current 'I'
This is similar to series capacitive and inductive line compensation attain by SSSC.

→ The injected series compensator v_{pq} can be kept constant. It is independent of line current variations

→ Fig ③ shows phase angle regulation, where $v_{pq} = V$ is injected with an angular induction. worst supply v_{pq} relation that achieves design phase shift without any change in magnitude.

→ Fig ④ shows multiple power flow control executed by simultaneously terminal v_{pq} regulation. $(\pm \Delta V)$ series capacitive

Line compensation (V_{pq}), Phase shifting (δ)

$$V_{pq} = \Delta V + V_q + V_r$$

$$P - jQ = \frac{V_s V_r}{X} \sin \delta \Rightarrow V_{pq} = 0 \text{ --- (1) without any compensator}$$

$$P - jQ = V_r \left[\frac{V_s + V_{pq} - V_r}{X} \right]^* \sin \delta \Rightarrow \text{with opt.c.}$$

$$V_{pq} \neq 0$$

$$P - jQ = V_r \left[\frac{V_s - V_r}{X} \right]^* + \frac{V_r V_{pq}}{-jX}^*$$

Independent. Real and Reactive power flow control.

V_{pq} = injected compensating V_{pq}

$$V_{pq} = 0 \text{ --- (1)}$$

There is no injected V_{pq} .

No compensator using.

$$P_o(\delta) = \frac{V_s V_r}{X} \sin \delta \text{ --- (2)}$$

$$Q_o(\delta) = \frac{-V_s V_r}{X} (1 - \cos \delta) \text{ --- (3)}$$


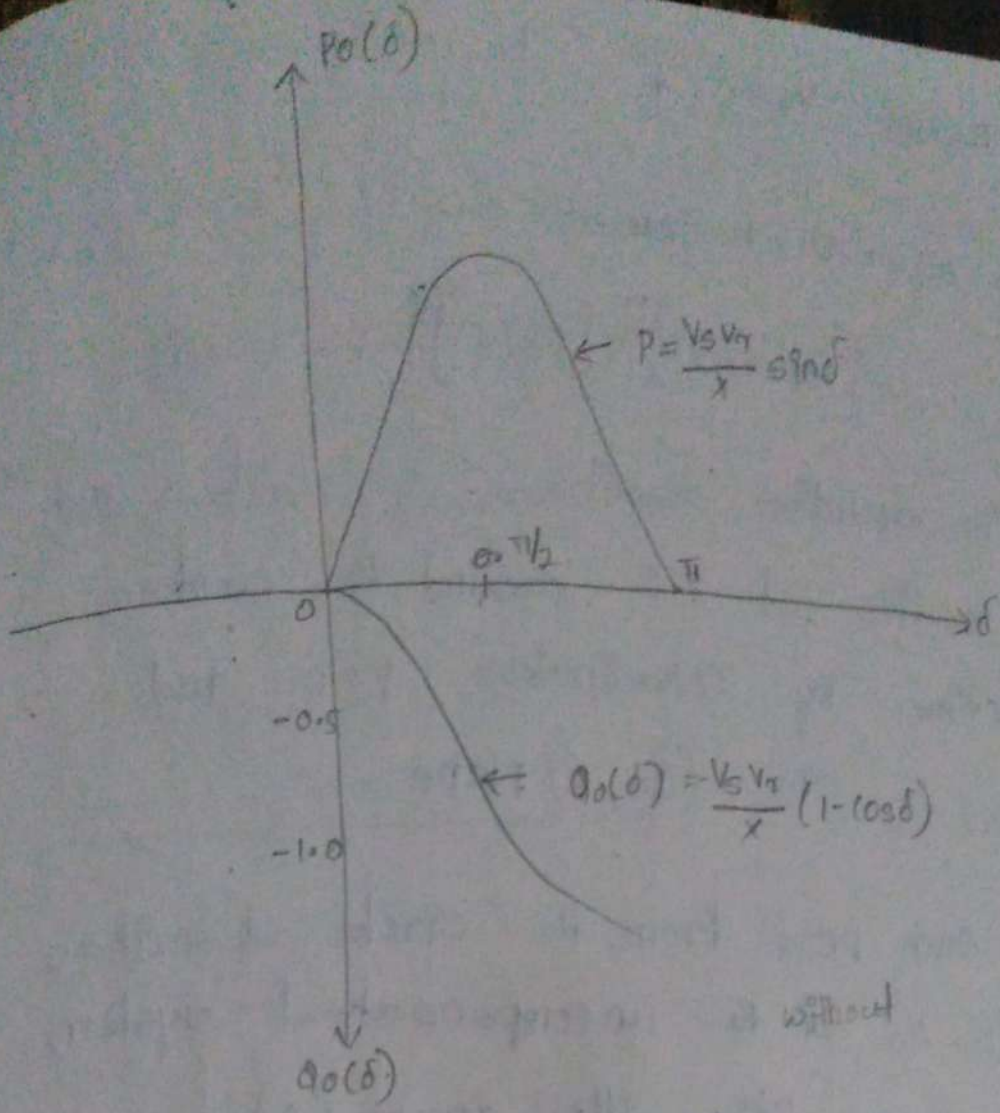


Fig (c) shows the relation b/w Real power $P_o(\delta)$, Reactive power with respect to phase angle.

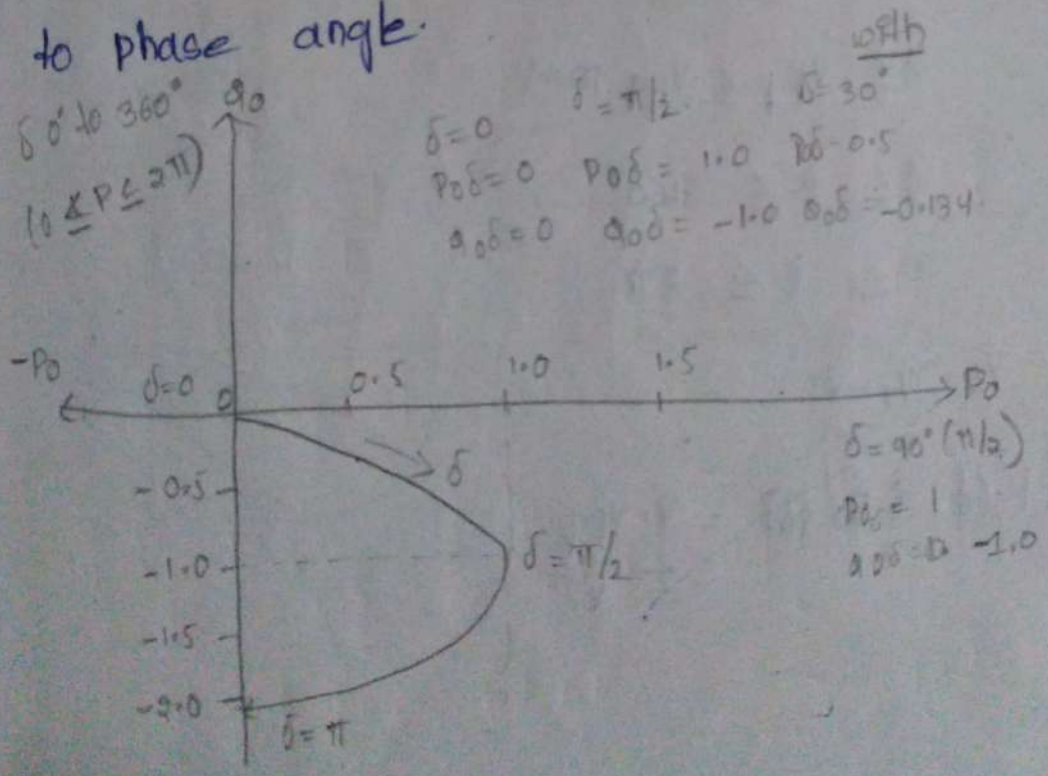

→ Assume $\frac{V_s \cdot V_r}{x} = 1$

The equation becomes.

$$[Q_0(\delta) + 1]^2 + [P_0(\delta)]^2 = 1 \quad \text{--- (4)}$$

This equation describes a circle with a radius of 1.0 around the centre defined by coordinates $P=0$ and $Q_r = -1$ in (Q_r, P) plane.

→ Each point from the circle describes P_0, Q_0 of the uncompensated system at a specific T/n angle (δ)

$$\therefore V_{pq} \neq 0$$

$$0 \leq V_{pq} \leq V_{pq} \text{ max.}$$

$$0 \leq \rho \leq 360^\circ$$

$$0 \leq \rho \leq 2\pi$$



$$V_s = V_r = V$$



$$P_0(\delta) \text{ \& \ } Q_0(\delta) = \frac{V_r V_{pq}}{x}$$

→ this is the radius of circle.

$$[P(\delta, P) - P_0(\delta)]^2 + [Q(\delta, P) - Q_0(\delta)]^2 = \left[\frac{V \cdot V_{pq \max}}{x} \right]^2$$

con

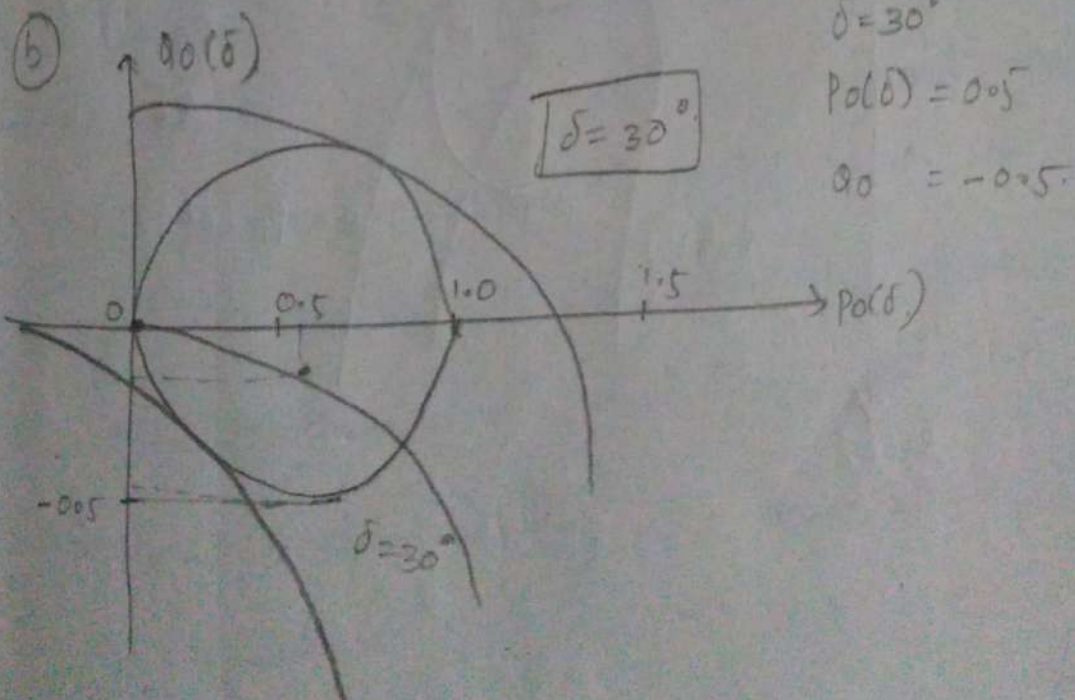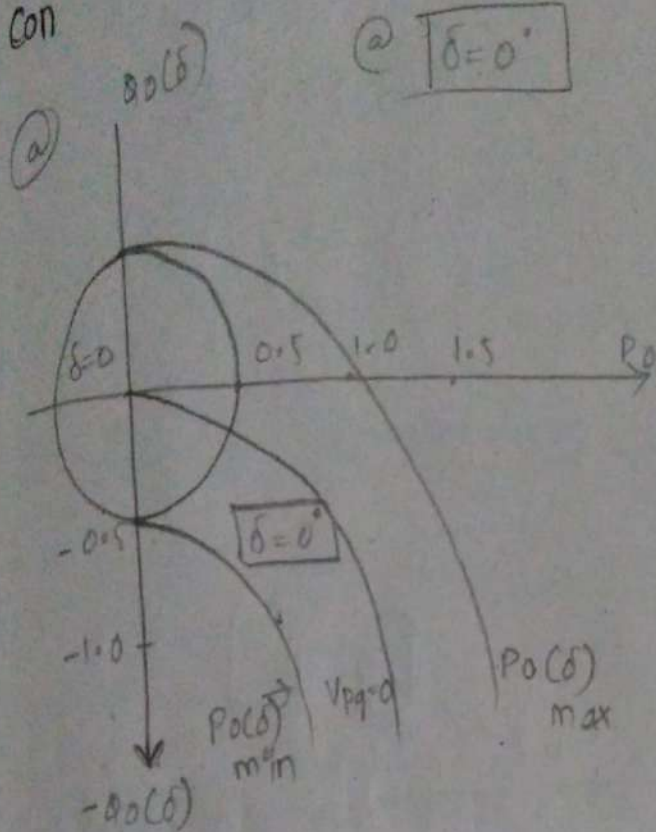

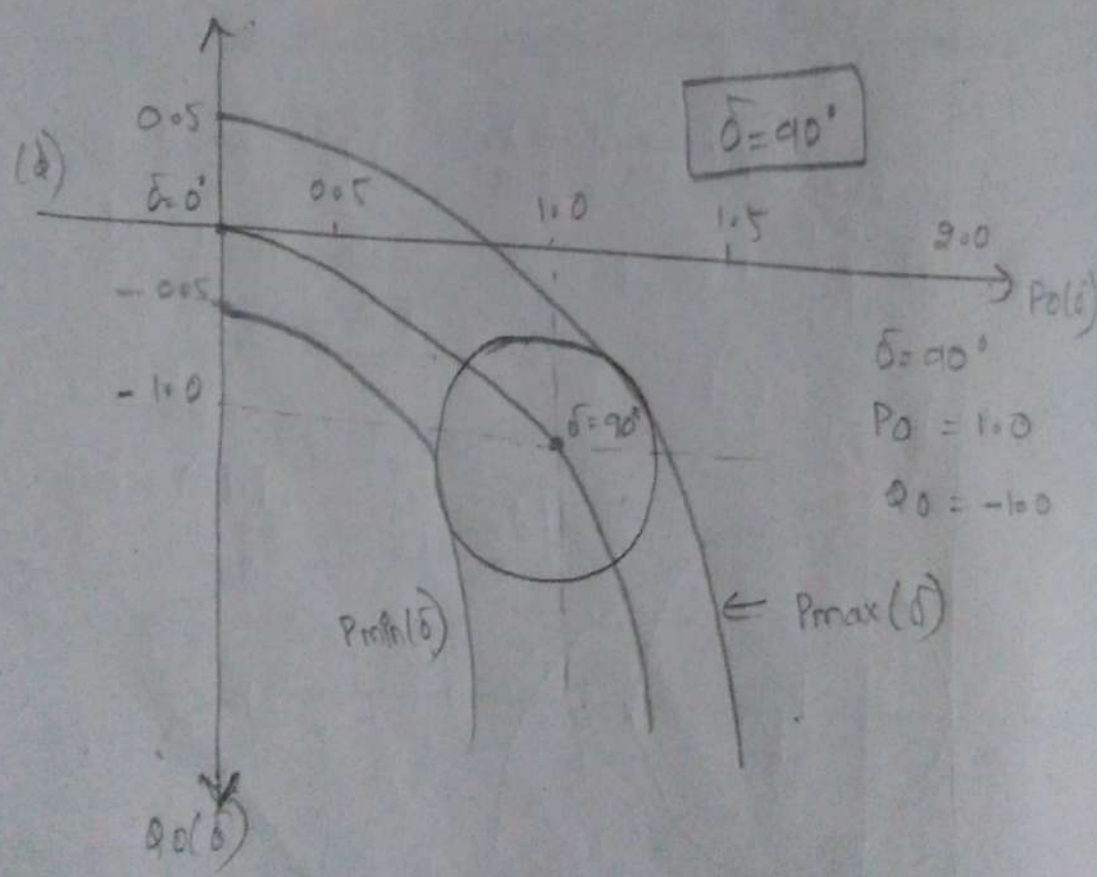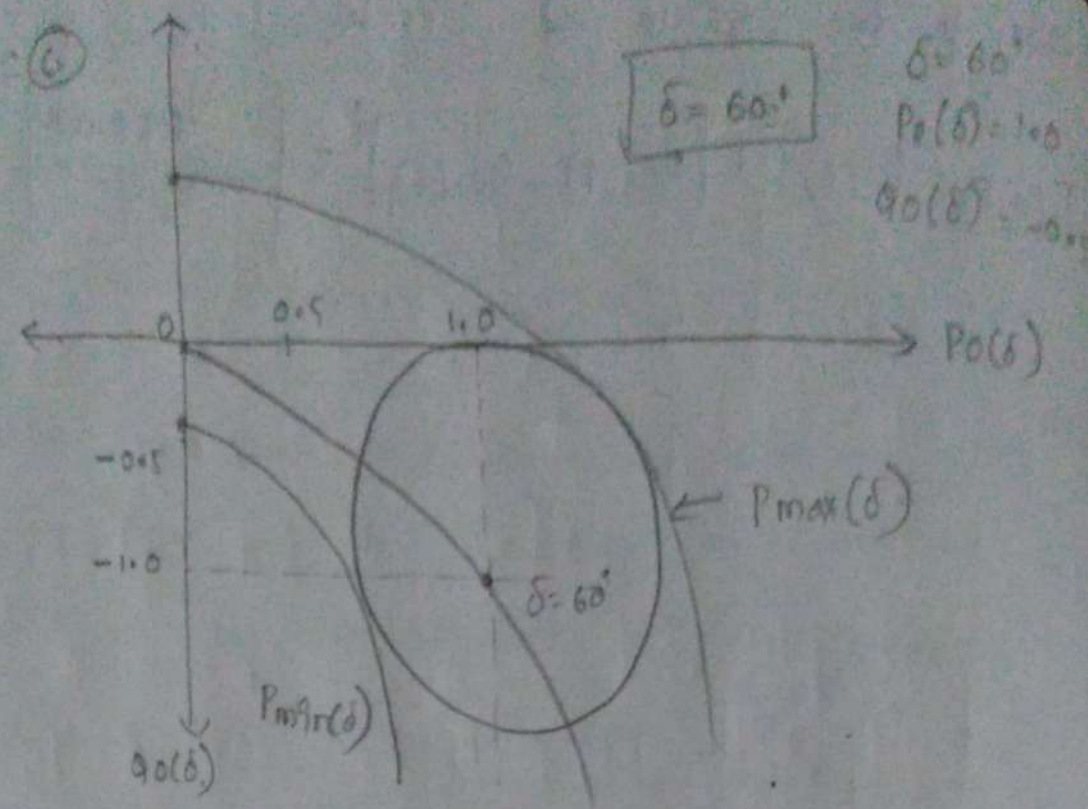

control region of the attainable power and Receiving & reactive power 'QR' with upfc control with a tln line,

$$\rightarrow \delta = 0^\circ, \text{ fig (a)}$$

$$\delta = 30^\circ, \text{ fig (b)}$$

$$\delta = 60^\circ, \text{ fig (c)}$$

$$\delta = 90^\circ, \text{ fig (d) shown above.}$$

\rightarrow In fig (a) illustrates, tln angle = 0

$$\delta = 0$$

$$V_{pq} = 0$$

$$P_0 = 0$$

$$Q_0 = 0$$

that means the system is at stand still at the origin of Q_r, P coordinates

\rightarrow This circle around origin at the

Q_r, P , gives the corresponding values of Real power and Reactive power.

\rightarrow similar control ch's for real power 'P' & reactive power 'Q' can be

absorbed at angles $0^\circ, 30^\circ, 60^\circ, 90^\circ$, shown
in fig (a), b, c, d,

→ At any t/n angle ' δ ' (0 to 360°), the
transmitted power ' P ' as well as real
power ' P_r ' can be controlled
freely by the vpf.c.

→ It is a unique capability to
control the real & reactive power
flow at any t/n angle.